

Registers & Counters

Logic and Digital System Design - CS 303

Erkay Savaş


Sabanci University

Registers

- Registers like counters are clocked sequential circuits
- A register is a group of flip-flops
 - Each flip-flop capable of storing one bit of information
 - An n-bit register
 - consists of n flip-flops
 - capable of storing n bits of information
 - besides flip-flops, a register usually contains combinational logic to perform some simple tasks
 - In summary
 - flip-flops to hold information
 - combinational logic to control the state transition

Counters


 
- A counter is essentially a register that goes through a predetermined sequence of states




Uses of Registers and Counters

- Registers are useful for storing and manipulating information
 - internal registers in microprocessors to manipulate data
- Counters are extensively used in control logic
 - PC (program counter) in microprocessors


4-bit Register

  


Register with Parallel Load

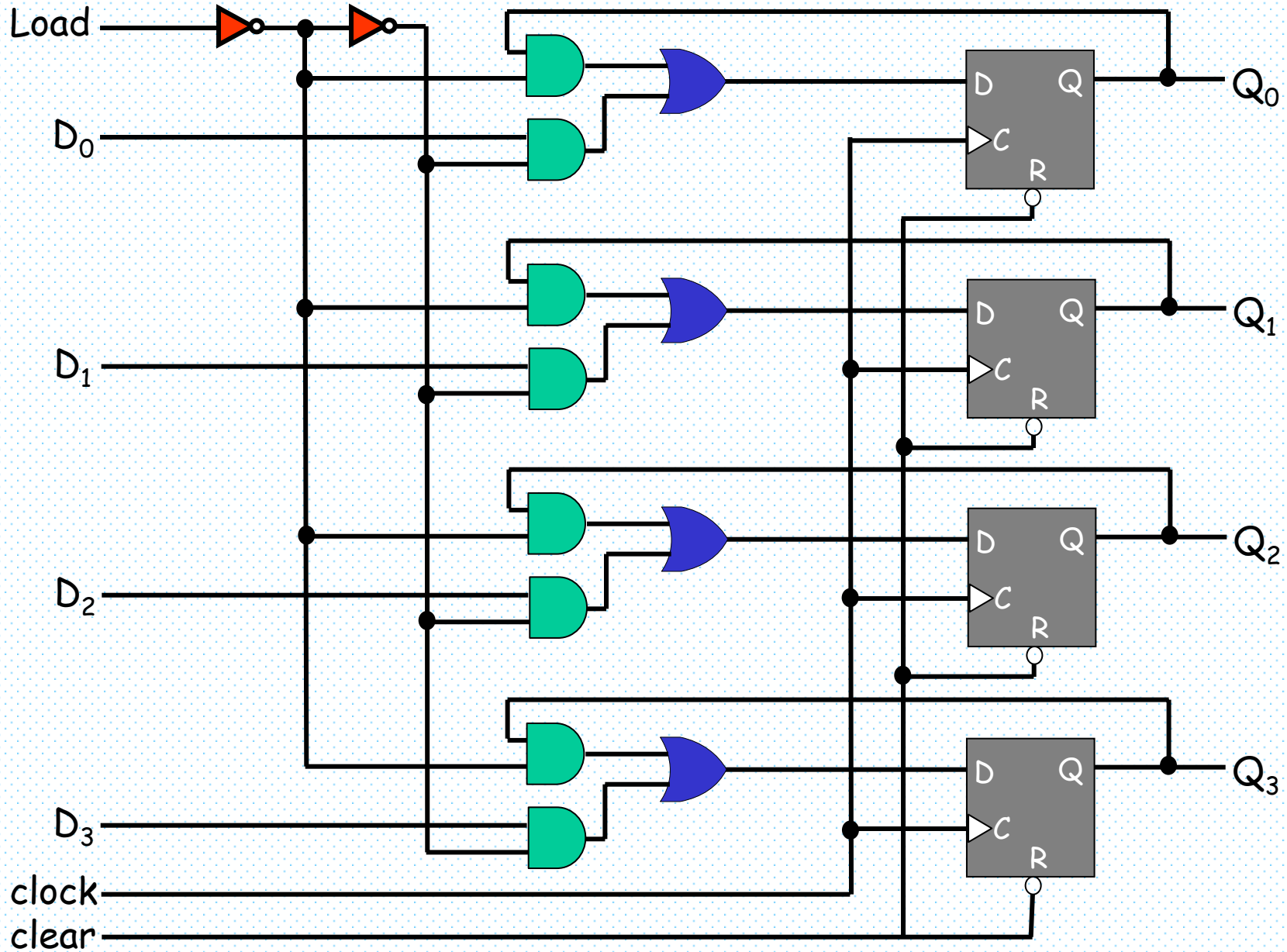


Loading Register

 

Register Transfer - 1

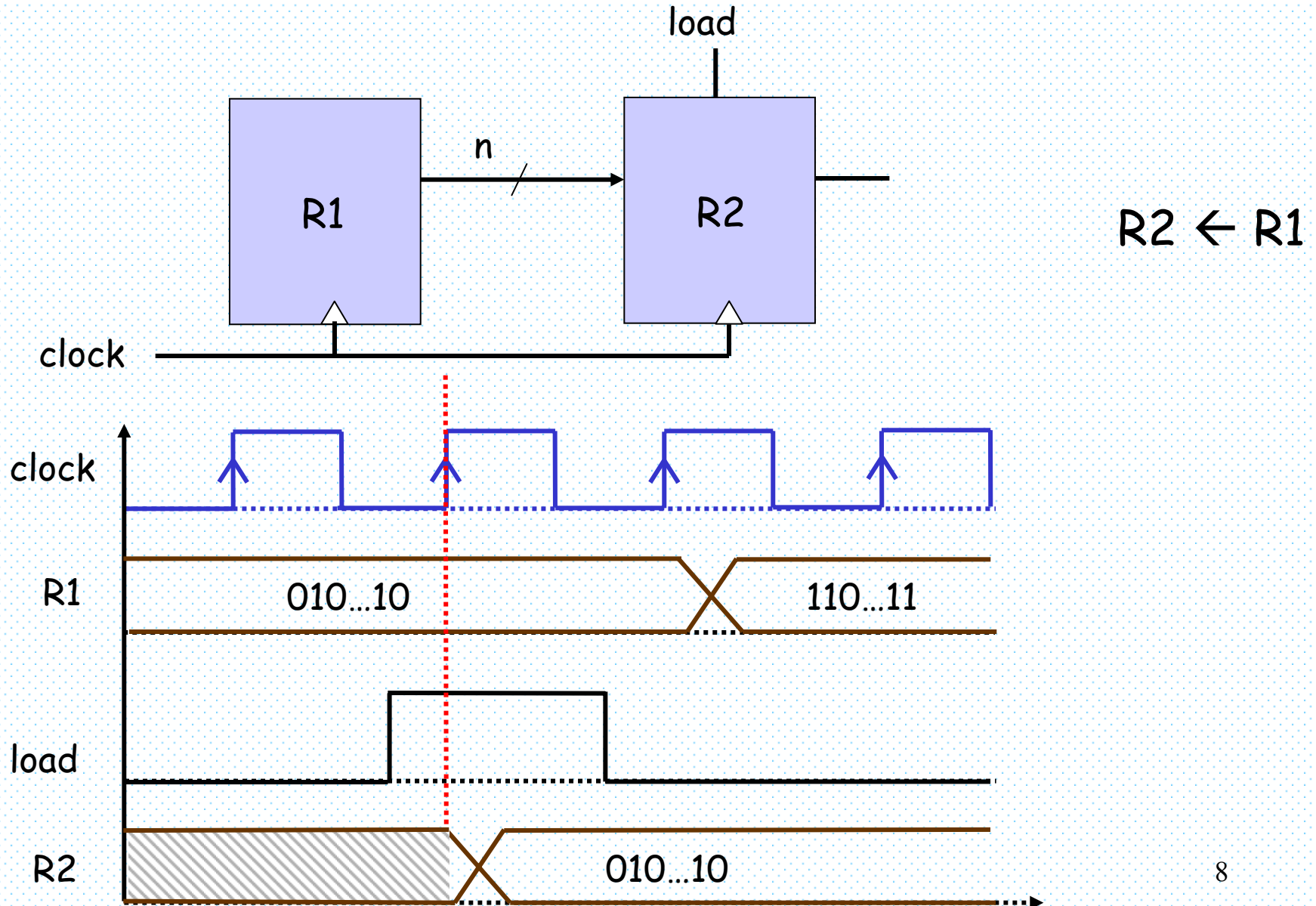


Register Transfer - 2

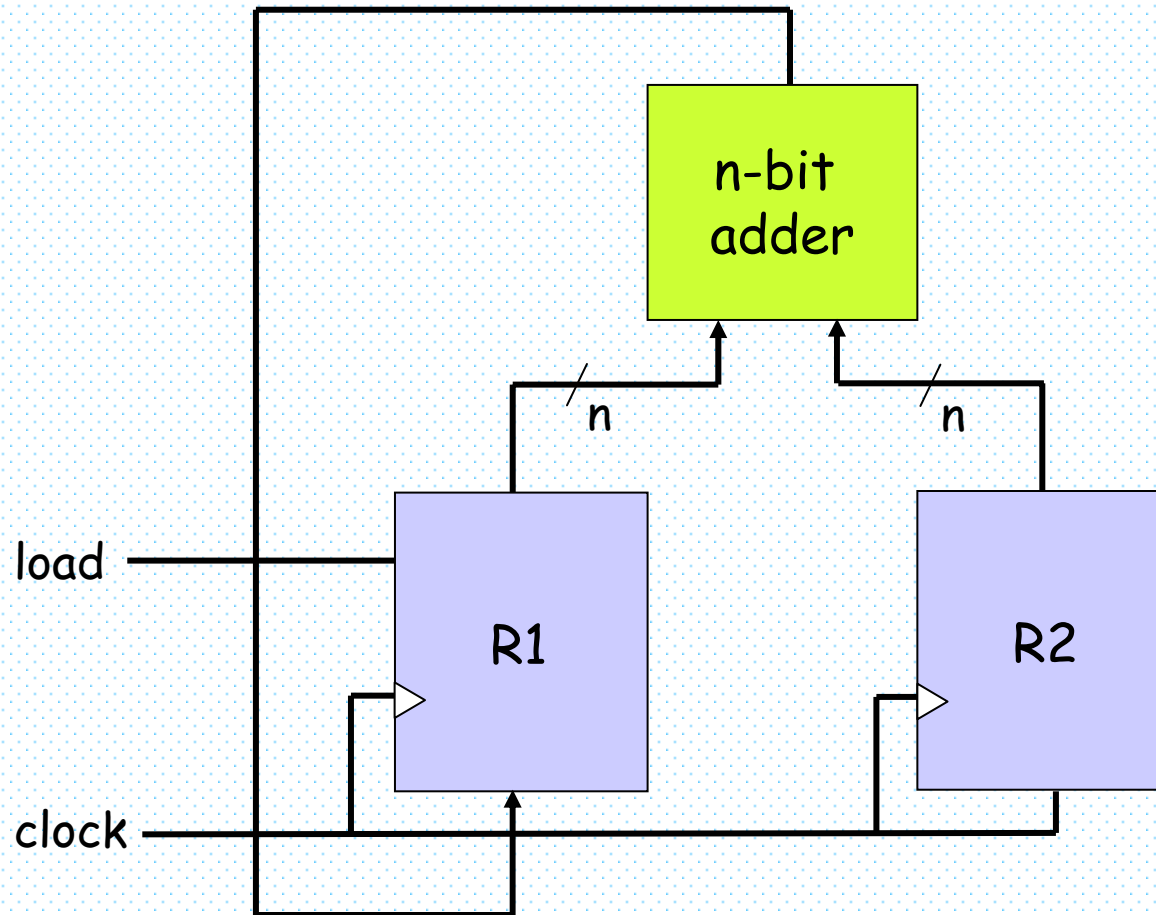


$$R1 \leftarrow R1 + R2$$

Datapath & Control Unit

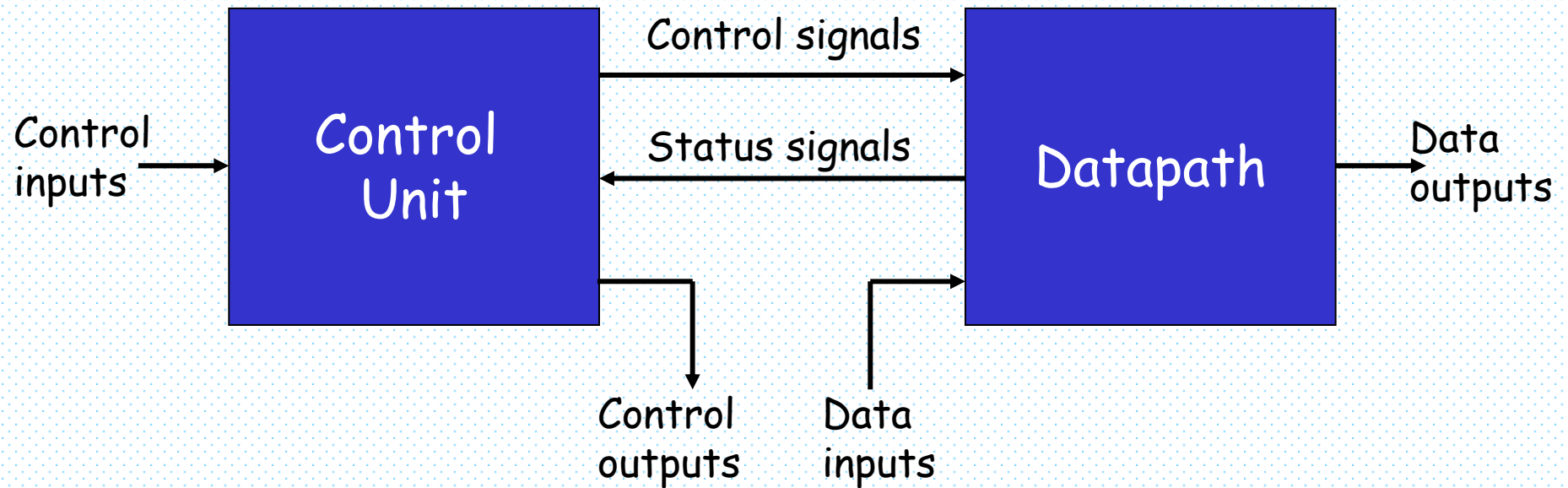

Shift Registers

 
- A register capable of shifting its information in one or both directions
 - Flip-flops in cascade



- The current state can be output in n clock cycles

Serial Mode

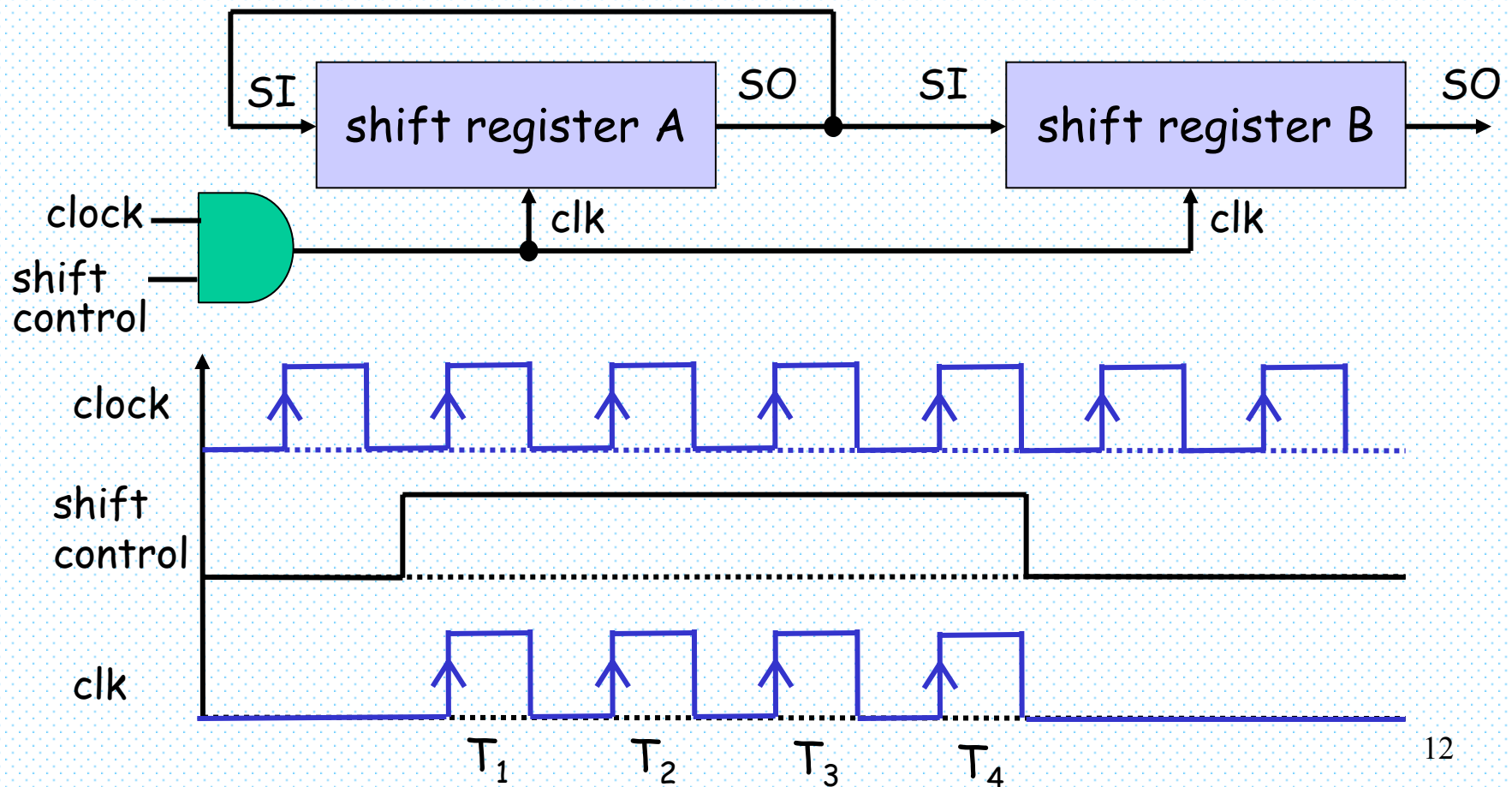- A digital system is said to operate in serial mode when information is transferred and manipulated one bit a time.



Serial Transfer


- Suppose we have two 4-bit shift registers

Timing pulse	Shift register A				Shift register B			
initial value	1	0	1	1	0	0	1	0
After T_1	1	1	0	1	1	0	0	1
After T_2	1	1	1	0	1	1	0	0
After T_3	0	1	1	1	0	1	1	0
After T_4	1	0	1	1	1	0	1	1

$$B \leftarrow A$$


Serial Addition

 - In digital computers, operations are usually executed in parallel, since it is faster
- Serial mode is sometimes preferred since it requires less equipment



Example: Serial Addition

- A and B are 2-bit shift registers

 

Designing Serial Adder - 1

$$Q(t+1) = JQ' + K'Q$$

Present state	Inputs		Next state	Output	Flip-flop inputs	
Q	x	y	Q	S	J _Q	K _Q
0	0	0	0	0	0	X
0	0	1	0	1	0	X
0	1	0	0	1	0	X
0	1	1	1	0	1	X
1	0	0	0	1	X	1
1	0	1	1	0	X	0
1	1	0	1	0	X	0
1	1	1	1	1	X	0

$$J_Q = xy$$

$$K_Q = x'y' = (x + y)'$$


$$S = x \oplus y \oplus Q$$

Designing Serial Adder - 2

$$J_Q = xy$$

$$K_Q = x'y' = (x + y)'$$


$$S = x \oplus y \oplus Q$$

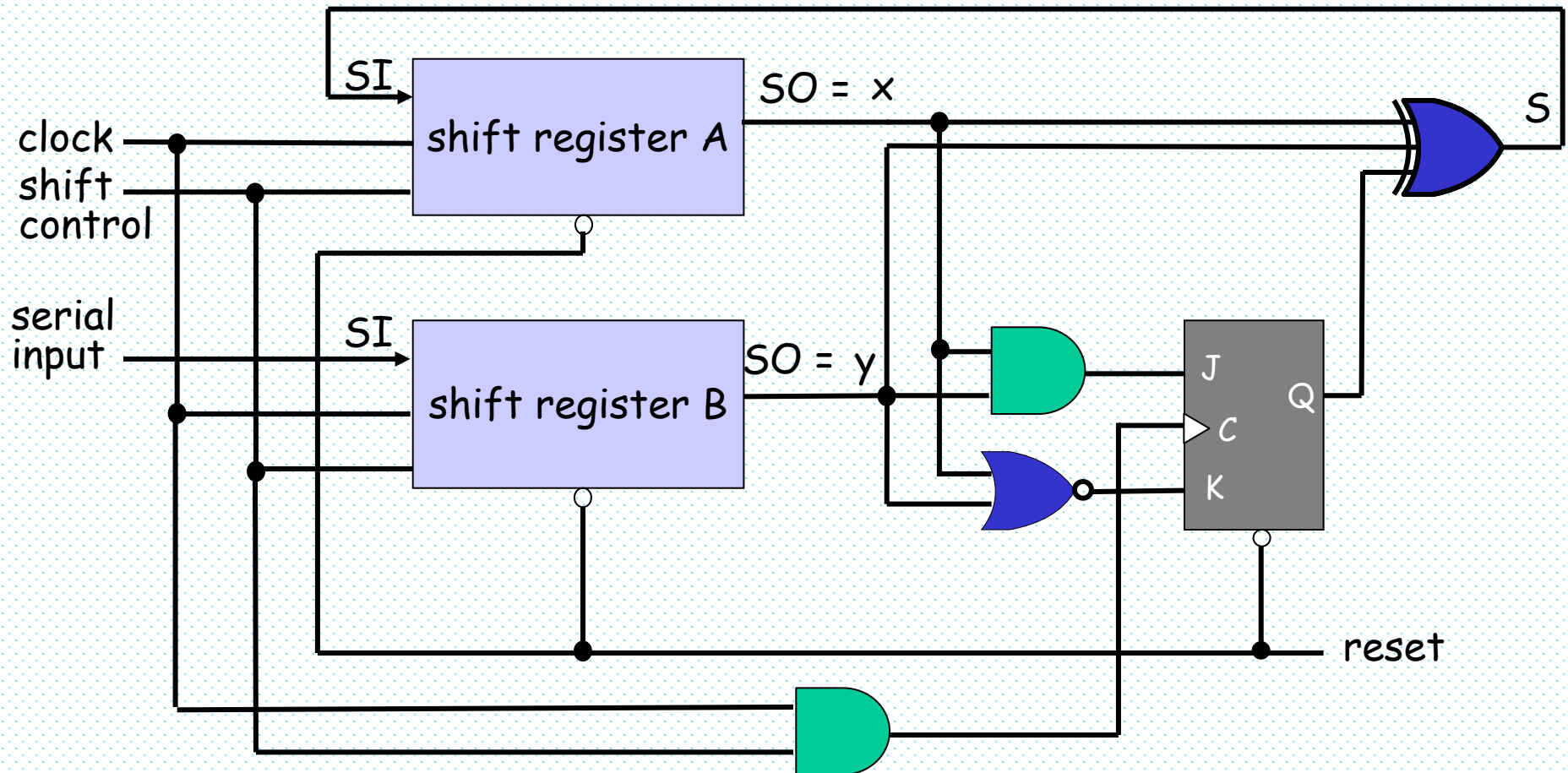

Universal Shift Register

- Capabilities:
 1. A *clear* control to set the register to 0.
 2. A *clock* input
 3. A *shift-right* control
 4. A *shift-left* control
 5. n input lines
 6. A *parallel-load* control
 7. n parallel output lines
 8. A *shift-control*

Universal Shift Register

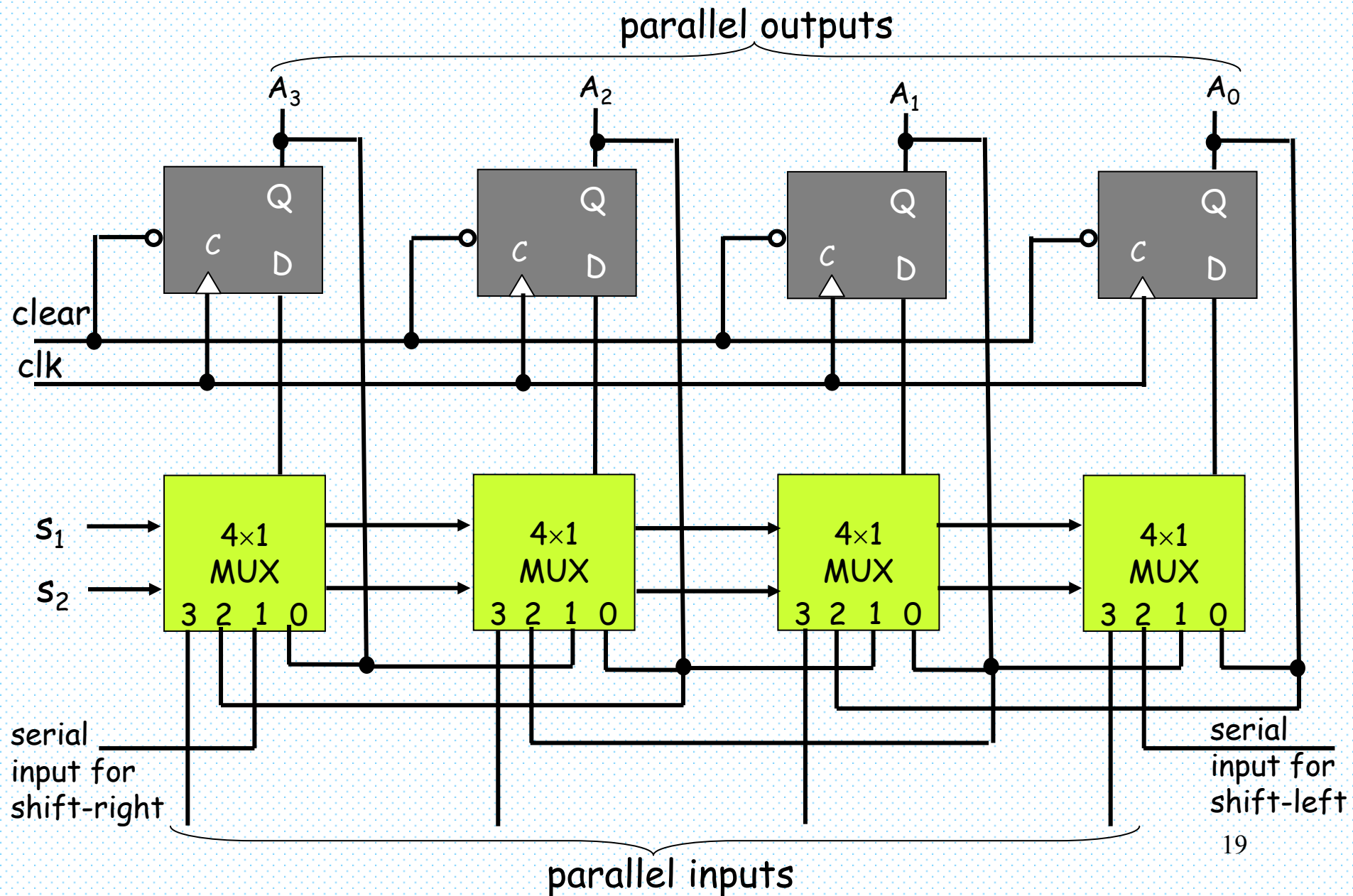

Universal Shift Register

Mode Control		
s_1	s_0	Register operation
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load

Counters

- A counter is basically a register that goes through a prescribed sequence of states upon the application of input pulses
 - input pulses are usually clock pulses
- Example: n-bit binary counter
 - count in binary from 0 to 2^n-1
- Classification
 1. Ripple counters
 - flip-flop output transition serves as *the* pulse to trigger other flip-flops
 2. Synchronous counters
 - flip-flops receive the same common clock as *the* pulse



Binary Ripple Counter

3-bit binary ripple counter


0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
0	0	0	0

- Idea:
 - to connect the output of one flip-flop to the *C* input of the next high-order flip-flop
- We need “complementing” flip-flops
 - We can use T flip-flops to obtain complementing flip-flops or
 - JK flip-flops with its inputs are tied together or
 - D flip-flops with complement output connected to the D input.

4-bit Binary Ripple Counter

  


4-bit Binary Ripple Counter

 

- Suppose the current state is 1100
- What is the next state?
- $A_0 = 1$ ($0 \rightarrow 1$)
- $A_1 = 1$ ($0 \rightarrow 1$)
- $A_2 = 0$ ($1 \rightarrow 0$)
- $A_3 = 1$
- next state: 1011
- Binary count-down counter

BCD Ripple Counter

- State diagram

 


BCD Ripple Counter


- State transitions

A_3	A_2	A_1	A_0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
0	0	0	0

BCD Ripple Counter with JK FFs

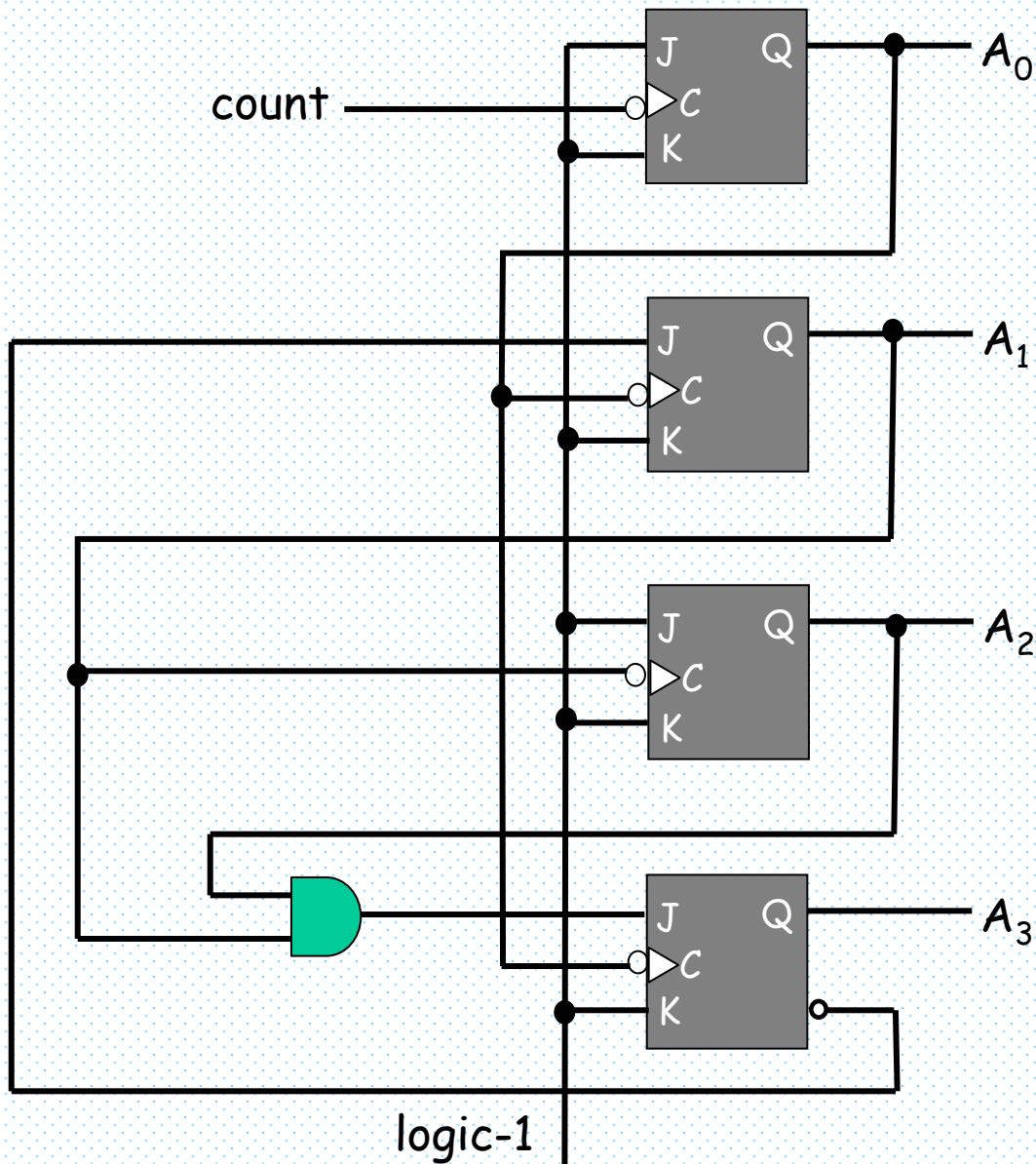

Multi-digit BCD Counter

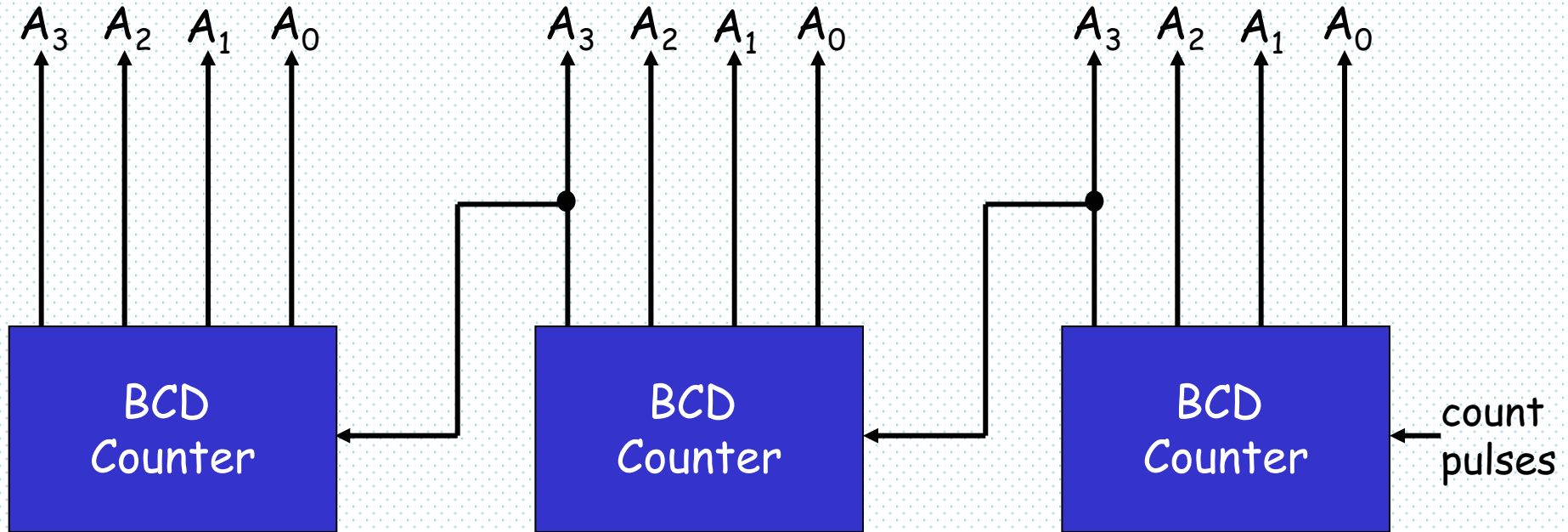


3-digit BCD counter

Synchronous Counters

- There is a common clock
 - that triggers all flip-flops simultaneously
 - If $T = 0$ or $J = K = 0$ the flip-flop does not change state.
 - If $T = 1$ or $J = K = 1$ the flip-flop does change state.
- Design procedure is so simple
 - no need for going through sequential logic design process
 - A_0 is always complemented
 - A_1 is complemented when $A_0 = 1$
 - A_2 is complemented when $A_0 = 1$ and $A_1 = 1$
 - so on


4-bit Binary Synchronous Counter

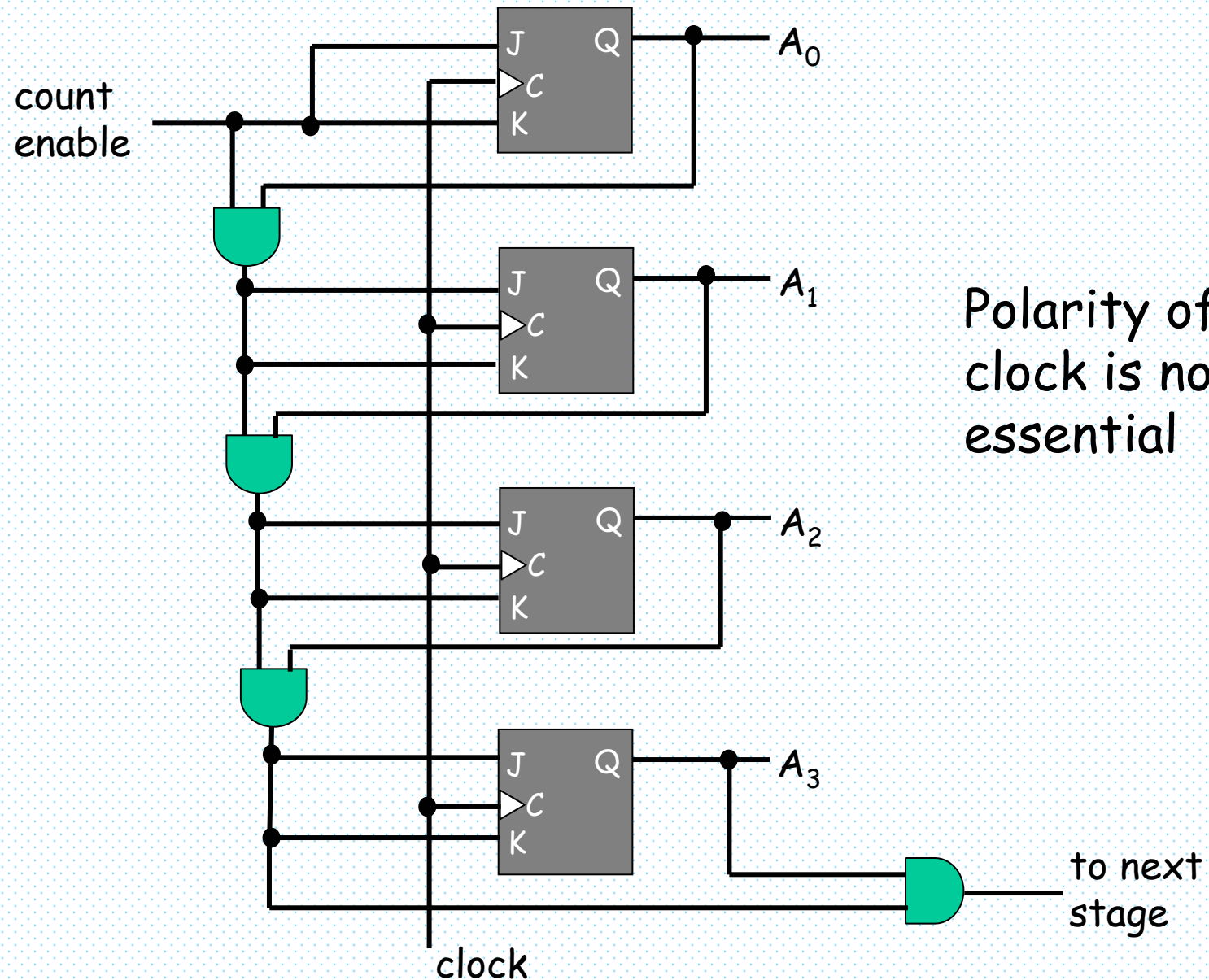

Up-Down Binary Counter

- When counting downward
 - the least significant bit is always complemented (with each clock pulse)
 - A bit in any other position is complemented if all lower significant bits are equal to 0.
 - For example: 0100
 - Next state: 0011
 - For example: 1100
 - Next state: 1011

Up-Down Binary Counter

 

- The circuit

Synchronous BCD Counter


- Better to apply the sequential circuit design procedure

Present state				Next state				output	Flip-Flop inputs			
A_8	A_4	A_2	A_1	A_8	A_4	A_2	A_1	Y	T_8	T_4	T_2	T_1
0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	1	0	0	1	0	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	0	1
0	0	1	1	0	1	0	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	0	1
0	1	0	1	0	1	1	0	0	0	0	1	1
0	1	1	0	0	1	1	1	0	0	0	0	1
0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	0	1
1	0	0	1	0	0	0	0	1	1	0	0	1

Synchronous BCD Counter

- The flip-flop input equations
 - $T_1 = 1$
 - $T_2 = A_8' A_1$
 - $T_4 = A_2 A_1$
 - $T_8 = A_8 A_1 + A_4 A_2 A_1$
- Output equation
 - $y = A_8 A_1$
- Cost
 - Four T flip-flops
 - four 2-input AND gates
 - one OR gate
 - one inverter

Binary Counter with Parallel Load

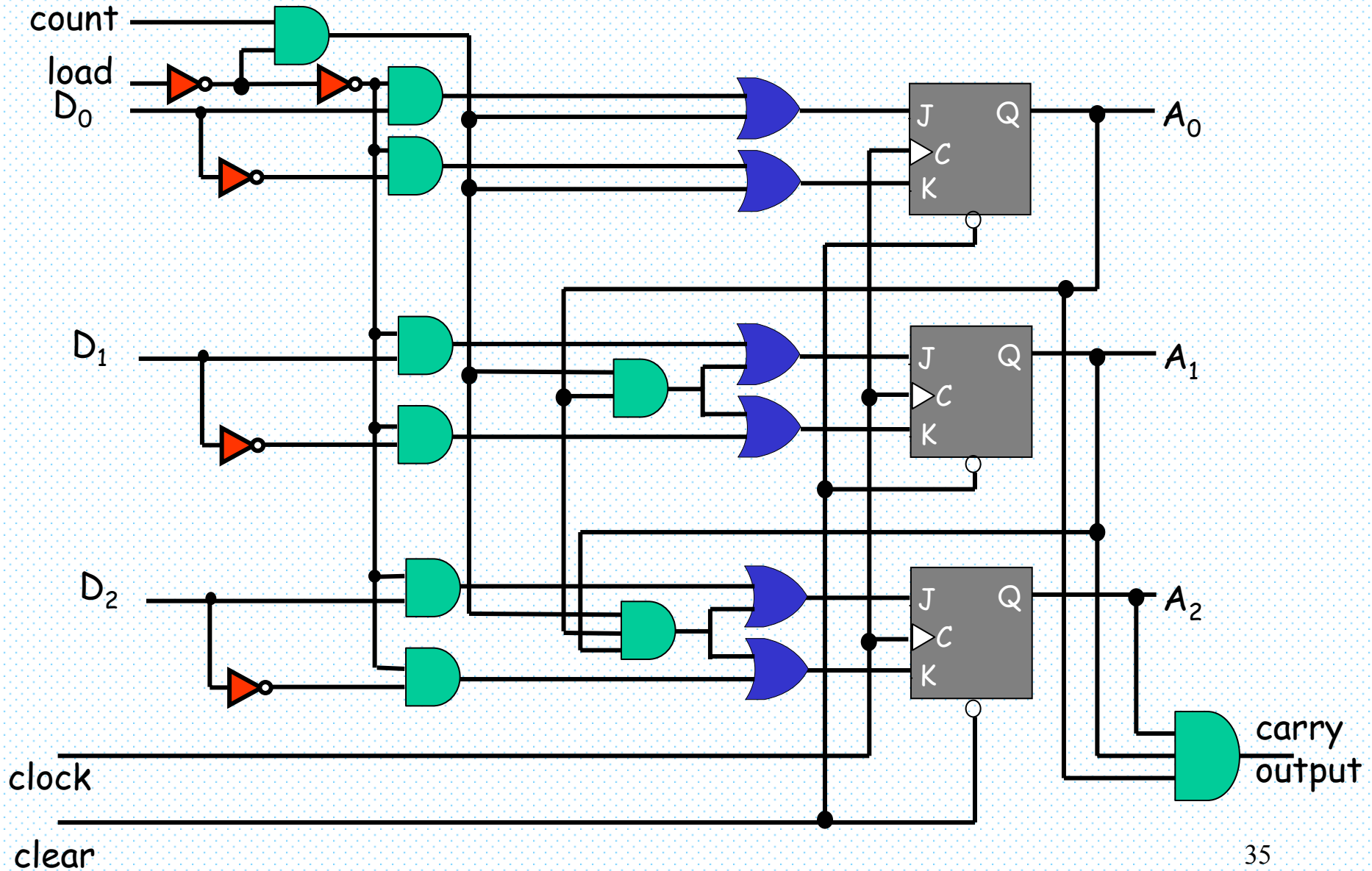

Binary Counter with Parallel Load


Function Table

clear	clock	load	Count	Function
0	X	X	X	clear to 0
1	↑	1	X	load inputs
1	↑	0	1	count up
1	↑	0	0	no change

Other Counters


- Ring Counter

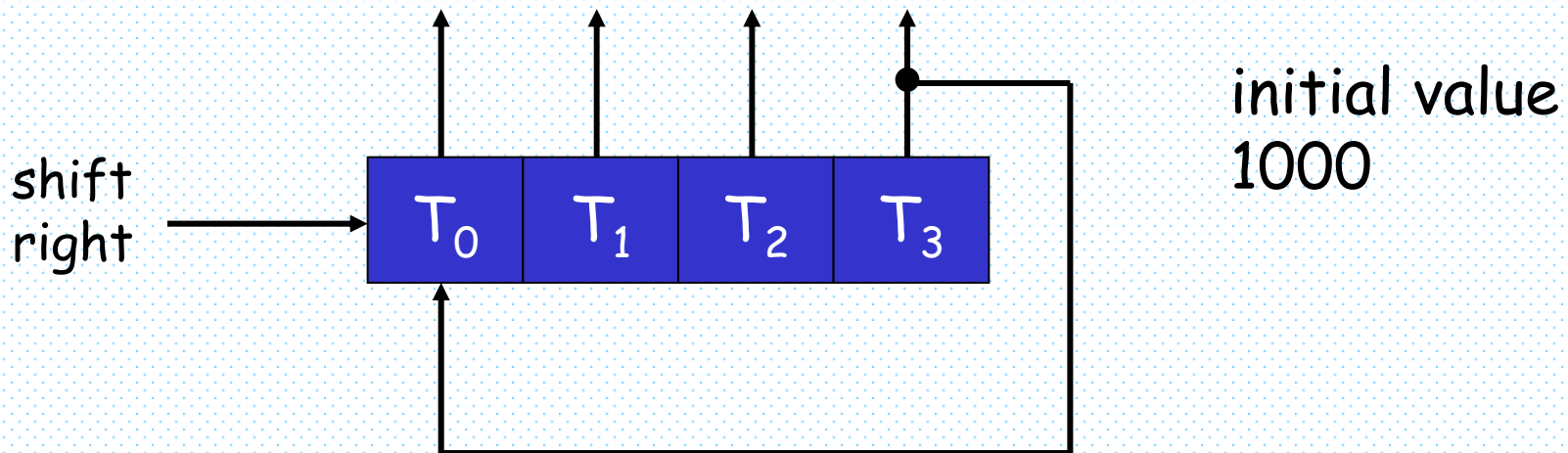- Timing signals control the sequence of operations in a digital system
- A ring counter is a circular shift register with only one flip-flop being set at any particular time, all others are cleared.




Ring Counter

- Sequence of timing signals

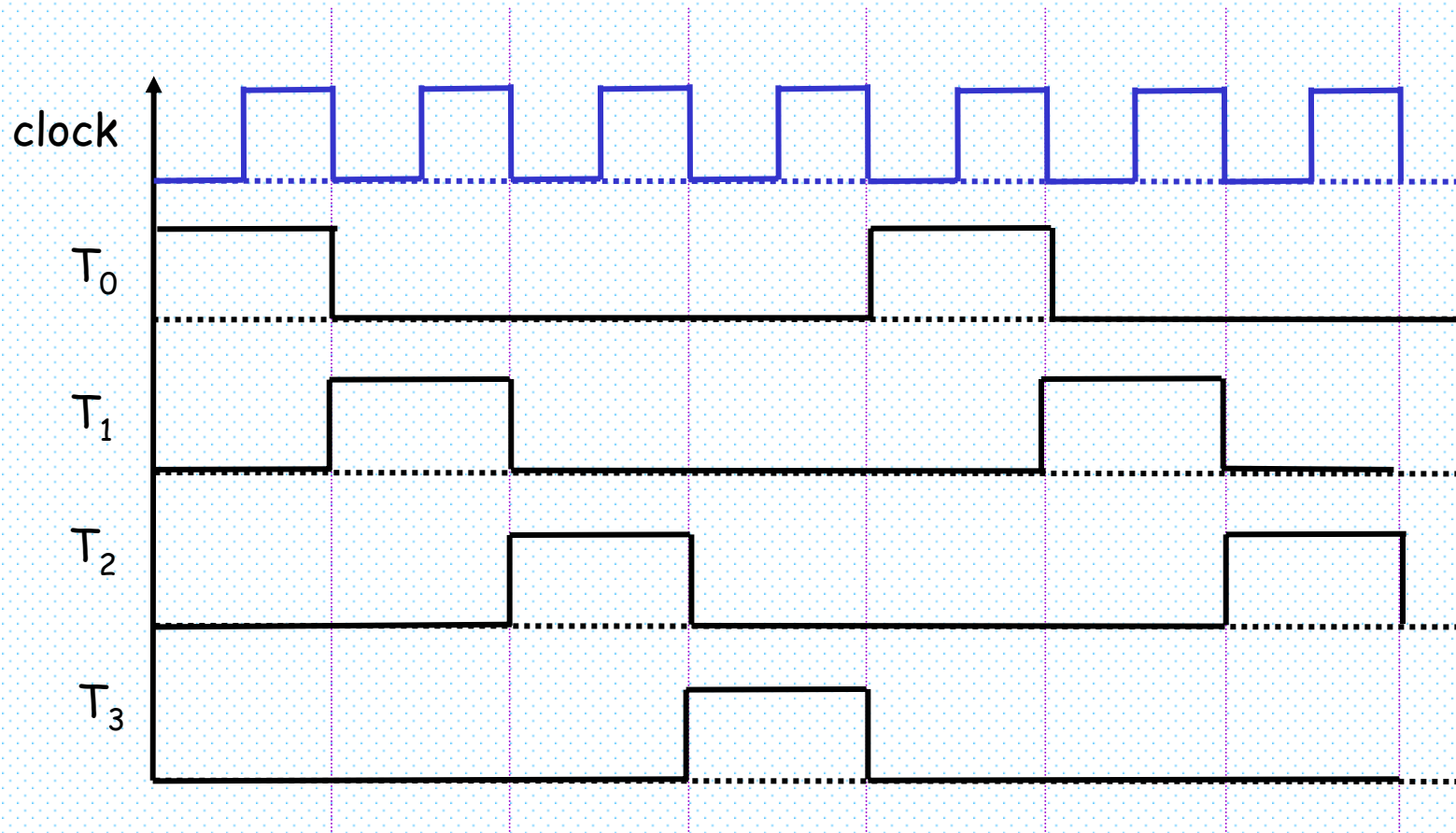

Ring Counter

 - To generate 2^n timing signals,
 - we need a shift register with 2^n flip-flops
- or, we can construct the ring counter with a binary counter and a decoder



Cost:


- 2 flip-flop
- 2-to-4 line decoder

Cost in general case:

- n flip-flops
- n -to- 2^n line decoder
 - 2^n n -input AND gates

Johnson Counter

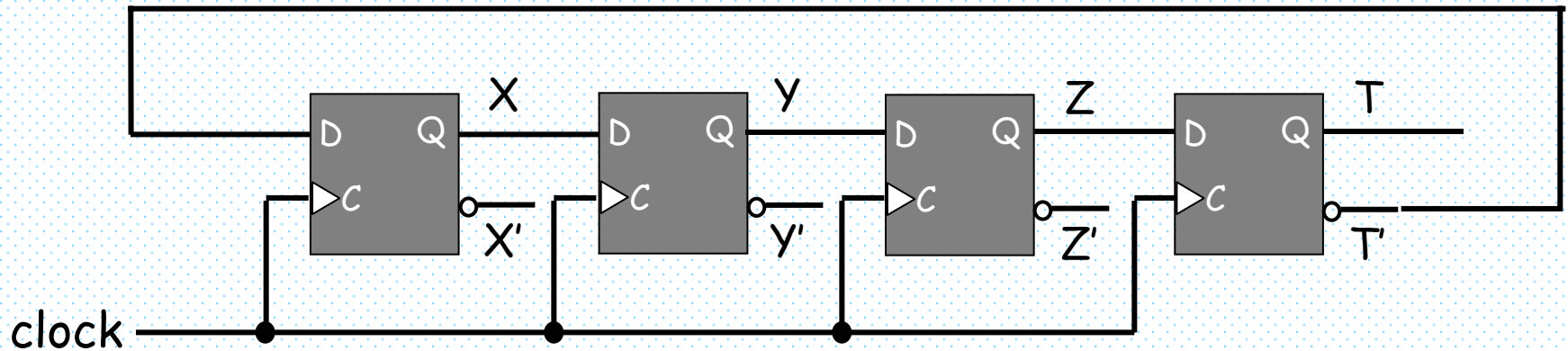- A k-bit ring counter can generate k distinguishable states
- The number of states can be doubled if the shift register is connected as a switch-tail ring counter




Johnson Counter

- Count sequence and required decoding

sequence number	Flip-flop outputs				Output
	X	Y	Z	T	
1	0	0	0	0	$X'T'$
2	1	0	0	0	XY'
3	1	1	0	0	YZ'
4	1	1	1	0	ZT'
5	1	1	1	1	XT
6	0	1	1	1	$X'Y$
7	0	0	1	1	$Y'Z$
8	0	0	0	1	$Z'T$



Johnson Counter

- Decoding circuit

 

Unused States in Counters

- 4-bit Johnson counter

  

Johnson Counter

Inputs				Outputs			
X	Y	Z	T	X	Y	Z	T
0	0	0	0	1	0	0	0
1	0	0	0	1	1	0	0
1	1	0	0	1	1	1	0
1	1	1	0	1	1	1	1
1	1	1	1	0	1	1	1
0	1	1	1	0	0	1	1
0	0	1	1	0	0	0	1
0	0	0	1	0	0	0	0
1	0	1	0	1	1	0	1
1	1	0	1	0	1	1	0
0	1	1	0	1	0	1	1
1	0	1	1	0	1	0	1
0	1	0	1	0	0	0	0
0	0	1	0	1	0	0	1
1	0	0	1	0	1	0	0
0	1	0	0	1	0	0	0

K-Maps

XY \ ZT		00	01	11	10
00	1			1	
01	1			1	
11	1			1	
10	1			1	

$$X = T$$

XY \ ZT		00	01	11	10
00					
01					
11	1	1	1	1	
10	1	1	1	1	

$$Y = X$$

XY \ ZT		00	01	11	10
00					
01				1	1
11	1	1	1	1	1
10					


$$Z = XY + YZ$$

XY \ ZT		00	01	11	10
00				1	1
01				1	1
11				1	1
10				1	1

$$T = Z$$

Unused States in Counters

- Remedy

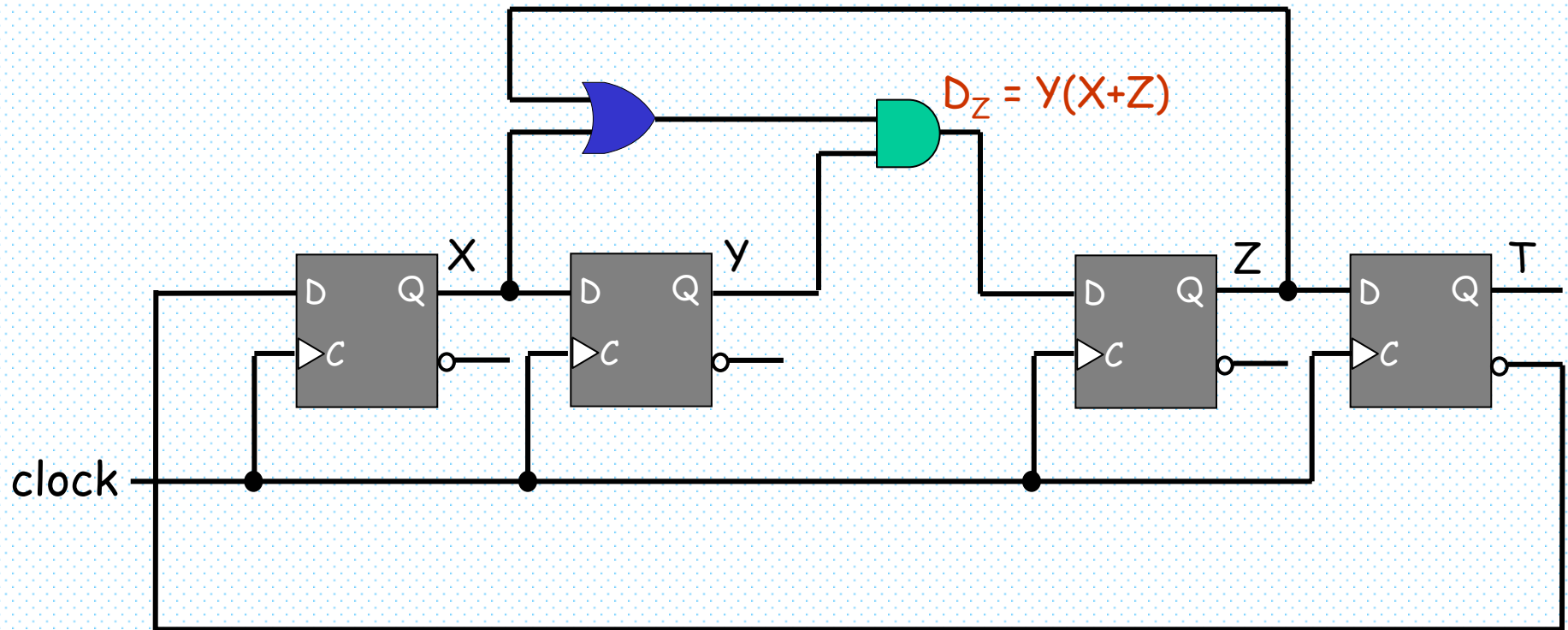

Unused States in Counters

- State diagram

