

# *VHDL* *Memory Models*

EL 310  
Erkay Savaş  
Sabancı University


# ROM

```
library ieee;
use ieee.std_logic_1164.all;
entity rom16x8 is
    port(address: in integer range 0 to 15;
          data: out std_ulogic_vector(7 downto 0));
end entity;
architecture sevenseg of rom16x8 is
    type rom_array is array (0 to 15) of std_ulogic_vector (7
        downto 0);

    constant rom: rom_array := ( "11111011", "00010010",
        "10011011", "10010011", "01011011", "00111010",
        "11111011", "00010010", "10100011", "10011010",
        "01111011", "00010010", "10101001", "00110110",
        "11011011", "01010010");

begin
    data <= rom(address);
end architecture;
```

# Static RAM

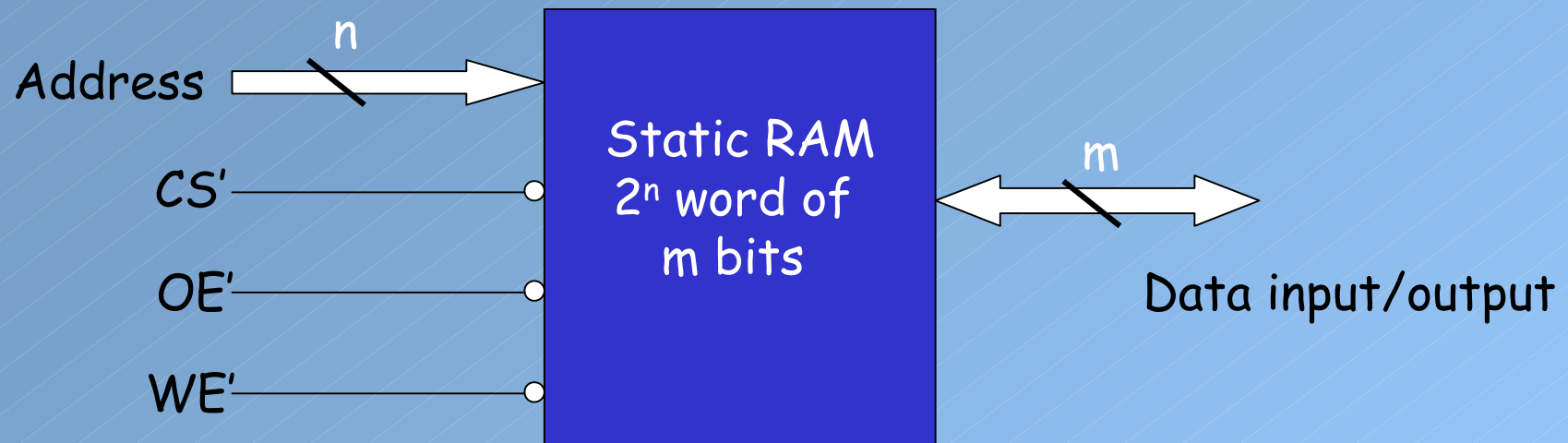


CS' - when asserted low, memory read and write operations are possible.

OE' - when asserted low, memory output is enabled onto an external bus

WE' - when asserted low, memory can be written
 
# *A Cell of Static RAM*

- The RAM contains address decoders and a memory array.
- A cell of RAM that stores one bit of data



Read mode:  $SEL' = '0'$  and  $WR' = '1'$ , ( $G='0'$ ) and  $data\_out = Q$

Write mode:  $SEL' = '0'$  and  $WR' = '0'$ , ( $G='1'$ ) and  $Q = data\_in$


When  $SEL' = '1'$  or  $WR' = '1'$ , the data is stored in the latch

When  $SEL' = '1'$ ,  $data\_out = 'Z'$

# *Truth Table of Static RAM*


$CS'$	$OE'$	$WE'$	Mode	I/O pins
H	X	X	not selected	high-Z
L	H	H	output disabled	high-Z
L	L	H	read	data_out
L	X	L	write	data_in

# 6116 Static CMOS RAM

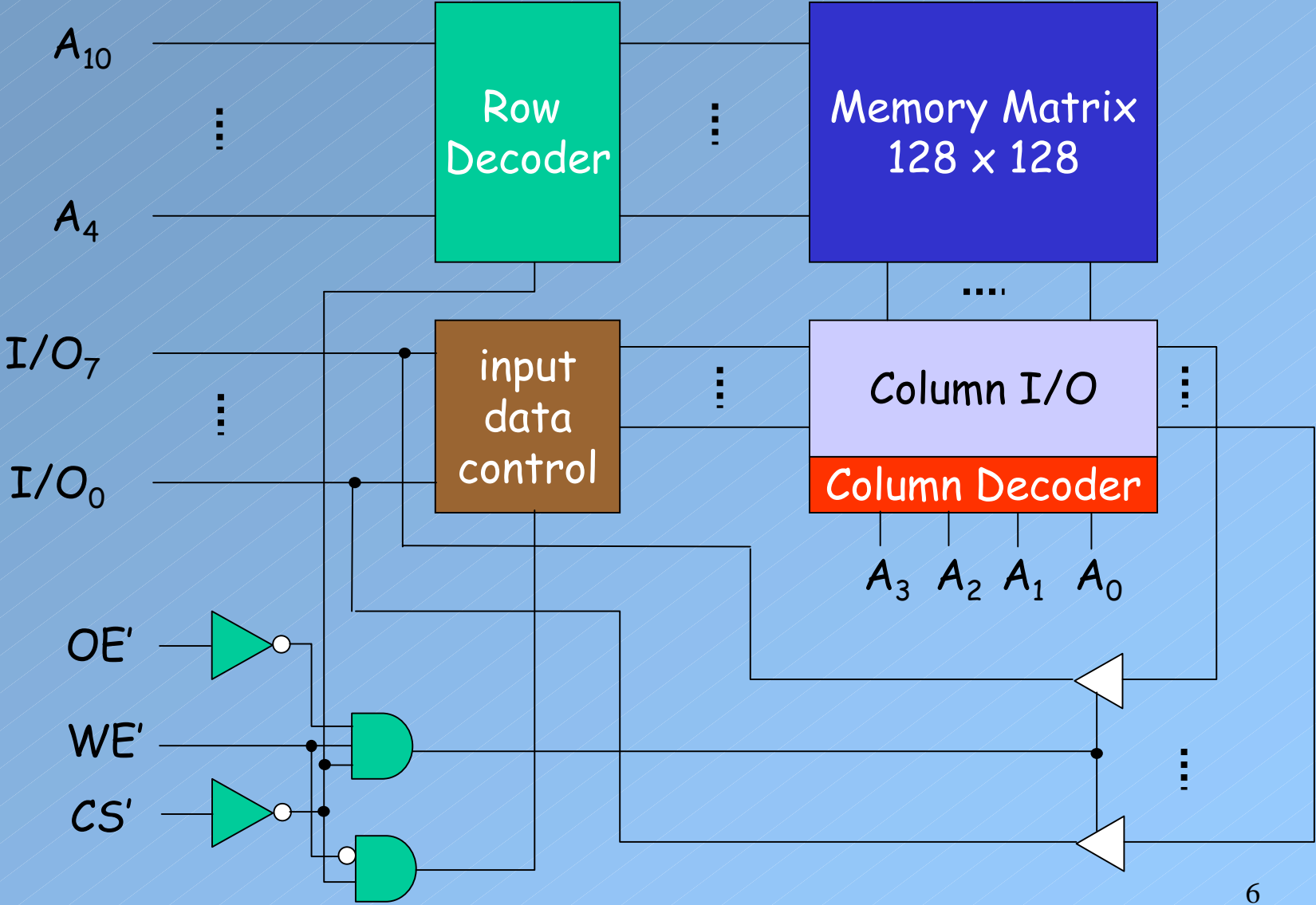

# Read Cycle Timing I

$CS' = 0, OE' = 0, WE' = 1$

 

The address must be stable for the read cycle time,  $t_{RC}$


After the address changes, the old data remains at the output for a time  $t_{OH}$

Then there is a transition period during which the data may change (cross-hatching section)

The new data is stable at the memory after the address access time  $t_{AA}$
 
# Read Cycle Timing II


Address is stable,  $OE' = 0$ ,  $WE' = 1$





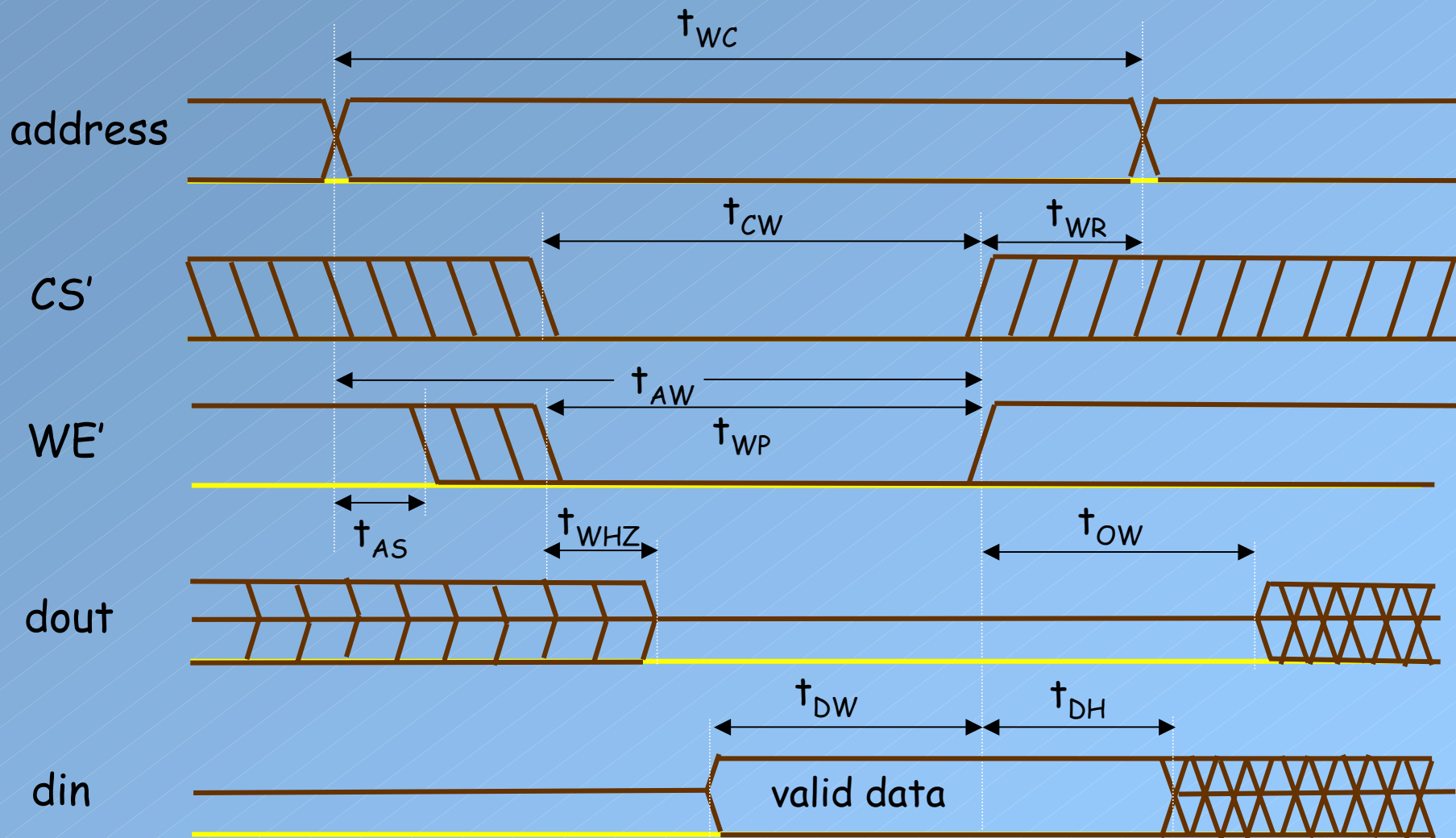
## *WE' Controlled Write Cycle Time ( $OE' = 0$ ).*

- CS' goes low before or at the same time as WE' goes low
- WE' goes high before or at the same time as CS' goes high


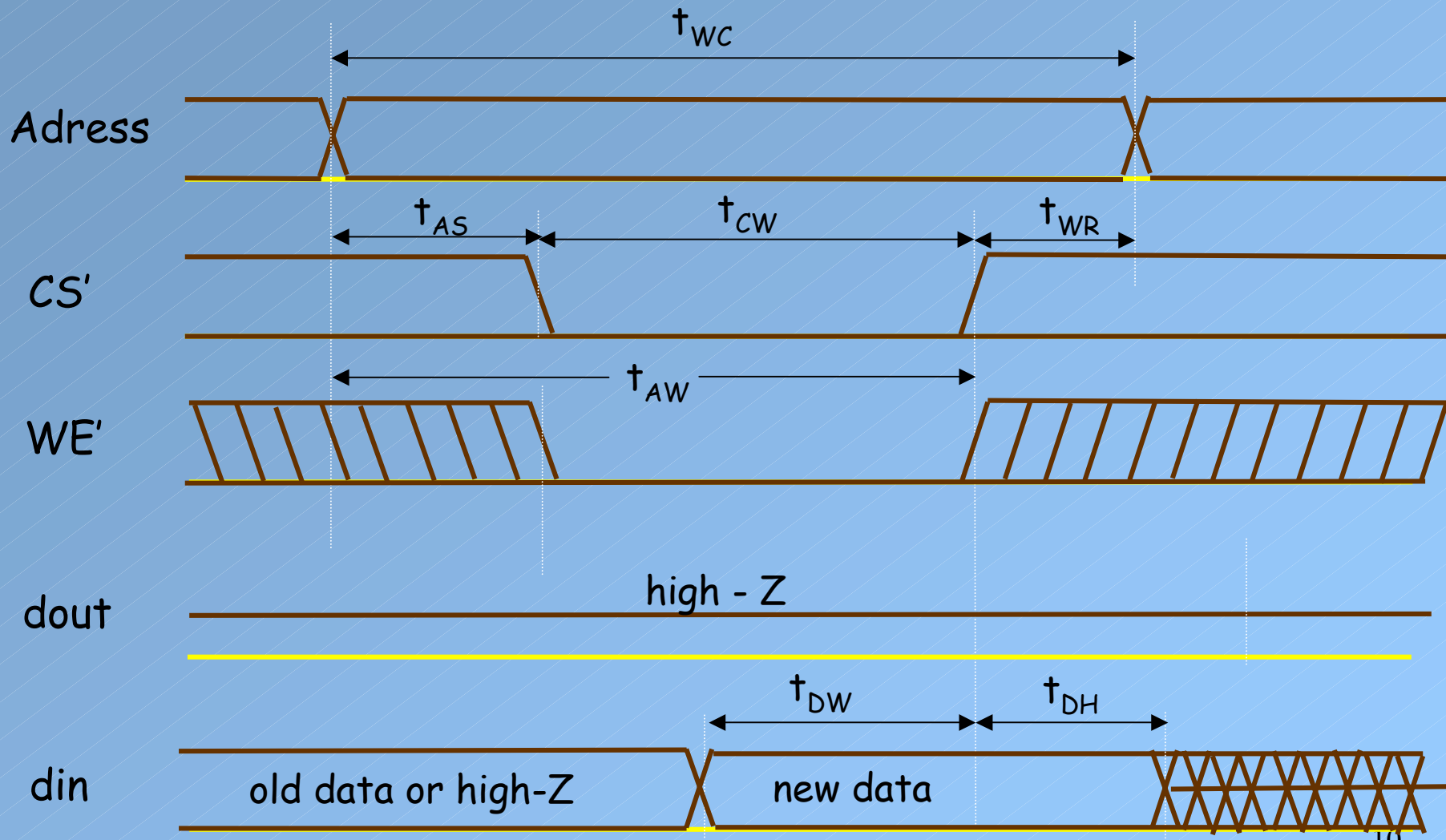
## *CS' controlled write cycle time ( $OE' = 0$ ).*

- WE' goes low before or at the same time as CS' goes low
- CS' goes high before or at the same time as WE' goes high



## *Writing to the Memory*

- In both  $CS'$  and  $WE'$  controlled write cycles, writing to memory occurs when both  $CS'$  and  $WE'$  are low,
- writing is completed when either one of these signals goes high.

# Timing Specifications for CMOS SRAM

Parameter	Symbol	61162-2		43258A-25	
		min	max	min	max
Read Cycle Time	$t_{RC}$	120	-	25	-
Address Access Time	$t_{AA}$	-	120	-	25
Chip Select Access Time	$t_{ACS}$	-	120	-	25
Chip selection to output in low-Z	$t_{CLZ}$	10	-	3	-
Output enable to output valid	$t_{OE}$	-	80	-	12
Output enable to output in low-Z	$t_{OLZ}$	10	-	0	-
Chip de-selection to output in high-Z	$t_{CHZ}$	10	40	3	10
Chip disable to output in high-Z	$t_{OHZ}$	10	40	3	10
Output hold from address change	$t_{OH}$	10	-	3	-

# Timing Specifications for CMOS SRAM

Parameter	Symbol	61162-2		43258A-25	
		min	max	min	max
Write Cycle Time	$t_{WC}$	120	-	25	-
Chip selection to end of write	$t_{CW}$	70	-	15	-
Address valid to end of write	$t_{AW}$	105	-	15	-
Address setup time	$t_{AS}$	0	-	0	-
Write pulse width	$t_{WP}$	70	-	15	-
Write recovery time	$t_{WR}$	0	-	0	-
Write enable to output in high-Z	$t_{WHZ}$	10	35	3	10
Data valid to end of write	$t_{DW}$	35	-	12	-
Data hold from end of write	$t_{DH}$	0	-	0	-
Output active from end of write	$t_{OW}$	10	-	0	-

# *Simple Memory Model*

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_arith.all;  
  
entity ram6116 is  
    port(address: in unsigned(7 downto 0);  
          data: inout std_logic_vector(7 downto 0);  
          WE_b, CS_b, OE_b: in std_ulogic);  
end entity ram6116;
```

# Simple Memory Model

```
architecture simple_ram of ram6116 is
  type ram_type is array (0 to 2**8-1) of
    std_logic_vector(7 downto 0);
  signal ram1: ram_type:= (others => (others => '0'));
begin
  process
  begin
    data <= (others => 'Z');  -- chip is not selected
    if (CS_b = '0') then
      if rising_edge(WE_b) then -- write
        ram1(conv_integer(address'delayed)) <= data;
        wait for 0 ns;
      end if;
      if WE_b = '1' and OE_b = '0' then -- read
        data <= ram1(conv_integer(address));
      else
        data <= (others => 'Z');
      end if;
    end if;
    wait on WE_b, CS_b, OE_b, address;
  end process; end simple_ram;
```

# *Synthesizeable Memory Model*

```
architecture simple_ram of ram6116 is
  type ram_type is array (0 to 2**8) of
    std_logic_vector(7 downto 0);
  signal raml: ram_type;
begin
  process (address, CS_b, WE_b, OE_b) is
  begin
    data <= (others => 'Z');  -- chip is not selected
    if (CS_b = '0') then
      if WE_b = '0' then -- write
        raml(conv_integer(address)) <= data;
      end if;
      if WE_b = '1' and OE_b = '0' then -- read
        data <= raml(conv_integer(address));
      else
        data <= (others => 'Z');
      end if;
    end if;
  end process;
end simple_ram;
```



# *Timing Model for SRAM I*

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
entity ram6116 is
  generic (constant t_AA: Time := 120 ns;
    constant t_ACS: Time := 120 ns;
    constant t_CLZ: Time := 10 ns;
    constant t_CHZ: Time := 10 ns;
    constant t_OH: Time := 10 ns;
    constant t_WC: Time := 120 ns;
    constant t_AW: Time := 105 ns;
    constant t_WP: Time := 70 ns;
    constant t_WHZ: Time := 35 ns;
    constant t_DW: Time := 35 ns;
    constant t_DH: Time := 0 ns;
    constant t_OW: Time := 10 ns);

  port(address: in unsigned(7 downto 0);
    data: inout std_logic_vector(7 downto 0);
    WE_b, CS_b, OE_b: in std_ulogic);
end entity ram6116;
```

# Timing Model for SRAM II

```
architecture SRAM of ram6116 is
  type ram_type is array(0 to 2**8) of std_logic_vector(7 downto 0);
  signal ram1: ram_type := (others => (others => '0'));
begin
  ram: process
  begin
    if (rising_edge(WE_b) and CS_b'delayed = '0')
      or (rising_edge(CS_b) and WE_b'delayed = '0') then
      -- write
      ram1(conv_integer(address'delayed)) <= data'delayed;
      -- data'delayed is the value of data just before the falling_edge
      data <= transport data'delayed after t_OW;
    end if;
    if (falling_edge(WE_b) and CS_b = '0') then
      -- enter write mode
      data <= transport "ZZZZZZZZ" after t_WHZ;
    end if;
```

# Timing Model for SRAM III

```
architecture SRAM of ram6116 is
    ...
begin
    ram: process
    begin
        ...
        if CS_b'event and OE_b = '0' then
            if CS_b = '1' then    -- RAM is de-selected
                data <= transport "ZZZZZZZZ" after t_CHZ;
            elsif WE_b = '1' then -- read
                data <= "XXXXXXXX" after t_CLZ;
                data <= transport ram1((conv_integer(address))) after t_ACS;
            end if;
        end if;
        if address'event and CS_b = '0' and OE_b = '0' and WE_b = '1'
        then
            data <= "XXXXXXXX" after t_OH;
            data <= transport ram1(conv_integer(address)) after t_AA;
        end if;
        wait on CS_b, WE_b, address;
    end process RAM;
    ...
end
```

# *Timing Model for SRAM IV*

```
architecture SRAM of ram6116 is
    ...
begin
    ...
    check: process
    begin
        if CS_b'delayed = '0' and NOW /= 0 ns then
            if address'event then
                assert (address'delayed'stable(t_WC)) -- t_RC = t_WC
                report "address cycle is too short"
                severity WARNING;
            end if;
        ...
    end process
end;
```

# *Timing Model for SRAM V*

```
architecture SRAM of ram6116 is
    ...
begin
    ...
    check: process
    begin
        if CS_b'delayed = '0' and NOW /= 0 ns then
            ...
            if rising_edge(WE_b) then
                assert (address'delayed'stable(t_AW))
                report "address not long enough to end of write"
                severity WARNING;
                assert (WE_b'delayed'stable(t_WP))
                report "write pulse is too short" severity WARNING;
                assert (data'delayed'stable(t_DW))
                report "data setup time is too short" severity WARNING;
                wait for t_DH;
                assert (data'last_event >= t_DH)
                report "data hold time is too short" severity WARNING;
            end if;
        end if;
        wait on WE_b, address, CS_b;
    end process check;
end architecture sram;
```

# *Dynamic RAM*

```
library ieee;
use ieee.std_logic_1164.all;
entity dram1024 is
    port(address: in integer range 0 to 2**5-1;
          data: inout std_ulogic_vector(7 downto 0);
          RAS, CAS, WE: in std_ulogic);
end entity;
```

# *Dynamic RAM*

```
architecture beh of dram1024 is
begin
  p0: process(RAS, CAS, WE) is
    type dram_array is array (0 to 2**10-1) of
      std_ulogic_vector (7 downto 0);
    variable row_address: integer range 0 to 2**5-1;
    variable mem_address: integer range 0 to 2**10-1;
    variable mem: dram_array;
  begin
    ...
  end process p0;
end architecture;
```

# *Dynamic RAM*

```
architecture beh of dram1024 is
begin
  p0: process(RAS, CAS, WE) is
  begin
    data <= (others => 'Z');
    if falling_edge(RAS) then row_address := address;
    elsif falling_edge(CAS) then
      mem_address := row_address*2**5 + address;
      if RAS = '0' and WE = '0' then
        mem(mem_address) := data;
      end if;
      if CAS = '0' and RAS = '0' and WE = '1' then
        data <= mem(mem_address);
      end if;
    end process p0;
end architecture;
```