

VHDL
Modeling Behavior
from Synthesis Perspective
- Part A -

EL 310
Erkay Savaş
Sabancı University

Motivation

- Synthesis of VHDL models with process construct.
- Processes provide powerful modeling abstraction for simulation purposes.
 - modeling complex digital system behavior that cannot be captured with only CSA statements.
- Increasing the level of modeling abstraction makes hardware inference process harder.
 - More than one hardware implementation is possible
 - Inference process has more work to do. Relationship between the language constructs and the real systems is no longer explicit.
 - Simple coding guidelines in order to ease the synthesis compiler's task.

Synthesis with Processes

- Process construct models have similarities to high-level programming languages
 - sequential style of high-level programming languages may lead to excessive logic and often long signal paths.
- Good rule of thumb:
 - Avoid long processes
 - promote concurrency within models through the use of multiple processes and CSA statements.
 - After all, processes are concurrent to other processes and to CSA statements.

Recall

- Combinational logic
 - The value of an output signal is defined for every combination of values of input signals
 - "Previous" values do not have to be remembered.
 - Make sure that every time a process is executed, each output should be assigned a value.
- Sequential logic
 - The values of an output signal may depend on "previous" values stored in the circuit
 - `if-then-else` constructs leads to a latch element if `else` branch does not assign a value to one of the output signals
 - Next issue: will edge-sensitive flip-flop or latch be inferred?
 - `wait until (falling_edge(clk));`

One Old Example

```
library IEEE;
use IEEE.std_logic_1164.all;


entity sig_var is
port(x,y,z: in std_logic;
      res1, res2: out std_logic);
end entity sig_var;

architecture behavioral of sig_var is
  signal sig_s1, sig_s2: std_logic;
begin


  proc1:process(x,y,z) is -- process 1 using variables
    variable var_s1, var_s2:std_logic;
  begin
    var_s1 := x and y;
    var_s2 := var_s1 xor z;
    res1 <= var_s1 nand var_s2;
  end process;

  proc2:process(x,y,z) is -- process 1 using signals
  begin
    sig_s1 := x and y;
    sig_s2 := sig_s1 xor z;
    res1 <= sig_s1 nand sig_s2;
  end process;
end architecture behavioral;
```

Simulation Results

 


Example: The Synthesized Logic

 

- Two processes result in identical logic for `res1` and `res2`.
- Both circuit are combinational
- combinational logic is a natural result of using "variables" that are assigned immediately with values evaluated at the RHS of assignment statements.

Synplify Pro RTL View

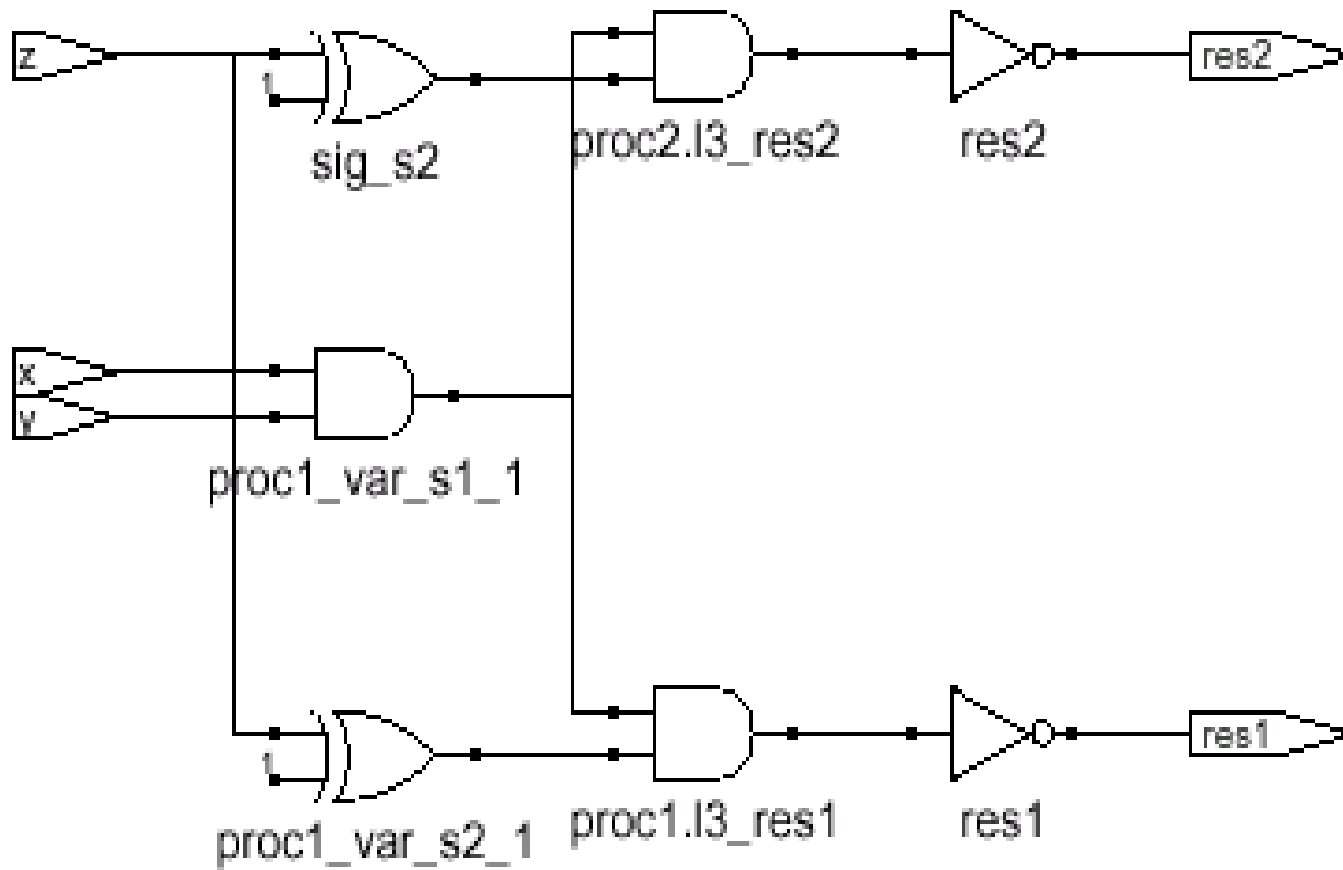

$$res1 = res2 = z + (xy)'$$

Example: The Synthesized Logic

- Recall that
 - the values of sig_s1 and sig_s2 used when the process proc2 is executed are the ones when the process is invoked,
 - Not the values are newly evaluated within the procedure
 - This would cause inference of storage elements.
- However, compilers generally optimize this sequence to produce combinational logic.
 - Thus, signals and variables behave identically with respect to the synthesis in this case.
 - Dependency in the sequential execution of signals will increase the critical path.

Sensitivity List Mismatch

- The signal `sig_s1` is not in the sensitivity list.
 - Therefore, an event on it (caused by another process perhaps) will not lead to the execution of process `proc2`.
 - However, an event on `sig_s1` will cause the re-computation of the output values in the synthesized circuit.
- Simulation semantics may not match the behavior of the synthesized circuit.

Data Dependency

- Independent of whether variables and signals are used, process statements introduce a data dependency between the process statements
- s1 <= ...
s2 <= ... s1 ...
s3 <= ... s2 ...
s4 <= ... s2 ...
and so on.
- Result: long chain of dependency to calculate s4.
- Consequence: a long signal path in the synthesized logic.

Synthesis of Conditional Statements


- If-Then-Else and If-Then-Elsif statements
 - All Boolean valued expressions are evaluated sequentially until the first true expression is encountered.

```
library IEEE;
use IEEE.std_logic_1164.all;

entity inf_latch is
port(sel,x,y,z: in std_logic;
      w: out std_logic);
end entity inf_latch;

architecture behavioral of inf_latch is
    variable s1, s2:std_logic;
begin
    process(x,y,z,sel) is
    begin
        if (sel = '1') then
            s1 := x and z;
            s2 := s1 xor y;
            w <= s1 and s2;
        end if;
        -- w gets a value only conditionally
        -- hence a latch is inferred.
    end process;
```

Example: Latch Inference

 

- If `sel = '1'` the new value of the signal `w` is computed as shown in the code.
- Otherwise it will keep its previous value stored in the latch.
- Rule: to avoid unnecessary latched inferences, the signal values should be assigned a value in every branch of conditional statements (both in `then` and `else` statements).
- remember that we have to make sure that all output signals get a value in every execution of process.

Alternative to Avoid Latches


- Assign a default value to the signal prior to the `if` statement

```
library IEEE;
use IEEE.std_logic_1164.all;

entity inf_latch is
port(sel,x,y,z: in std_logic;
      w: out std_logic);
end entity inf_latch;

architecture behavioral of inf_latch is
variable s1, s2:std_logic;
begin
process(x,y,z,sel) is
begin
    w <= '0'; -- output signal set to a default value to avoid latch
    if (sel = '1') then
        s1 := x and z; -- body generates combinational logic
        s2 := s1 xor y;
        w <= s1 and s2;
    end if;
end process;
```

Avoid Latches by Default Value

 

Efficiency


- Avoiding unnecessary latches is one aspect of effective design for combinational circuit synthesis
- Efficiency in terms of speed and/or size is the other.

```
library IEEE;
use IEEE.std_logic_1164.all;

entity inference is
port(sel,x,y,z: in std_logic;
      w: out std_logic);
end entity inference;

architecture behavioral of inference is
variable s1, s2:std_logic;
begin
process(x,y,z,sel) is
begin
  if (sel = '1') then
    w <= x and y;
  else
    w <= x and z;
  end if;
end process;
end architecture;
```


Example: Efficiency

 

- The general principle:
- combinational logic is generated for each branch of an if-then-else construct.
- A multiplexor is generated to select the outcome

More Efficient Design - 1


- a small rearrangement will simplify the design

```
library IEEE;
use IEEE.std_logic_1164.all;

entity inference is
port(sel,x,y,z: in std_logic;
      w: out std_logic);
end entity inference;

architecture behavioral of inference is
begin
process(x,y,z,sel) is
    variable right: std_logic;
begin
    if (sel = '1') then
        right := y;
    else
        right := z;
    end if;
    w <= x and right;
end process;
end architecture;
```

More Efficient Design - 2

 

- Coding styles help us to control how much hardware is generated.
- Golden rule: move complex or hardware intensive operations that are replicated in then and else branches out of the if-then-else statement.

Multiple Levels of Nesting


```
library IEEE;
use IEEE.std_logic_1164.all;

entity nested is
port(sel1, sel2, sel3, x,y,z: in std_logic;
     res: out std_logic);
end entity nested;

architecture behavioral of nested is
begin
process(x, y, z, sel1, sel2, sel3) is
begin
    if (sel1 = '1') then
        res <= x and y;
    elsif(sel2 = '1') then
        res <= y xor z;
    elsif(sel3 = '1') then
        res <= x or y;
    end if;
end process;
end architecture;
```

Question: Is latch inferred?

Example: Multiple Levels of Nesting

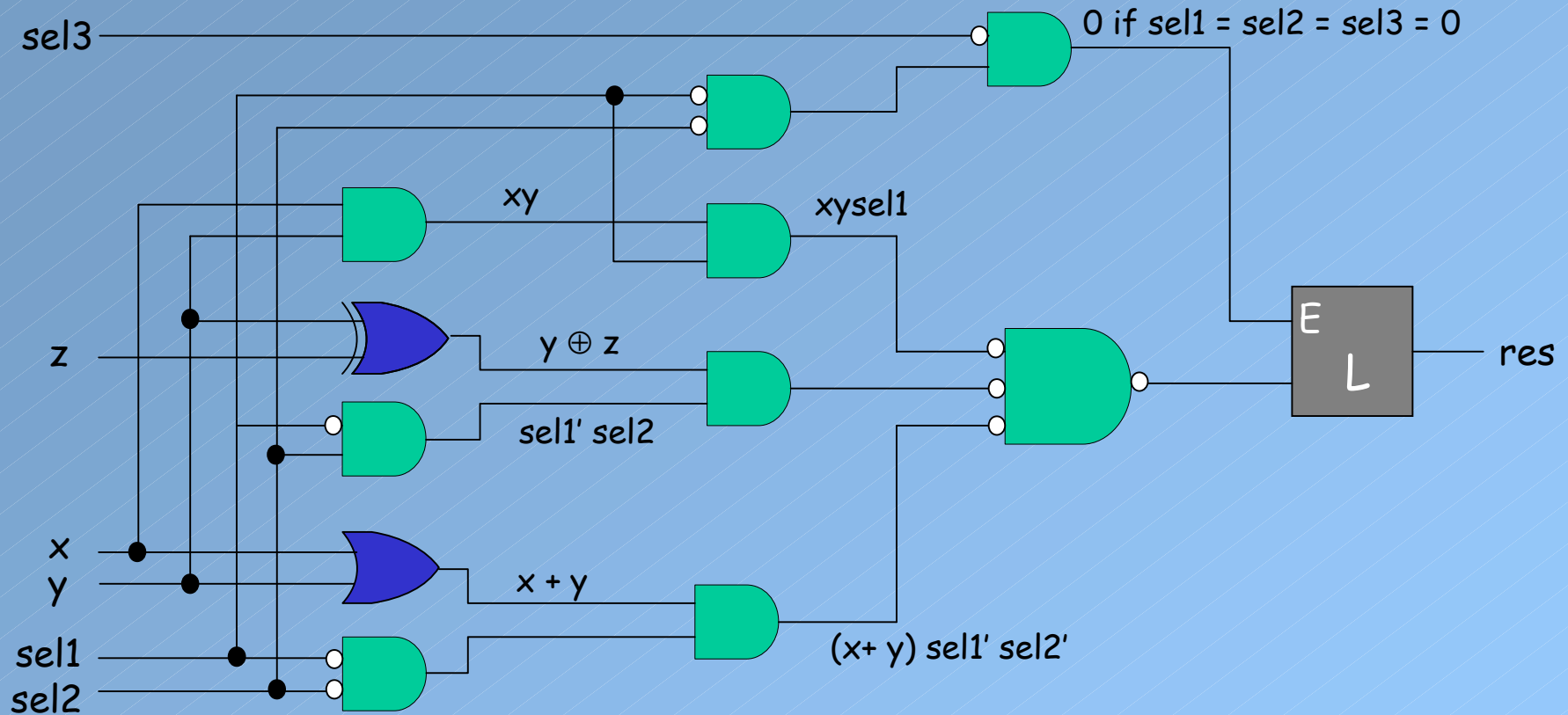


- Priority logic is implemented.
- What is the highest priority?

Nested If Statements

```
library IEEE;
use IEEE.std_logic_1164.all;
entity nested_ifs is
port(sel0, sel1, x,y,z: in std_logic;
      res: out std_logic);
end entity nested_ifs;
architecture behavioral of nested_ifs is
begin
process(x, y, z, sel0, sel1) is
begin
    if (sel0 = '0') then
        if (sel1 = '1') then
            res <= x and y;
        else
            res <= '0';
        end if;
    end if;
end process;
end architecture;
```

-- included to avoid latch inference

Nested If Statements

 


- Latch is inferred because of the outer if-then-else statement

Nested If Statements

```
library IEEE;
use IEEE.std_logic_1164.all;
entity nested_ifs is
port(sel0, sel1, x,y,z: in std_logic;
res: out std_logic);
end entity nested_ifs;
architecture behavioral of nested_ifs is
begin
process(x, y, z, sel0, sel1) is
begin
    if (sel0 = '0') then
        if (sel1 = '1') then
            res <= x and y;
        end if;
    end if;
end process;
end architecture;
```


Nested If Statements

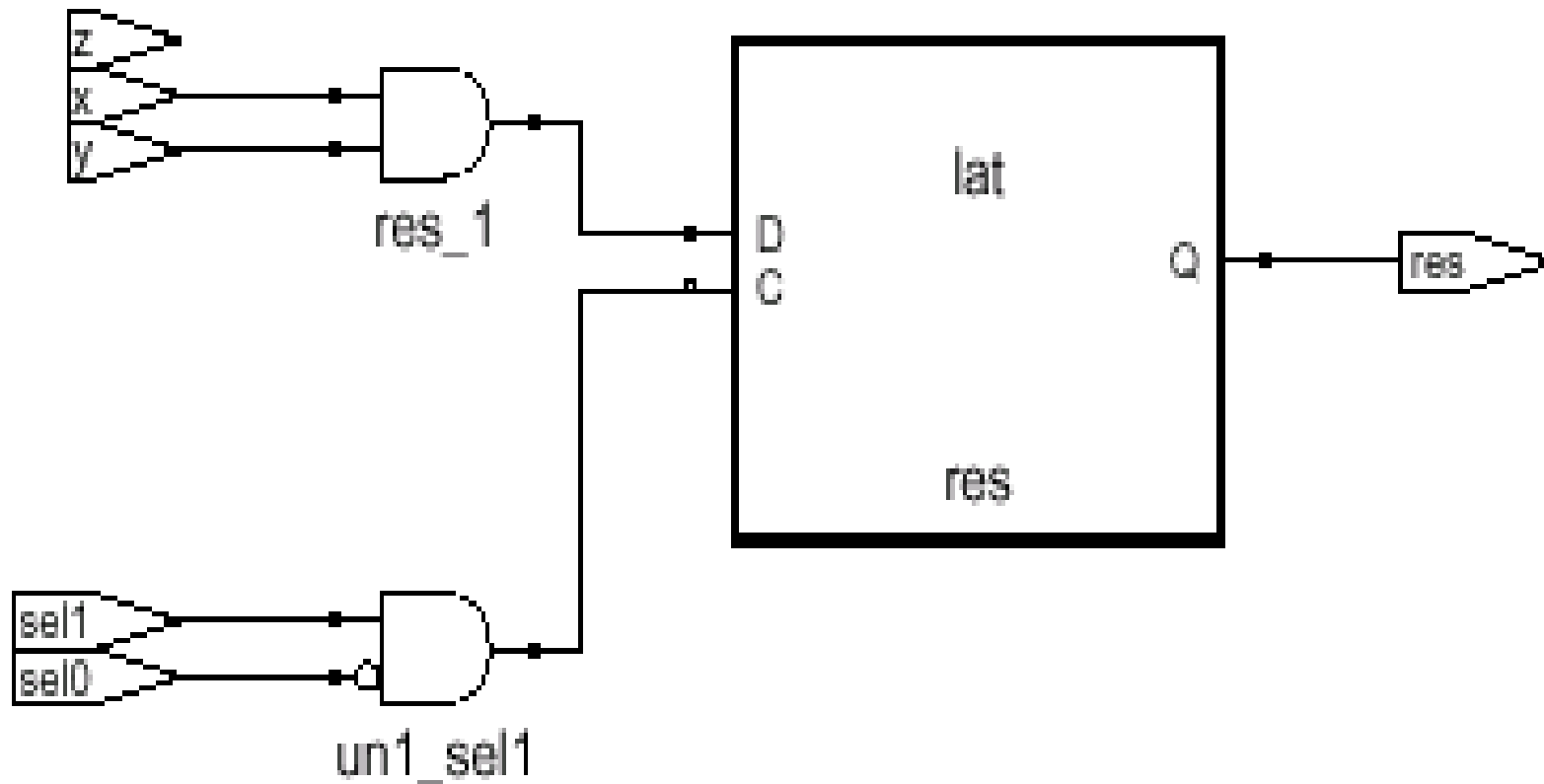

Remove the inner if-then-else from the outer one
in order to infer combinational logic

Don't Cares in Conditional Expressions

```
library IEEE;
use IEEE.std_logic_1164.all;


entity sig_var is
port(sel: in std_logic_vector(1 downto 0);
      x,y,z: in std_logic;
      w: out std_logic);
end entity sig_var;

architecture behavioral of sig_var is
begin
process(x, y, z) is
begin
    if (sel = '-0') then
        w <= x xnor y;
    else
        w <= x xnor z;
    end if;
end process;
end architecture;
```

comparisons with don't cares in conditional expressions return always FALSE.

Don't Cares in Conditional Expressions

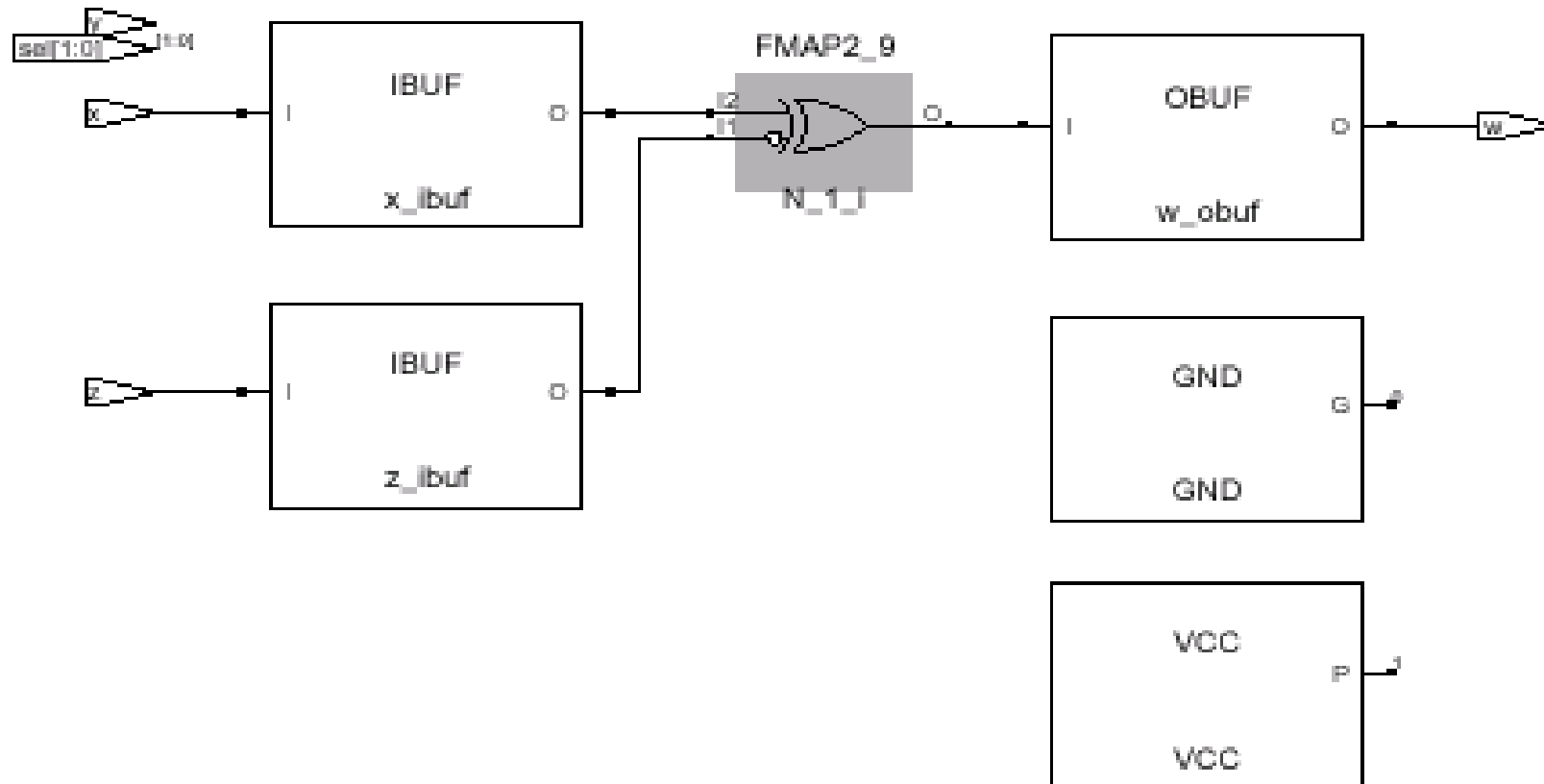Synthesis compiler generates a logic in which then branch is never taken



Case Statement

- Case statement is similar to `if-then-else` constructs
 - but identifies mutually exclusive blocks of code.
 - Only one branch of a case statement can be true
 - and collectively all branches cover all possible values of select expression.
 - The `others` clause helps cover all possible values of select expression
 - Selecting one of the several possible alternatives suggests that a multiplexor is inferred.
 - Select expression provides the control signals for multiplexor.

Case Statement: Example


```
library IEEE;
use IEEE.std_logic_1164.all;

entity case_ex is
port(sel: in integer range 0 to 3;
      x,y,z: in std_logic;
      res: out std_logic);
end entity case_ex;

architecture behavioral of case_ex is
begin
  process(x, y, z, sel) is
  begin
    case sel is
      when 0 => res <= x and y;
      when 1 => res <= y xor z;
      when 2 => res <= x nand z;
      when others => res <= x nor z;
    end case;
  end process;
end architecture;
```

A combinational logic is inferred when output signals receive a value in all branches of the case

Case Statement: Example

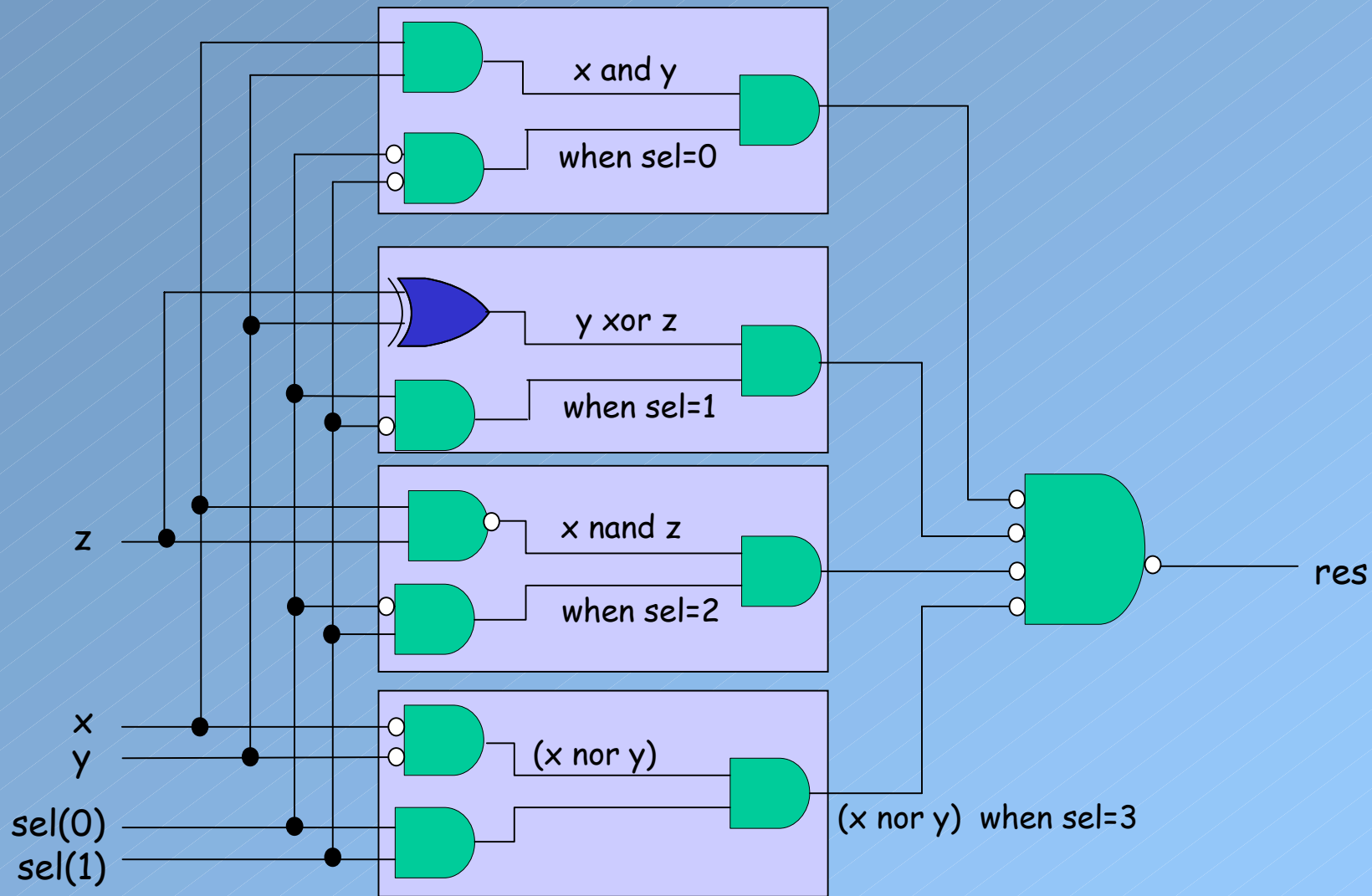

`sel: in integer range 0 to 3;` is mapped to a two-bit signal


Latch Inference from Case Statement

```
library IEEE;
use IEEE.std_logic_1164.all;

entity case_ex is
port(sel: in integer range 0 to 3;
      x,y,z: in std_logic;
      res: out std_logic);
end entity case_ex;

architecture behavioral of case_ex is
begin
  process(x, y, z, sel) is
  begin
    case sel is
      when 0 => res <= x and y;
      when 1 => res <= y xor z;
      when 2 => res <= x nand z;
      when others => null; -- in this case the value of res
                           -- remains unaltered
    end case;
  end process;
end architecture;
```

Latch Inference from Case Statement

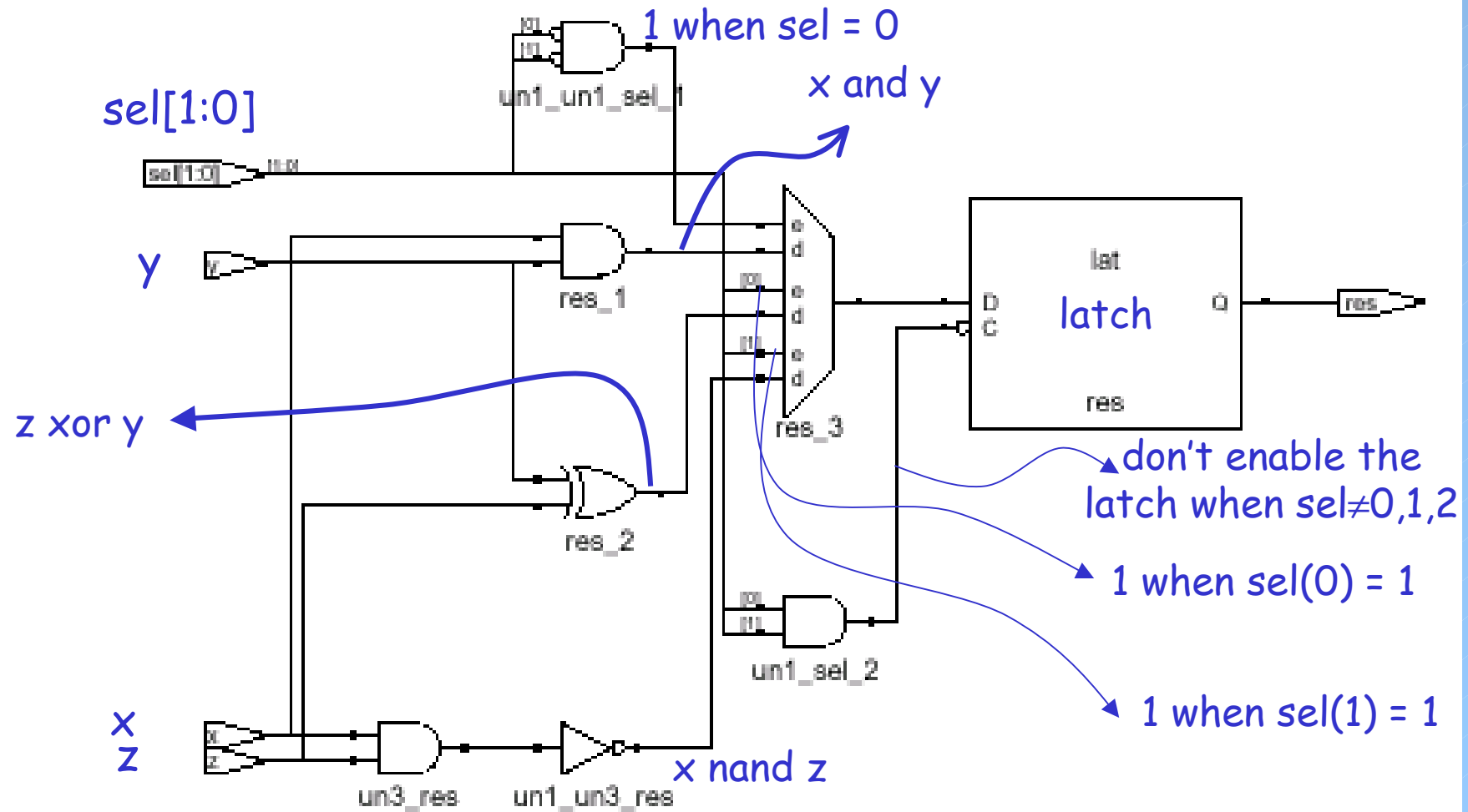

Avoiding Latch Using Default Value

```
entity case_ex is
port(sel: in integer range 0 to 3;
      x,y,z: in std_logic;
      res: out std_logic);
end entity case_ex;

architecture behavioral of case_ex is
begin
process(x, y, z, sel) is
begin
  res <= '0';
  case sel is
    when 0 => res <= x and y;
    when 1 => res <= y xor z;
    when 2 => res <= x nand z;
    when others => null;
  end case;
end process;
end architecture;
```

Any case statement has an equivalent if-then-elsif form.
Question: what is the difference between the two?


Using don't cares in Case Statements

```
entity case_ex is
port(sel: in integer range 0 to 3;
      x,y,z: in std_logic;
      res: out std_logic);
end entity case_ex;

architecture behavioral of case_ex is
begin
process(x, y, z, sel) is
begin
  case sel is
    when 0 => res <= x and y;
    when 1 => res <= y xor z;
    when 2 => res <= x nand z;
    -- when others => res <= '0';
    when others => res <= '-';
  end case;
end process;
end architecture;
```

Use don't cares in when others to let the synthesis tool to optimize the circuit.

Using don't cares in Case Statements

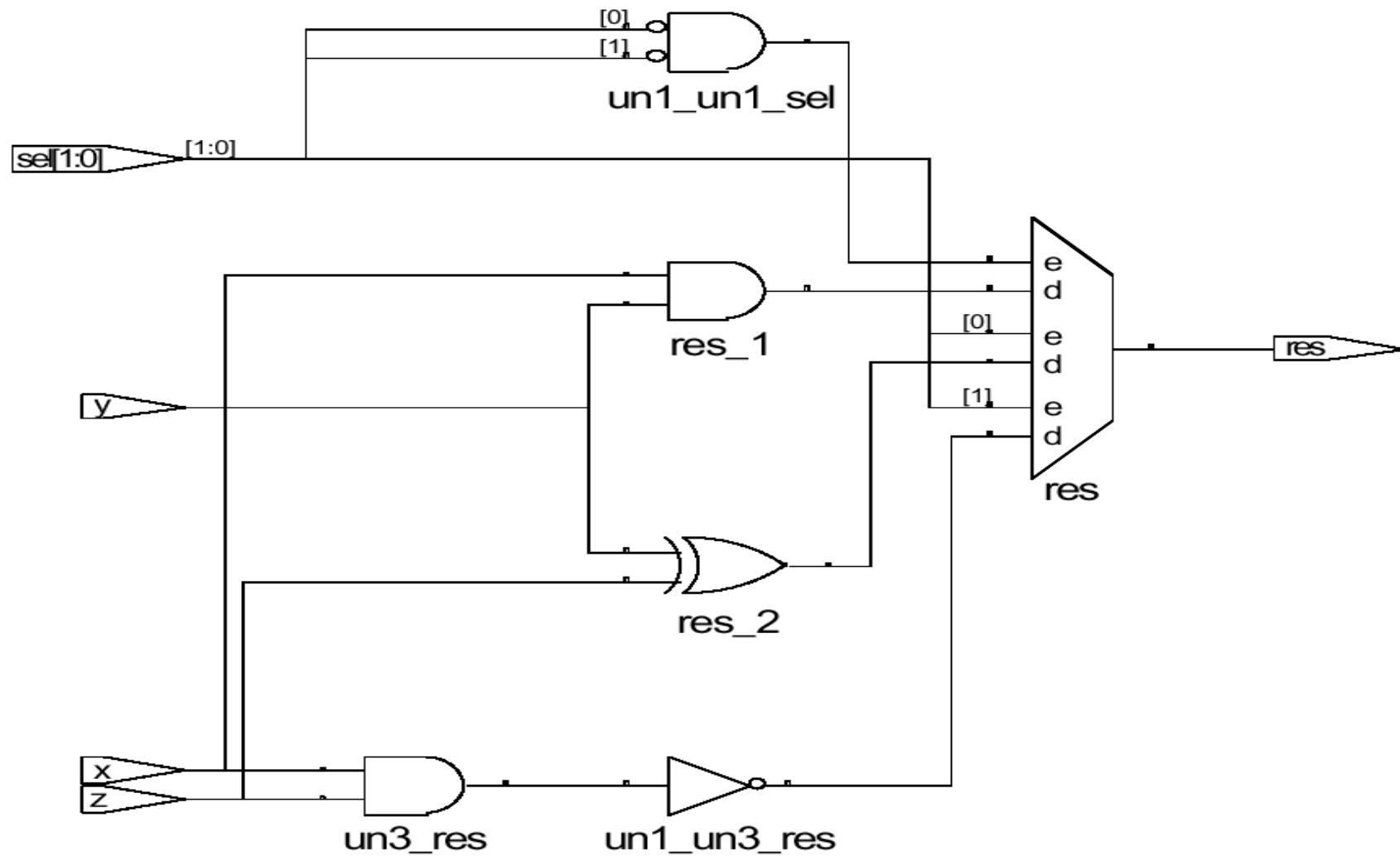

circuit output res is not defined for sel
= 3

Loop Statements

- For-Loop
 - Most common construct for loops supported by synthesis compilers
 - At compile-time, it is possible to know when the loops ends; the logic is inferred accordingly.
 - With while-loops, when the loop ends may be data dependent.
 - Therefore, a state machine controller is synthesized to cycle datapath a data-dependent number of times.
 - For-loops, on the other hand, is easy to synthesize. since the number of iterations is known.

For Loops

- Example:

- **for** N **in** 3 **downto** 1 **loop**
 shift_reg(N) <= shift_reg(N-1);
end loop;
- The loop can easily be replaced by sequential code
shift_reg(3) <= shift_reg(2);
shift_reg(2) <= shift_reg(1);
shift_reg(1) <= shift_reg(0);
- This technique is known as loop unrolling, and it is also being commonly used in conventional languages for optimization purposes.
- In VHDL synthesis, loop unrolling is also used as an optimization technique.

Loop Unrolling: Example


```
library IEEE;
use IEEE.std_logic_1164.all;

entity iteration is
port(clk, reset, data: in std_logic;
      res: out std_logic_vector(3 downto 0));
end entity iteration;

architecture behavioral of iteration is
  signal shift_reg: std_logic_vector(3 downto 0);
begin
  process(clk, reset, data) is
  begin
    if(rising_edge(clk)) then
      if(reset = '1') then res <= "0000";
      else
        for N in 3 downto 1 loop
          shift_reg(N) <= shift_reg(N-1);
        end loop;
        shift_reg(0) <= data;
        res <= shift_reg;
      end if;
    end if;
  end process;
end architecture;
```

Loop Unrolling: Example

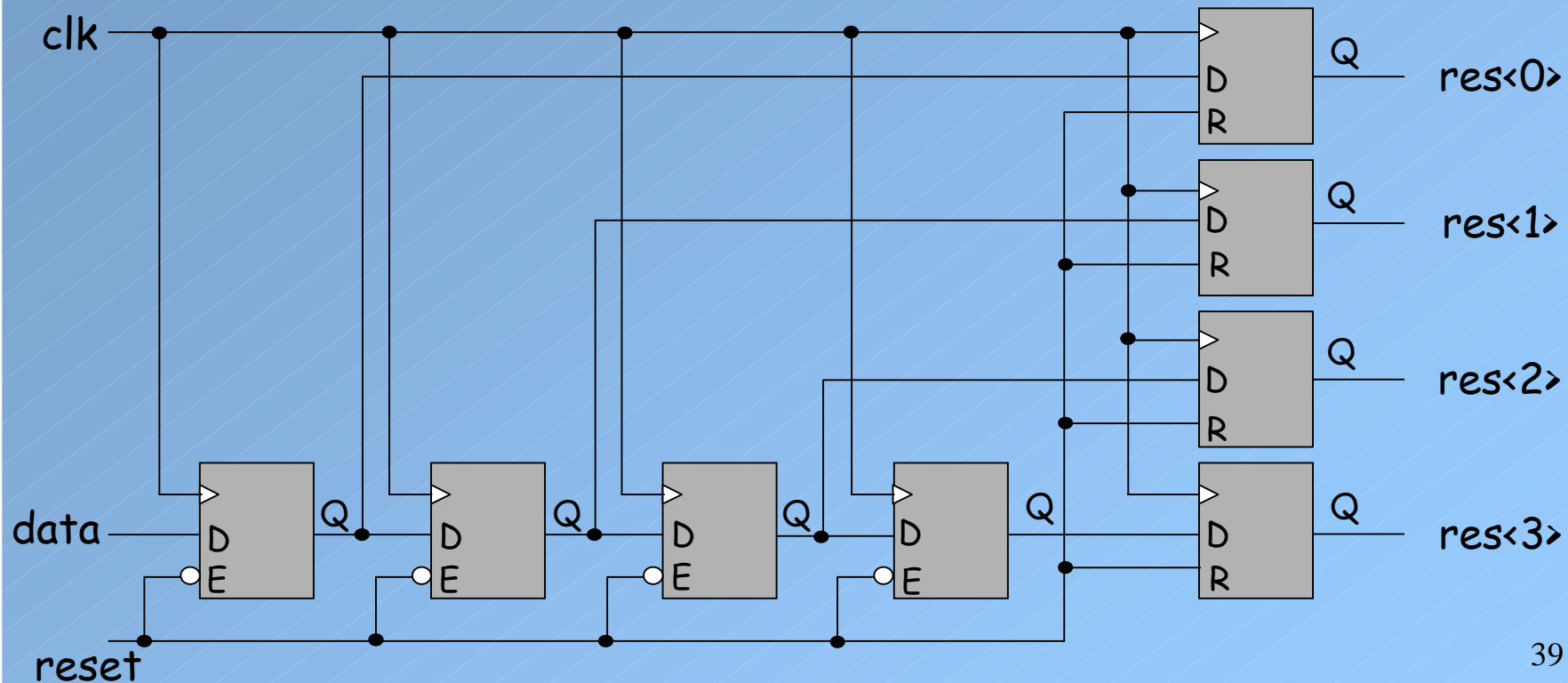- Latch inference
 - Because of `if(rising_edge(clk)) then` with no else, a storage element will be inferred.
 - But due to the call to function `rising_edge()` a flip-flop instead of a latch is inferred.



While Loop

```
entity iteration is
port(clk, reset, data: in std_logic;
      res: out std_logic_vector(3 downto 0))
end entity iteration;
architecture behavioral of iteration is
    signal shift_reg: std_logic_vector(3 downto 0);
begin
    process(clk, reset, data) is
        variable N: integer;
    begin
        if(rising_edge(clk)) then
            if(reset = '1') then res <= "0000";
            else
                N := 3;
                while N > 0 loop
                    shift_reg(N) <= shift_reg(N-1); N := N - 1;
                end loop;
                shift_reg(0) <= data; res <= shift_reg;
            end if;
        end if;
    end process;
end architecture;
```


Exit Statement

```
sum := 1; j := 0;  
L2: loop;  
    j := j+21;  
    sum := sum *10;  
    exit when sum > 100;  
end loop L2;
```

- The `exit` statement can be used only inside a loop.
- It causes execution to jump out of the innermost loop or the loop whose label is specified.
- `exit` [loop-label][**when** condition];

```
sum := 1; j := 0;  
L3: loop;  
    j := j+21;  
    sum := sum *10;  
    if sum > 100 then  
        exit L3;  
    end if;  
end loop L3;
```

Next Statement

- A sequential statement that can be used only inside a loop.
- Syntax: **next** [loop-label][**when** condition];
- It results in skipping the remaining statements in the current iteration of the loop;
- execution resumes with the first statement in the next iteration of this loop, if one exists.

```
for j in 10 downto 5 loop
  if sum < total_sum then
    sum := sum + 2;
  elsif sum = total_sum then
    next;
  else
    null;
  end if;
  k := k + 1;
end loop;
```

Next Statement

- The next statement can also cause an inner loop to be exited.

```
L4: for k in 10 downto 1 loop
  -- statements section 1
  L5: loop
    -- statements section 2
    next L4 when WR_DONE = '1';
    -- statements section 3
  end loop L5;
  -- statements section 4
end loop L4;
```

- When `WR_DONE = '1'` becomes true, statements section 3 and 4 are skipped, and execution jumps to the beginning of the next iteration of loop L4.
- Notice that loop L5 is terminated by `next` statement.

Loops

- Some synthesis compilers forces the type of the loop index to integers or only a subsets of array types.
- The dependencies across iterations of a loop will lead to long signal paths.
- Example:

```
- reg(0) <= datain(0);  
  for N in 1 to 3 loop  
    reg(N) <= reg(N-1) xor datain(N);  
  end loop;
```


- When you unroll

```
reg(0) <= datain(0);  
reg(1) <= reg(0) xor datain(1);  
reg(2) <= reg(1) xor datain(2);  
reg(3) <= reg(2) xor datain(3);
```

Loops: Example

```
library IEEE;
use IEEE.std_logic_1164.all;
entity iteration is
port(data: in std_logic_vector(3 downto 0);
      res: out std_logic_vector(3 downto 0));
end entity iteration;
architecture behavioral of iteration is
    signal reg: std_logic_vector(3 downto 0);
begin
    for1: process(data) is
    begin
        reg(0) <= data(0);
        for N in 1 to 3 loop
            reg(N) <= reg(N-1) xor data(N);
        end loop;
        res <= reg;
    end process;
end architecture;
```

Loops: Example

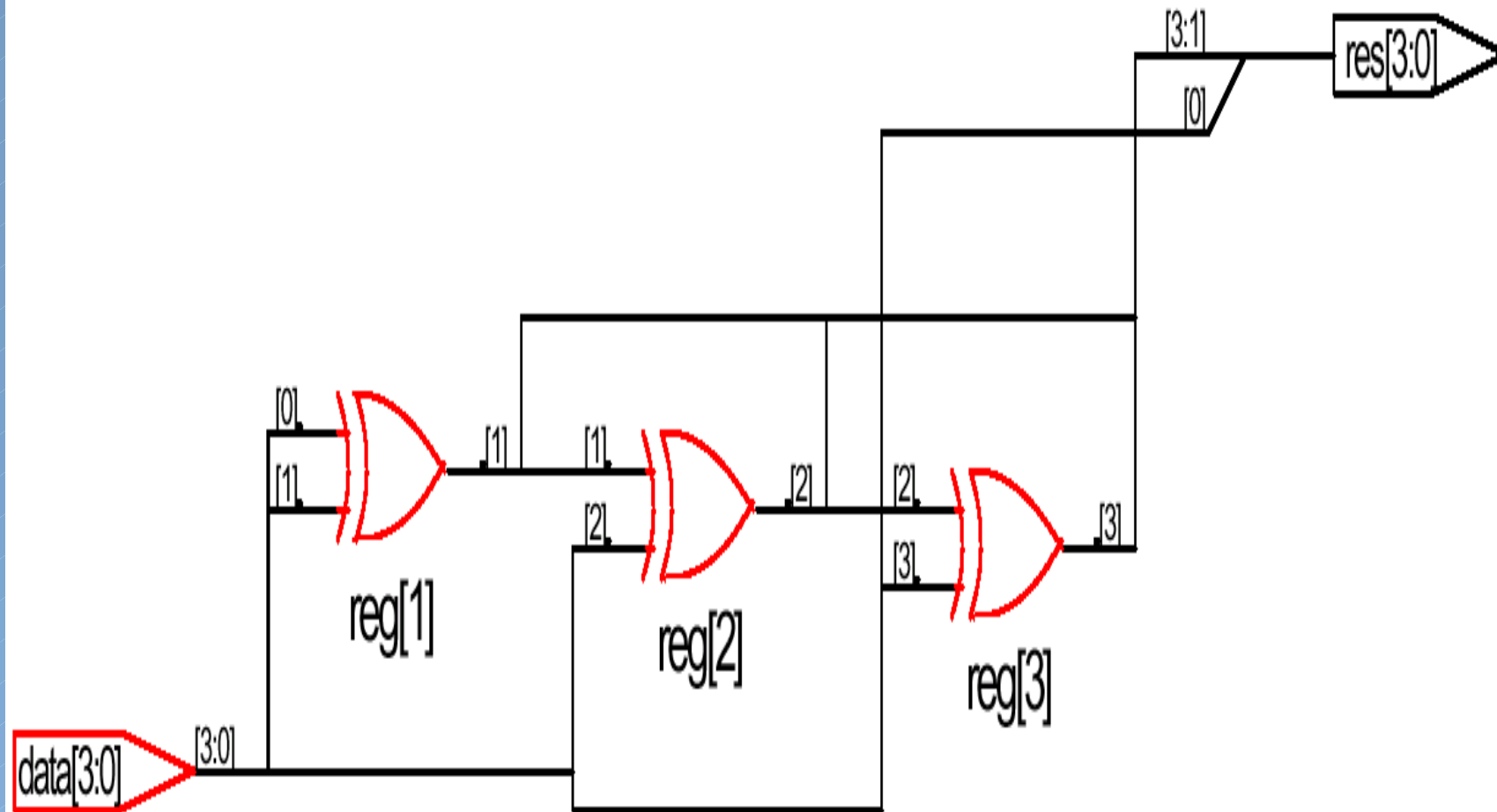

Sensitivity List in Synthesis

- Process is executed when there is an event on any signal in the sensitivity list.
 - When a signal is not in the sensitivity list, an event on this signal does not cause the execution of the process.
 - However, when the VHDL code is synthesized into a logic circuit, a change on any signal will lead to the re-calculation of the other signals that depends on this signal.
 - Therefore, simulation results after synthesis may not match exactly to those before the synthesis.
 - Lesson: Include all signals of process in the sensitivity list when performing simulations.

Variables

- Variables are language objects that is useful in describing the behavior of the circuit.
 - They are typically used to transfer values between statements in a process
 - Compiler may collapse variable assignment statements and eliminate some of them.
 - When it is not possible to do so, then a variable is synthesized to a wire connecting gates.

Inferring Latches

```
...  
L1: if(s1 = '1') then  
...  
L2: if(s2 = '1') then  
      Aout <= '1';  
    else  
      Aout <= '0';  
    end if;  
end if;  
...
```

- Question: Is a latch for Aout inferred?

Buffer and Inout Entity Modes

- A signal can serve as both a driver and as an output signal
 - `Aout <= in1 and in2;`
 `Bout <= Aout xor in3;`
- In this case, Aout signal must be defined as either buffer or inout;
- It is important for hierarchical models
- For the time being, try to avoid situations like this, using the following:
 - `VarAout := in1 and in2;`
 `Bout <= VarAout xor in3;`
 `Aout <= VarAout;`


Inference Using Signals vs. Variables

```
library IEEE;
use IEEE.std_logic_1164.all;
entity sigvar is
port(sel: in std_logic; x, y, z: in std_logic; v: out std_logic);
end entity sigvar;
architecture behavioral of sigvar is
signal sig_s1: std_logic;
begin
process(x, y, z, sel) is
variable var_s1: std_logic;
begin
    L1: if(sel = '1') then
        sig_s1 <= x and z;
        v <= sig_s1 xor y;
    end if;


    L2: if(sel = '0') then
        var_s1 := x and z;
        v <= var_s1 xor y;
    end if;
end process;
end architecture;
```

Question: Find the latches that will be inferred?

Inference Using Signals vs. Variables

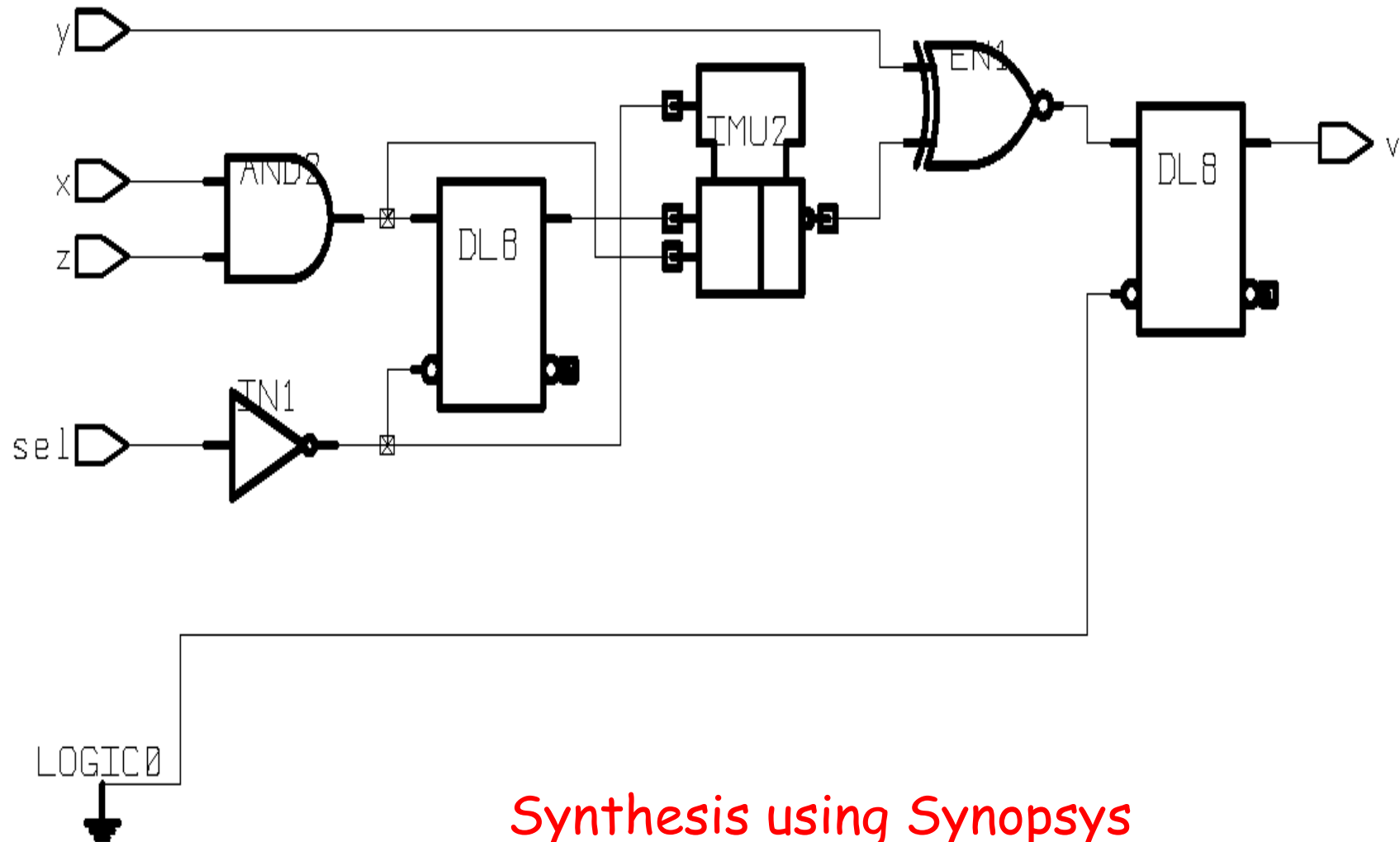

Inference Using Signals vs. Variables

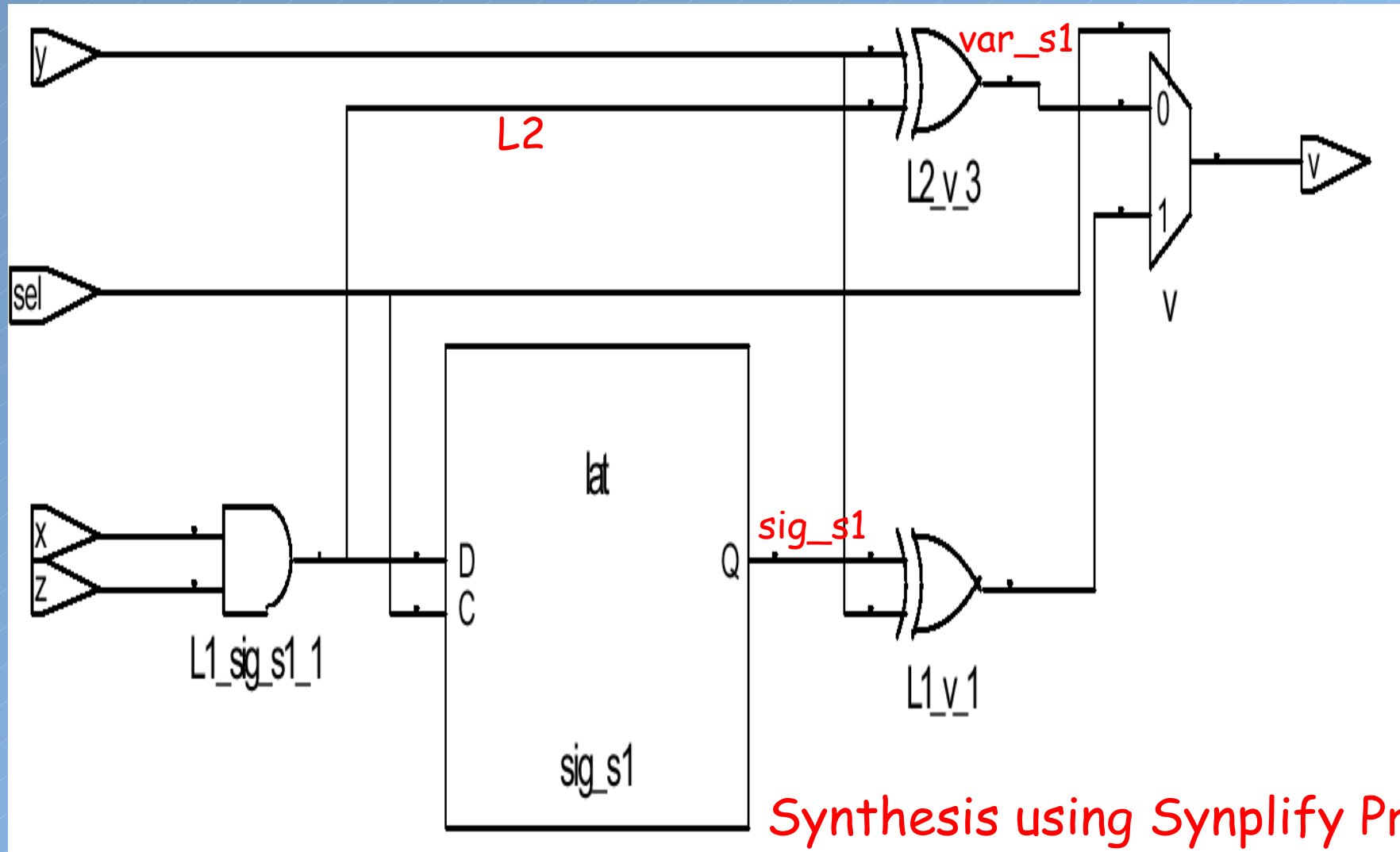

Synthesis using Synplify Pro

Latch Inference for Variables


```
library IEEE;
use IEEE.std_logic_1164.all;
entity sigvar is
port(clk, x, y: in std_logic;
      res: out std_logic);
end entity sigvar;
architecture behavioral of sigvar is
begin
process
    variable var_s1, var_s2: std_logic;
begin
    wait until(rising_edge(clk));
    var_s1 := x nand var_s2;
    var_s2 := var_s1 xor y;
    res <= var_s1 xor var_s2;
end process;
end architecture;
```

Question: Find the latches that will be inferred

Latch Inference for Variables

- Signal `res`:
 - `wait until(rising_edge(clk));` statement causes a flip-flop.
 - When there is no `rising_edge` of the clock, the signal `res` should retain its value.
- Variable `var_s2`:
 - variable `var_s2` is used before it is defined.
 - Variables retain their values across process invocations.
 - Therefore, a flip-flop is inferred when a variable is used before it is defined.

Latch Inference for Variables

 


Latch and Flip-Flop Inference

- `if`, `case`, `wait`, conditional and selected signal assignment statements can be used to infer latches.
 - For example, "`if (sel = '1') then`" will lead to the inference of a latch.
- `if(rising_edge(clk)) then` is used to infer an edge-triggered flip-flop.
 - `if(clk'event and clk = '1')` then may not detect a transition from '0' to '1'.
 - The attribute `clk'last_value` may be useful in detecting 0-to-1 transition.
 - However, it cannot be used in synthesis.
 - Use functions `rising_edge()` or `falling_edge()`.
 - The Xilinx XC4000 series FPGAs support both edge-triggered and level-sensitive devices.

Flip-Flops with Asynchronous Reset

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
entity counter_async is
port(clk, reset: in std_logic; res: out unsigned(3 downto 0));
end entity counter_async;
architecture behavioral of counter_async is
begin
process(clk, reset) is
    variable var_count: unsigned(3 downto 0);
begin
    if(reset='1') then res <= "0000";
    else
        if (rising_edge(clk)) then
            var_count := var_count + 1;
            res <= var_count;
        end if;
    end if;
end process;
end architecture;
```

Flip-Flops with Asynchronous Resets

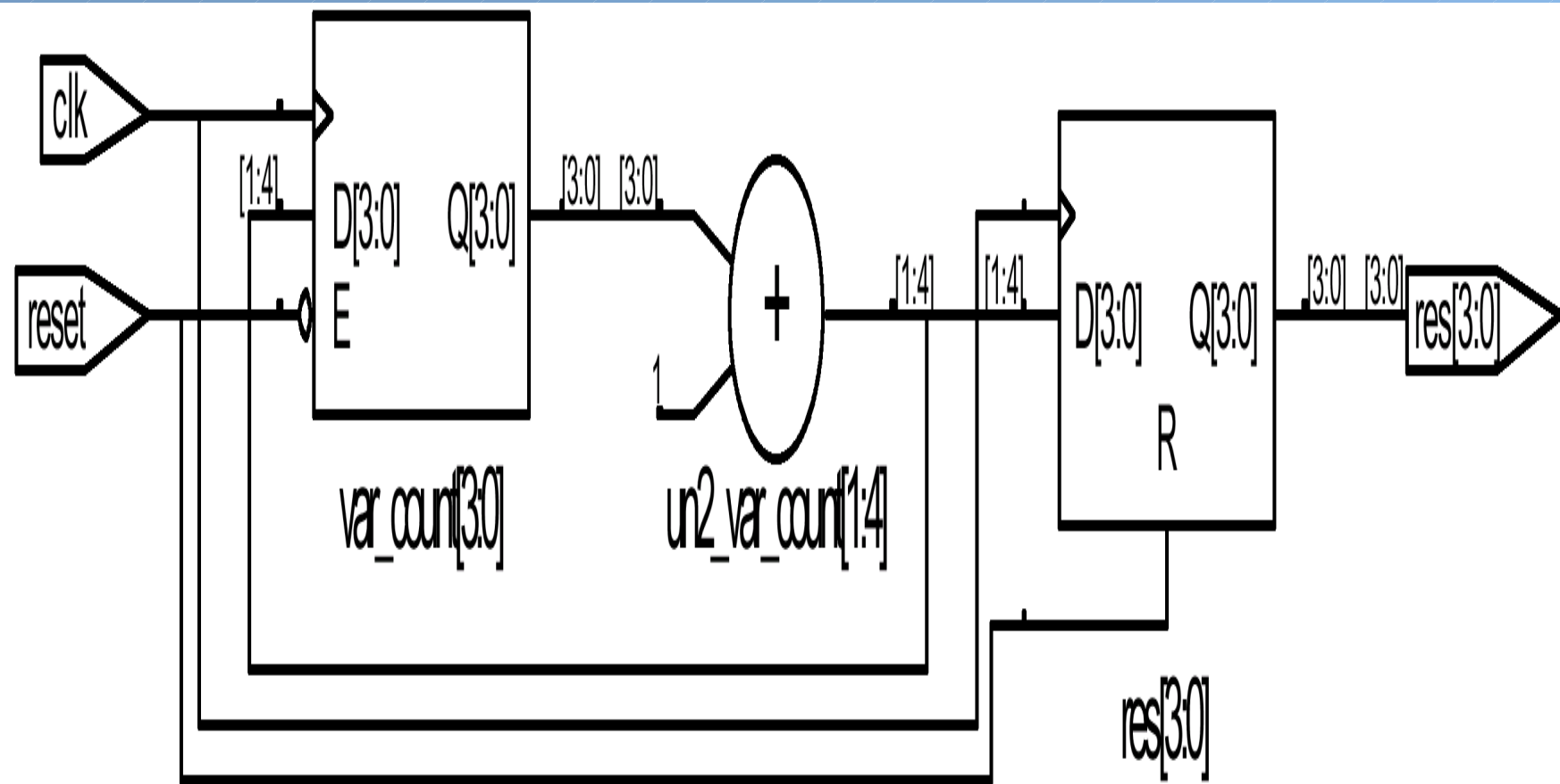


Asynchronous clear and set signal can be synthesized only if they exist in the target library.

Flip-Flops with Synchronous Resets

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
entity counter_async is
port(clk, reset: in std_logic; res: out unsigned(3 downto 0));
end entity counter_async;
architecture behavioral of counter_async is
begin
process(clk, reset) is
    variable var_count: unsigned(3 downto 0);
begin
    if (rising_edge(clk)) then
        if(reset='1') then
            res <= "0000";
        else
            var_count := var_count + 1;
            res <= var_count;
        end if;
    end if;
end process;
end architecture;
```


Flip-Flops with Synchronous Resets

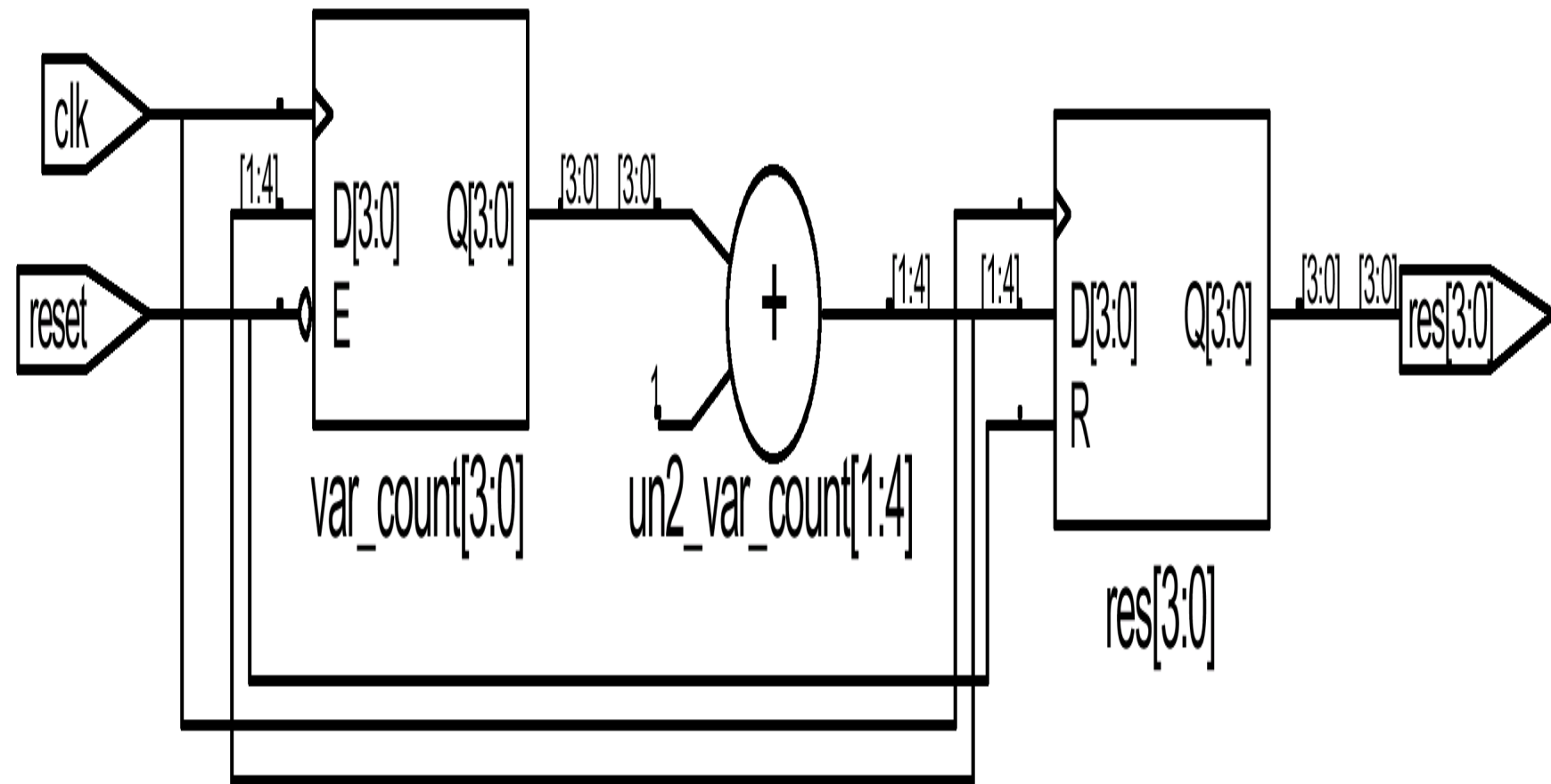

Example in the Textbook

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
entity counter_async is
port(clk, reset: in std_logic; res: out unsigned(3 downto 0));
end entity counter_async;
architecture behavioral of counter_async is
begin
process(clk, reset) is
variable var_count: unsigned(3 downto 0);
begin
    if (rising_edge(clk)) then
        if(reset='1') then
            res <= "0000";
        else
            var_count := var_count + 1;
        end if;
        res <= var_count;
    end if;
end process;
end architecture;
```

Example in the Textbook

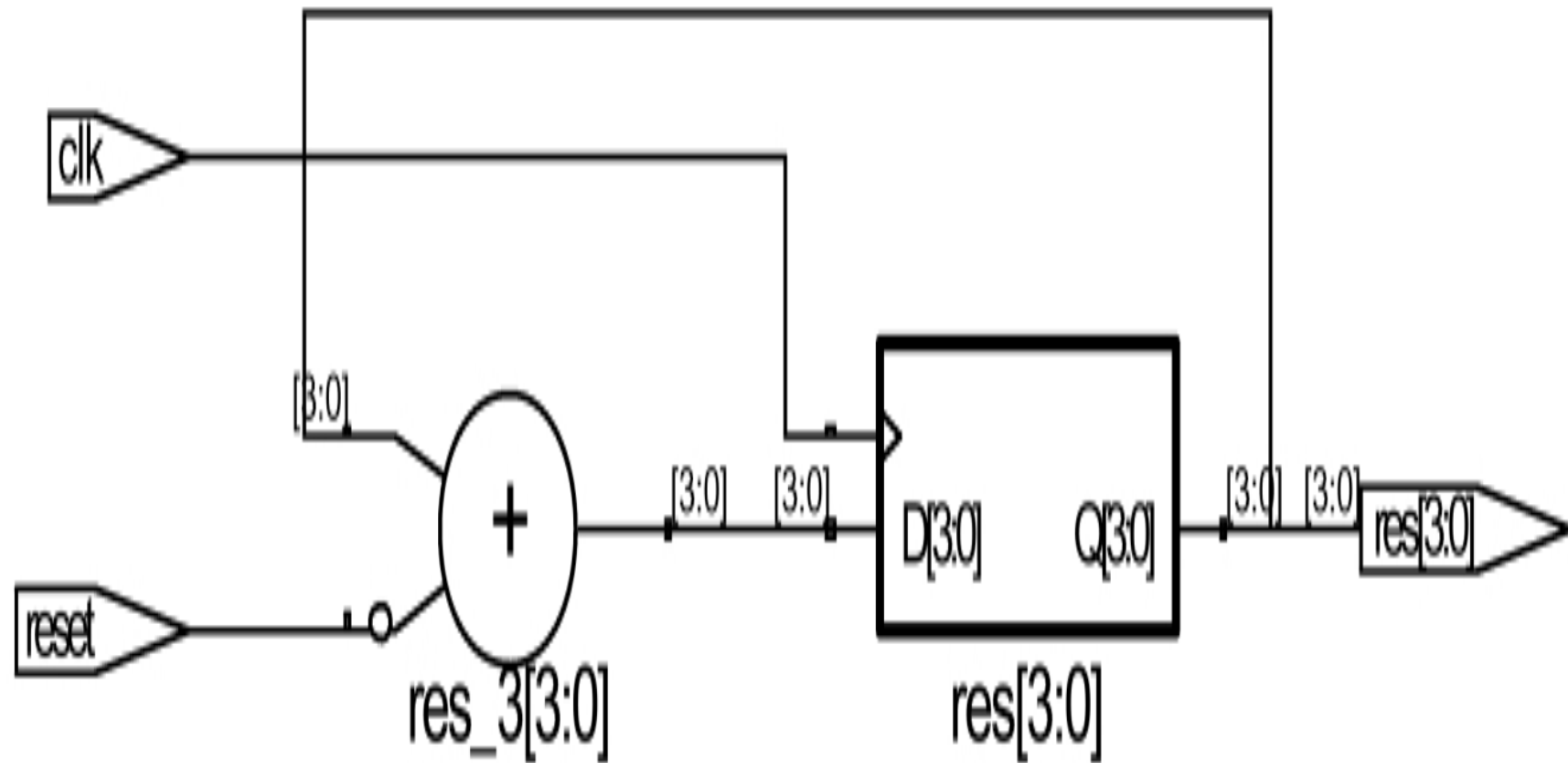

What is the reason for this difference?