

# *VHDL* *MIPS32*

EL 310  
Erkay Savaş  
Sabancı University

# *MIPS32 Architecture*

- 32 bit architecture
  - registers, ALU, instructions, shifter, data and address are 32 bit
- Load/Store architecture
  - There are special instructions to access memory such as `lw` (load word) and `sw` (store word)
  - No ALU operation involves an operand from the memory.
- RISC based
  - simple instructions
  - most of the instruction can be completed in five clock cycles

# *MIPS32 Registers*

Name	Register no	Usage	Preserved on call
\$zero	0	the constant value 0	n.a.
\$v0-\$v1	2-3	values for results and expression evaluation	no
\$a0-\$a3	4-7	arguments	no
\$t0-\$t7	8-15	temporaries	no
\$s0-\$s7	16-23	saved	yes
\$t8-\$t9	24-25	more temporaries	no
\$gp	28	global pointer	yes
\$sp	29	stack pointer	yes
\$fp	30	frame pointer	yes
\$ra	31	return address	yes

# *Instruction Formats*

- There are three instruction format types

**R type**

<b>op</b>	<b>rs</b>	<b>rt</b>	<b>rd</b>	<b>shamt</b>	<b>funct</b>
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits

**I type**

<b>op</b>	<b>rs</b>	<b>rt</b>	<b>16-bit address</b>
-----------	-----------	-----------	-----------------------

**J type**

<b>op</b>	<b>26-bit address</b>
-----------	-----------------------

# *R-type Instruction*

R type

op	rs	rt	rd	shamt	funct
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits

name	Example						Comments
add	0	18	19	17	0	32	add \$s1, \$s2, \$s3
sub	0	18	19	17	0	34	sub \$s1, \$s2, \$s3
slt	0	18	19	17	0	42	sub \$s1, \$s2, \$s3
jr	0	31	0	0	0	8	jr \$ra

# *I-type Instruction*


I type

op	rs	rt	16-bit address
----	----	----	----------------

name	Example				Comments
lw	35	18	17	Immediate	lw \$s1, 100(\$s2)
sw	43	18	17	Immediate	sw \$s1, 100(\$s2)
beq	4	17	18	Immediate	beq \$s1, \$s2, 100
bne	5	17	18	Immediate	bne \$s1, \$s2, 100

# Addressing Modes

## Base addressing

 


## data memory



`lw $s1, index($s2)`

## PC-relative addressing

 


## instruction memory




`beq $s1, $s2, Loop`

# *J-type Instructions*

J type

 

name		Example	Comments
j	2	Immediate	j 10000
jal	3	Immediate	jal 10000

 


Pseudo-direct addressing




# ALU Symbol & Control

ALU control lines	Function
000	and
001	or
010	add
110	subtract
111	Set on less than

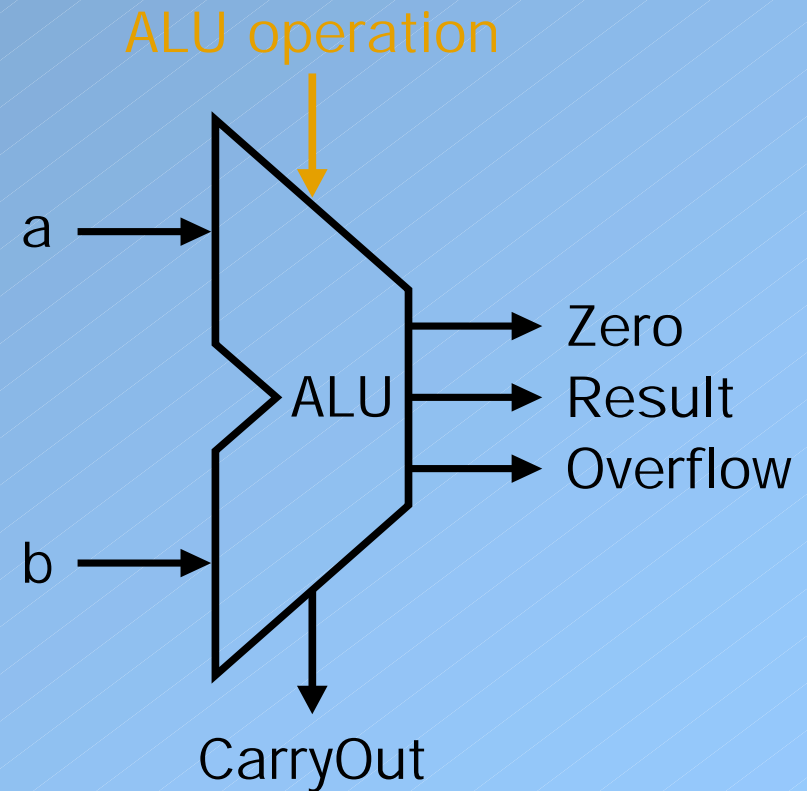


# *Implementing Instruction Fetch*

 


# Implementing R-Type ALU Operations

op	rs	rt	rd	shamt	funct
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits


add rd, rs, rt

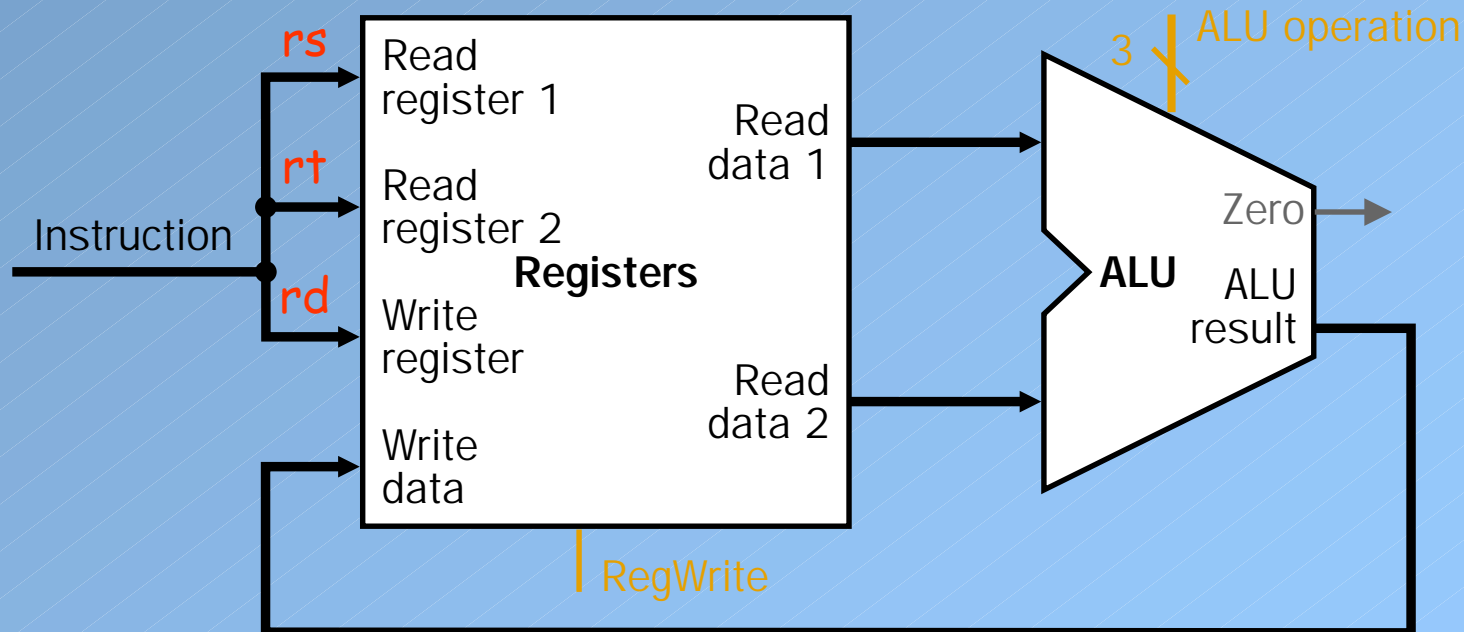

# Implementing Load & Stores

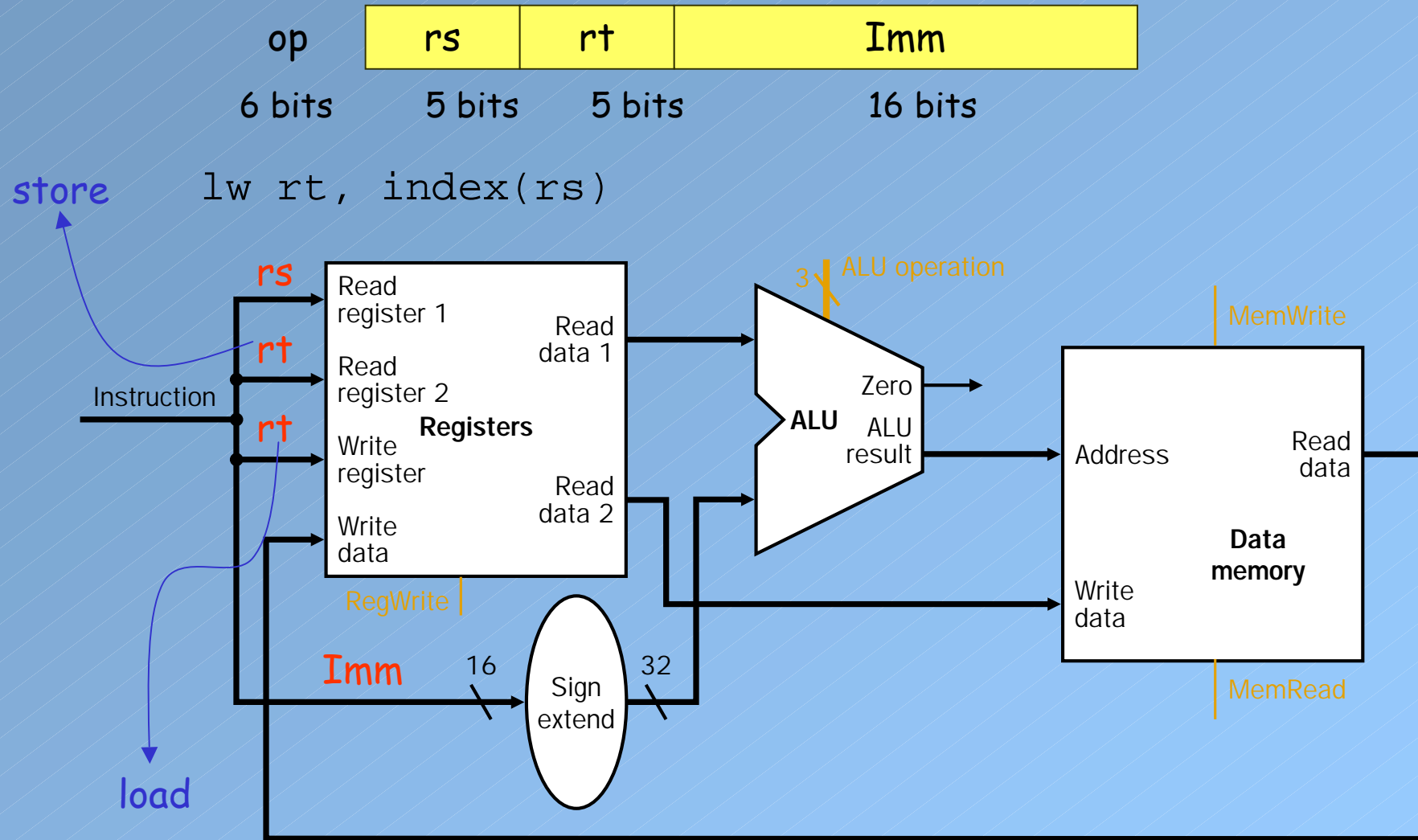


# Implementing Branches

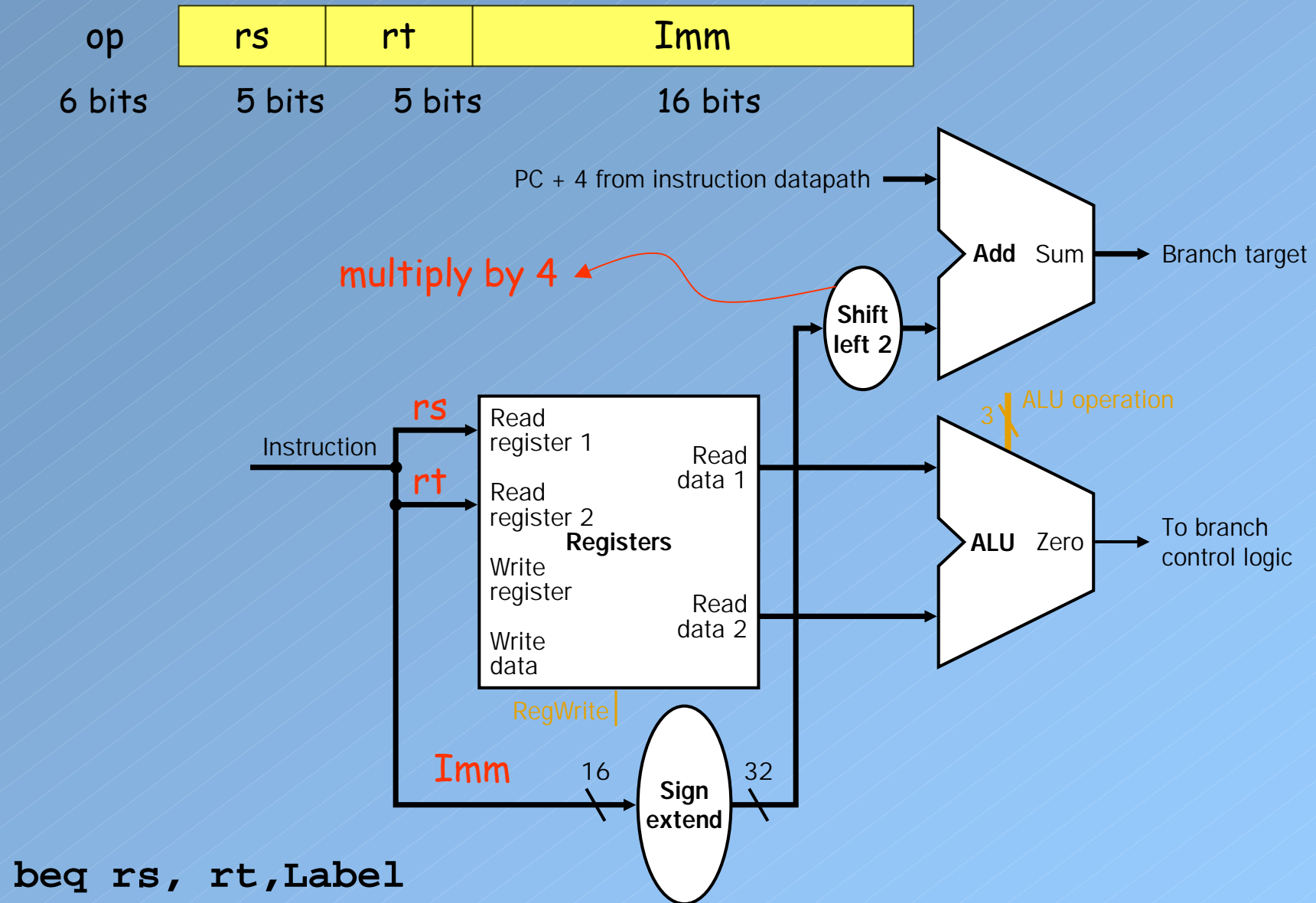
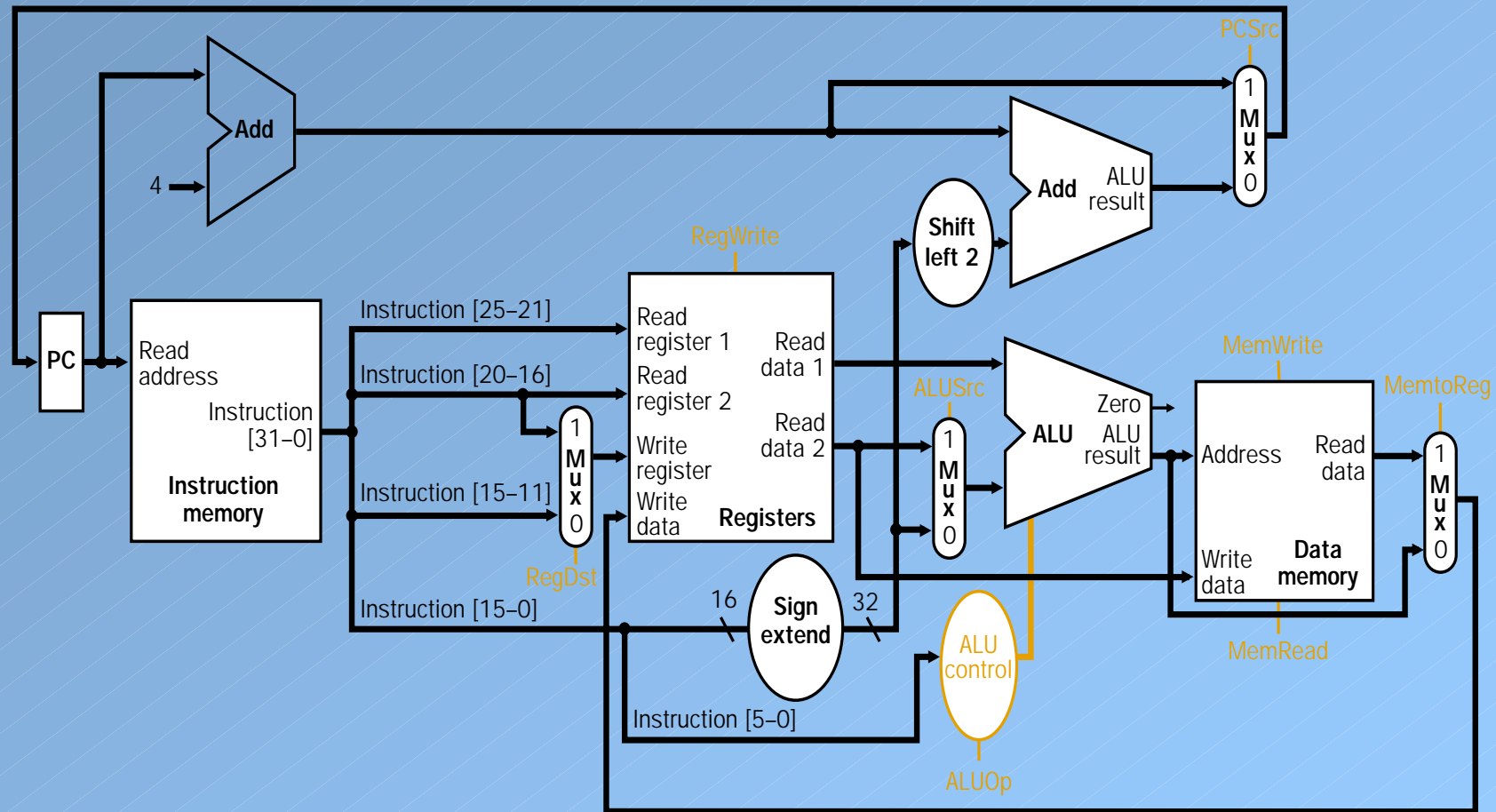
# Building the Datapath

Idea: Use multiplexors to stitch them together



# *Control*

- Control Signals
  - Selecting the operations to perform (ALU, load/store, beq, etc.)
  - Controlling the flow of data (multiplexor's select inputs)
  - Read/write enable inputs of memory and register file
- Information comes from the 32 bits of the instruction

# *ALU Control Unit*

- ALU performs
  - addition for loads and stores
  - subtraction for branches (beq)
  - no operation for jumps
  - or the operation is determined by the function field for R-type of information.
- ALU Control unit will have the following inputs:
  - two-bit control field called ALUOp
  - and Function field



# ALU Control Unit

Instruction opcode	ALUop	Instruction operation	Func field	Desired ALU action	ALU control output
lw	00	Load word	xxxxxx	add	010
sw	00	Store word	xxxxxx	add	010
beq	01	Branch equal	xxxxxx	subtract	110
R-type	10	Add	100000	add	010
R-type	10	Subtract	100010	subtract	110
R-type	10	AND	100100	and	000
R-type	10	OR	100101	or	001
R-type	10	slt	101010	slt	111


# *Truth Table for ALU Control Unit*

ALUOp		Funct field						Operation
ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0	
0	0	X	X	X	X	X	X	010
X	1	X	X	X	X	X	X	110
1	X	X	X	0	0	0	0	010
1	X	X	X	0	0	1	0	110
1	X	X	X	0	1	0	0	000
1	X	X	X	0	1	0	1	001
1	X	X	X	1	0	1	0	111


You can map the truth table to gates

# *Implementing the Control*

- ALU Control Block

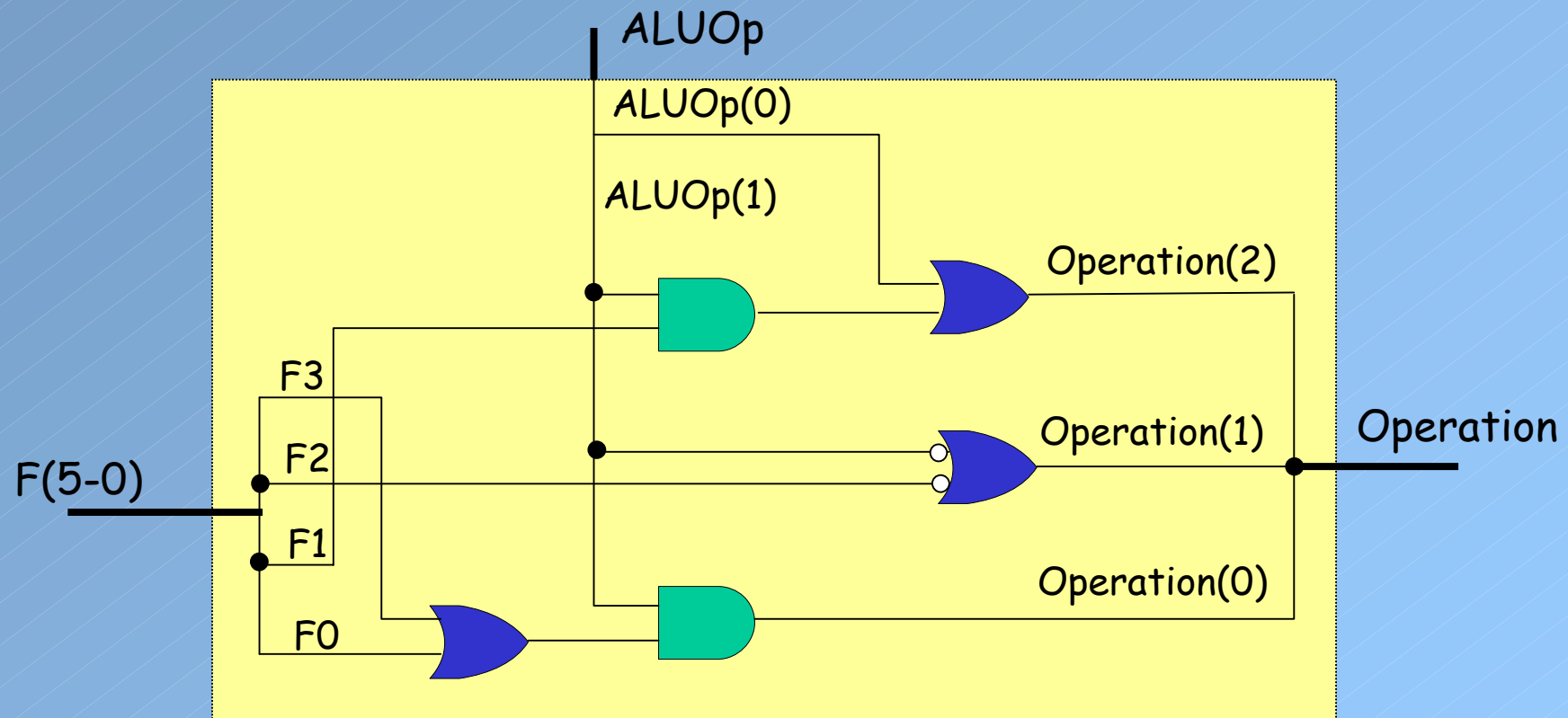


# *Datapath with the ALU Control Unit*

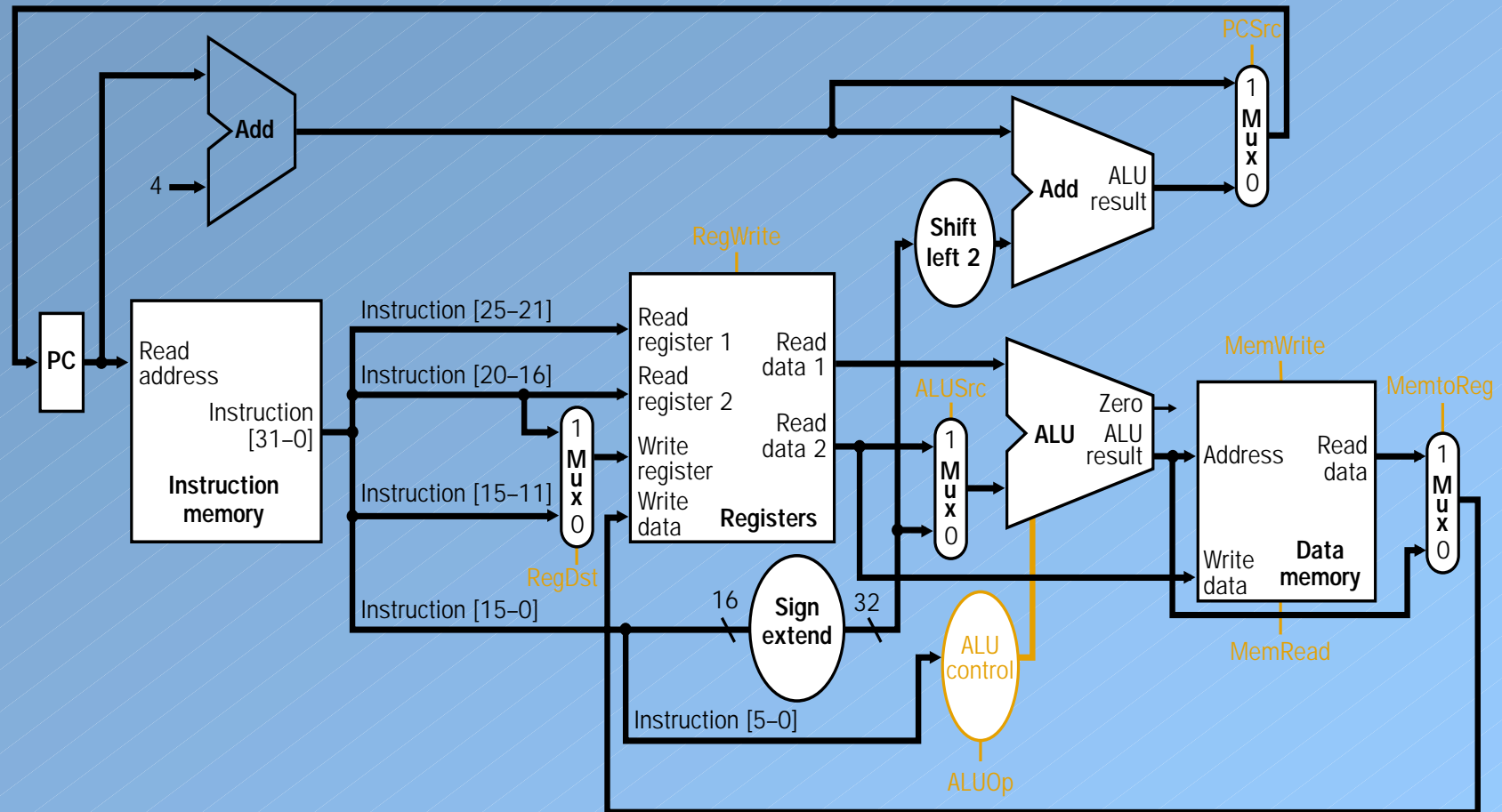


# Seven Control Signals

Signal name	Effect when de-asserted	Effect when asserted
RegDst	The destination register no comes from <code>rt</code> .	The destination register no comes from <code>rd</code> .
RegWrite	None	Destination register is written with value on <code>Writedata</code>
ALUSrc	2 <sup>nd</sup> ALU operand comes from <code>Read_Data_2</code>	2 <sup>nd</sup> ALU operand is the sign extended, lower 16 bit of the instruction
PCSrc	The PC is replaced by <code>PC + 4</code>	The PC is replaced by the branch target address
MemRead	None	Memory is read
MemWrite	None	Memory is written
MemtoReg	The value to the register <code>Writedata</code> input comes from the ALU.	The value to the register <code>Writedata</code> input comes from the data memory


# *RegDst & RegWrite*

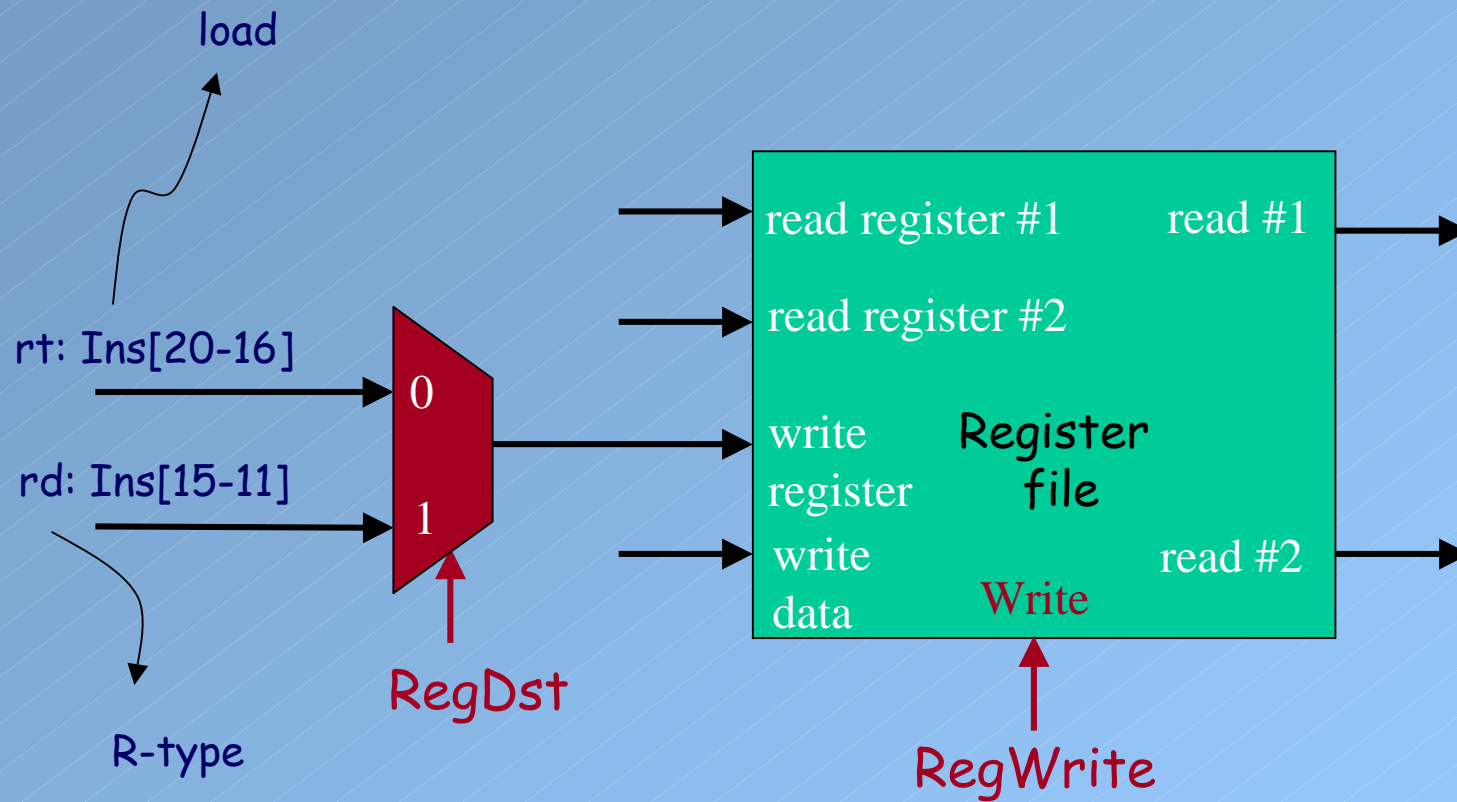

# ALUSrc

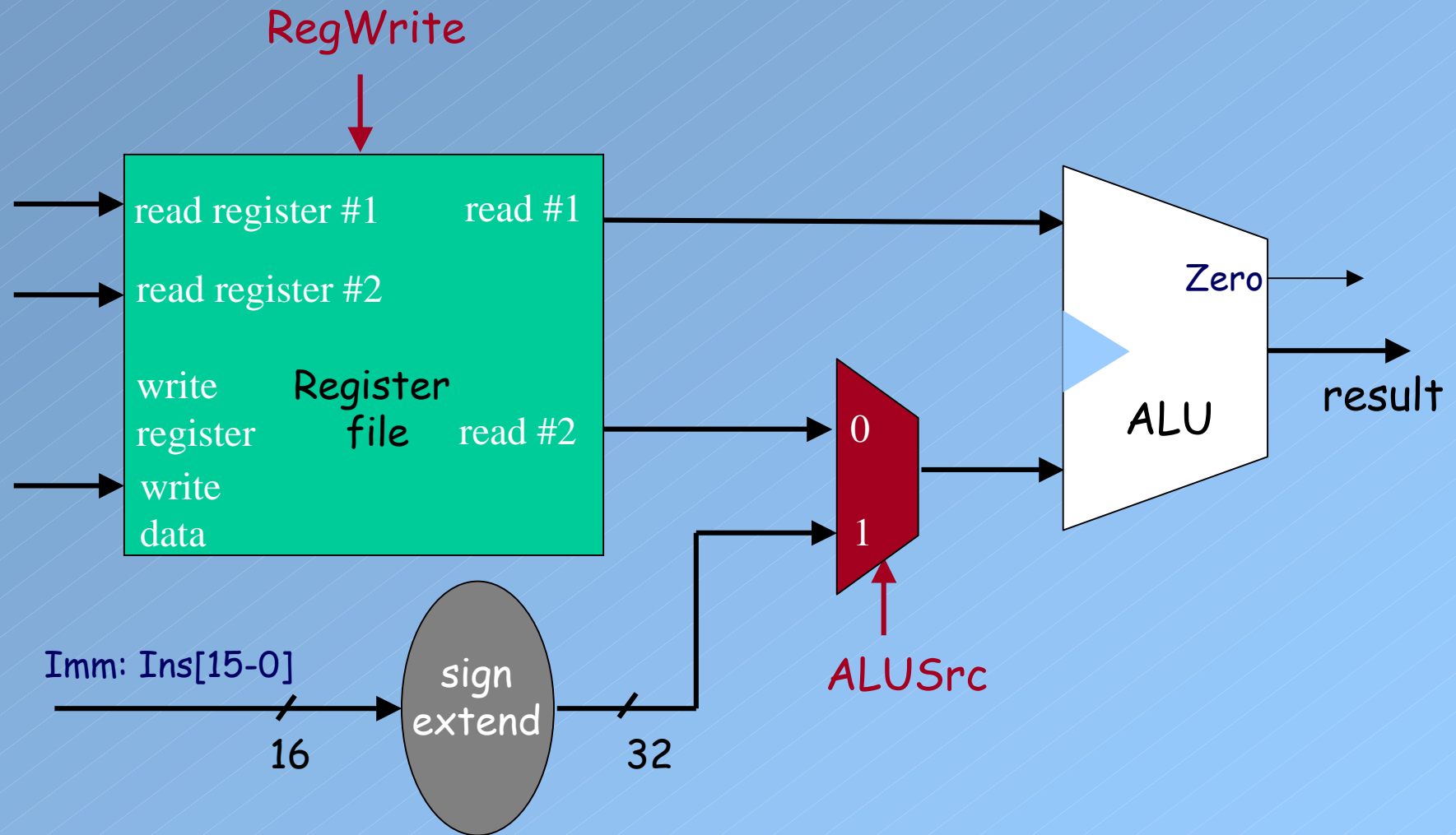


# MemtoReg

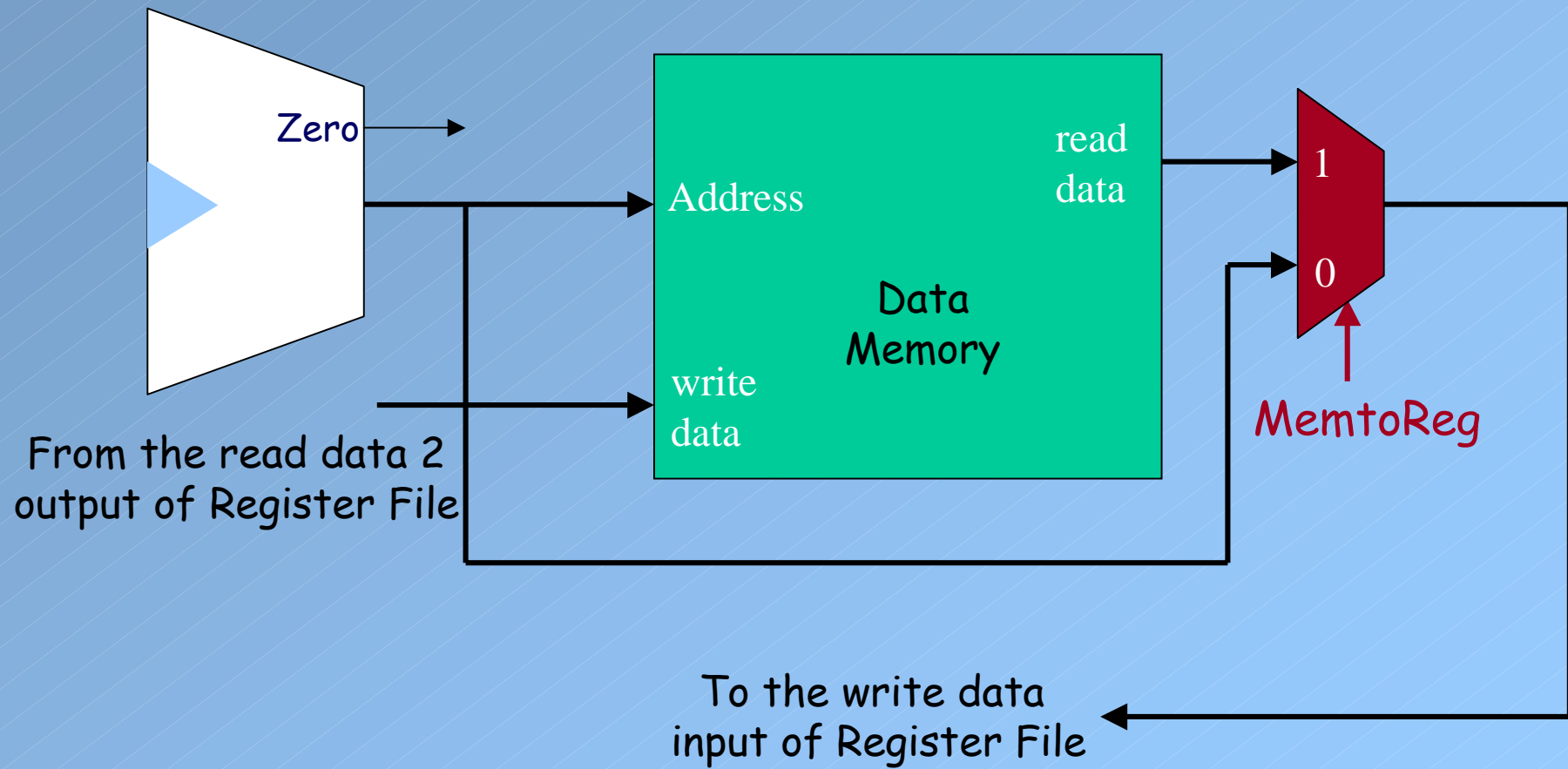




# PCSrc

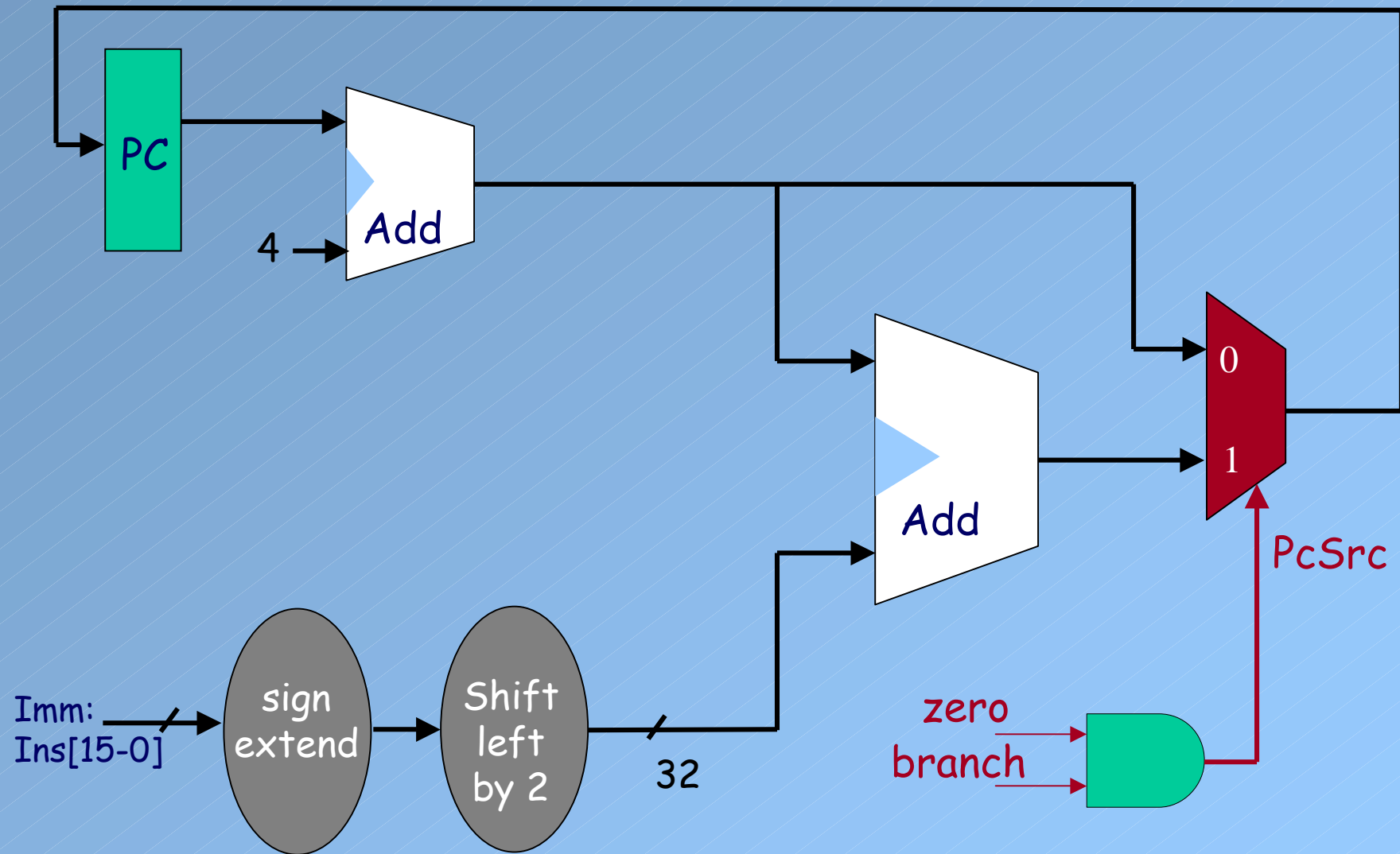

# *Datapath & Control*

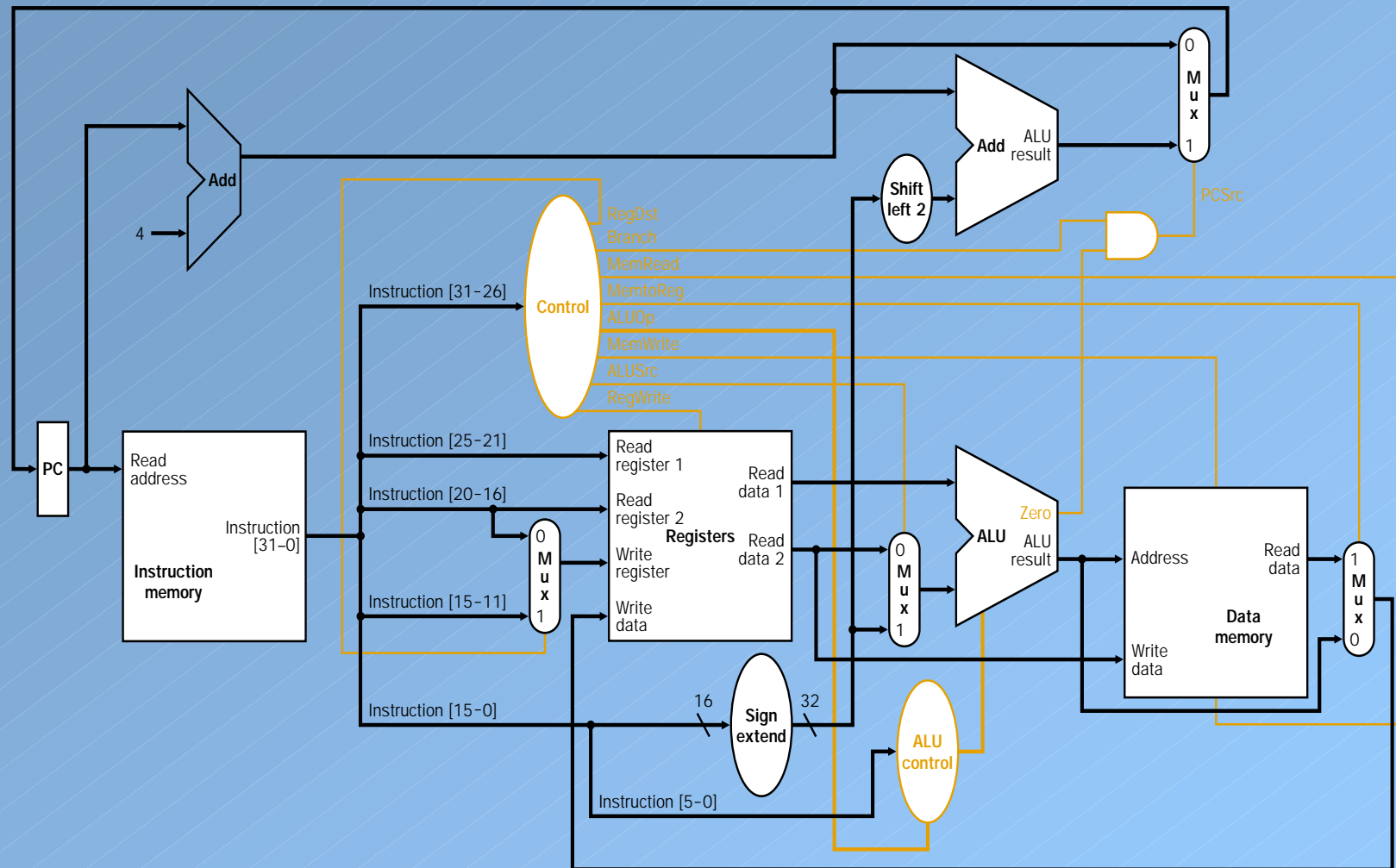


# Operation of the Datapath

Instruction	RegDest	ALUSrc	Memto-Reg	Reg Write	Mem Read	Mem Write	Branch	ALU Op1	ALU Op0
R-format	1	0	0	1	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0
sw	X	1	X	0	0	1	0	0	0
beq	X	0	X	0	0	0	1	0	1

Example Flow: beq \$s0, \$s1, address

- The instruction is fetched from memory and PC is incremented
- Read two register values
- Subtract one from the other, calculate the branch address
- Use the zero signal to determine which of the addresses is to be used for fetching the next instruction

# Single Cycle Datapath

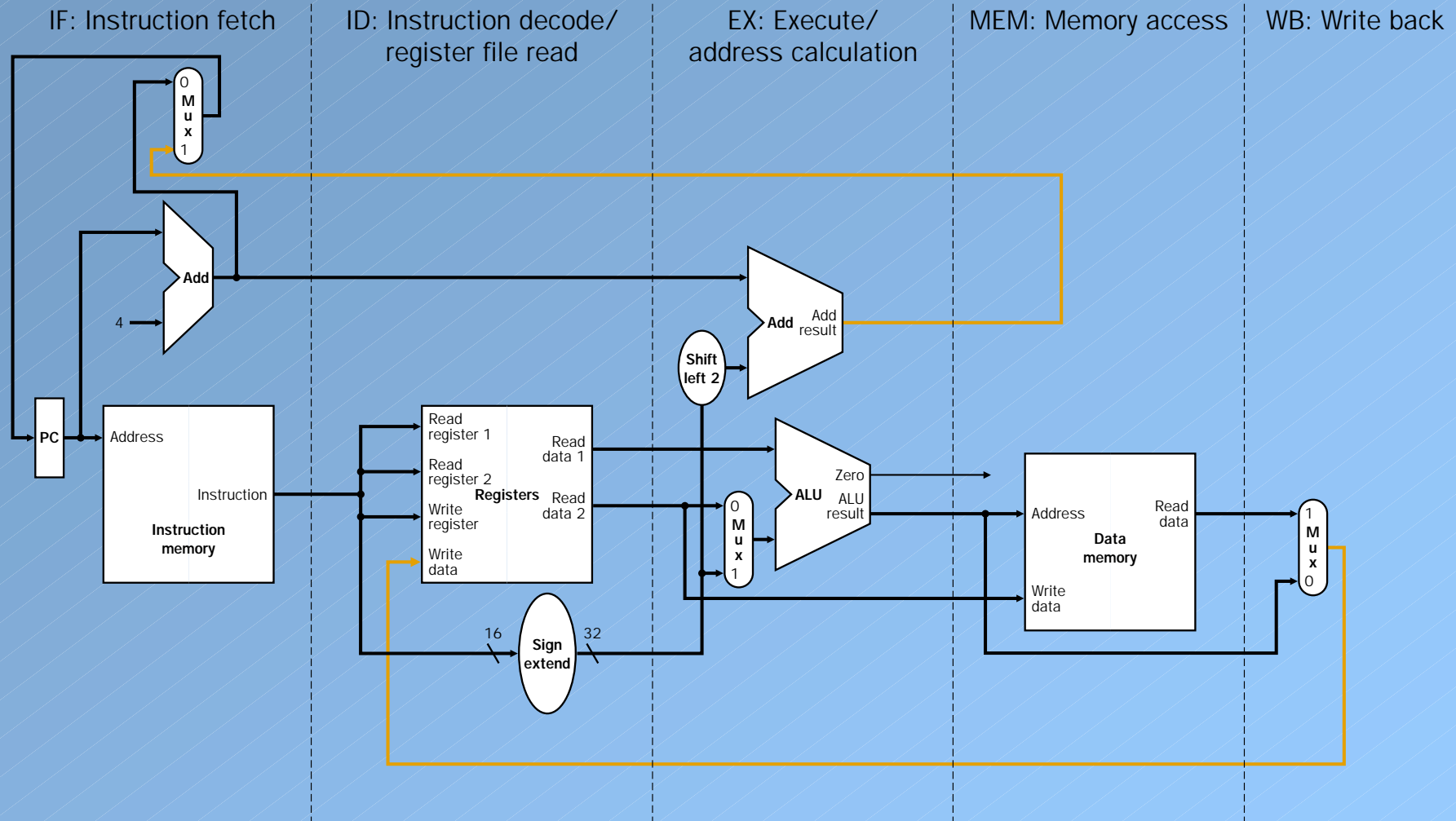

# *The Stages of an Instruction*



- MIPS instructions classically take five steps:
  1. Fetch instruction from memory (IF)
  2. Read registers while decoding the instruction (ID)
  3. Execute the operation or calculate an address (EX)
  4. Access an operand in memory (MEM)
  5. Write result into a register (WB)

# *Times of Different Instruction Steps*

Instruction class	Inst. Fetch	Register Read	ALU op	Data access	Register write	Total time
lw	2 ns	1ns	2 ns	2 ns	1 ns	8 ns
sw	2 ns	1ns	2 ns	2 ns		7 ns
R-format	2 ns	1ns	2 ns		1 ns	6 ns
Branch	2 ns	1ns	2 ns			5 ns

Clock period that can be used in single-cycle implementation will be 8 ns for all instruction.

# Pipelined vs. Nonpipelined

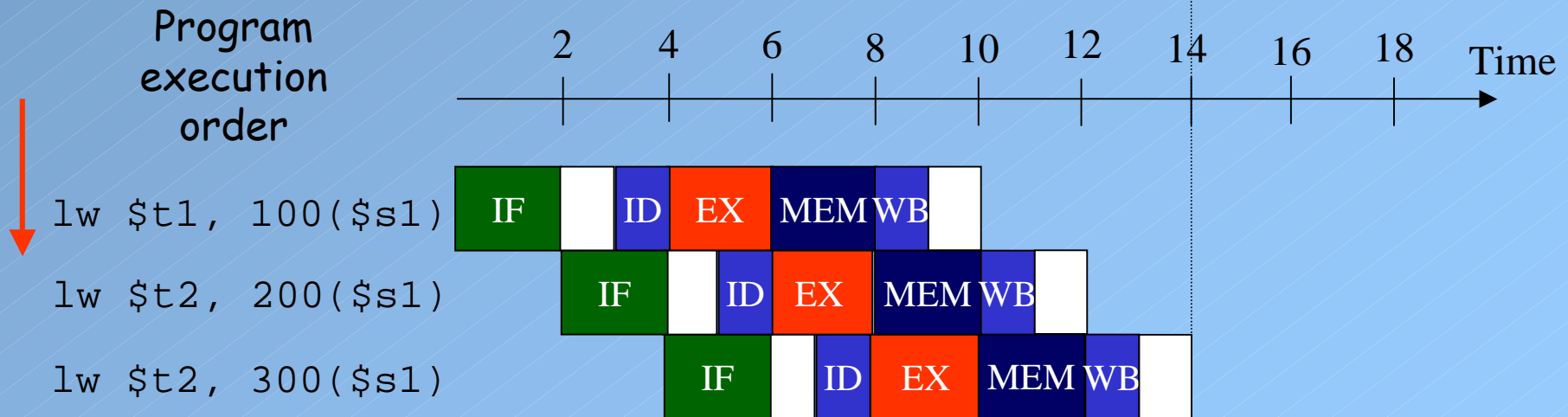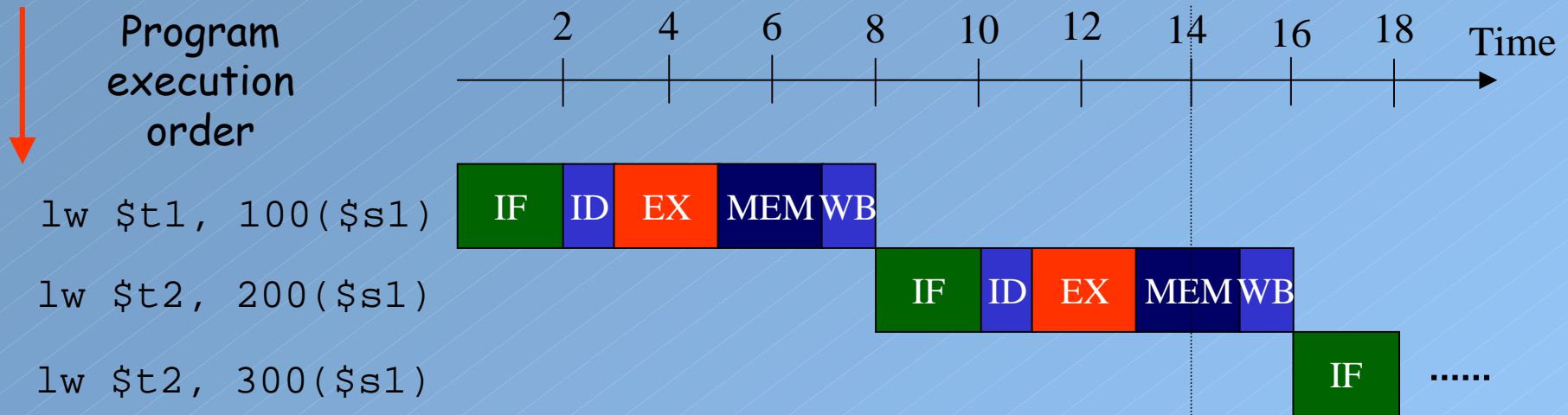


# *Design of Pipelined Datapath*


- Break the datapath into smaller segments
- Portions of datapath can be shared by instructions
- Use registers between two consecutive segments of the datapath to hold the intermediate results.
- Pipeline registers
- Data transfer between the stages happens through the pipeline registers




# Pipelined Datapath

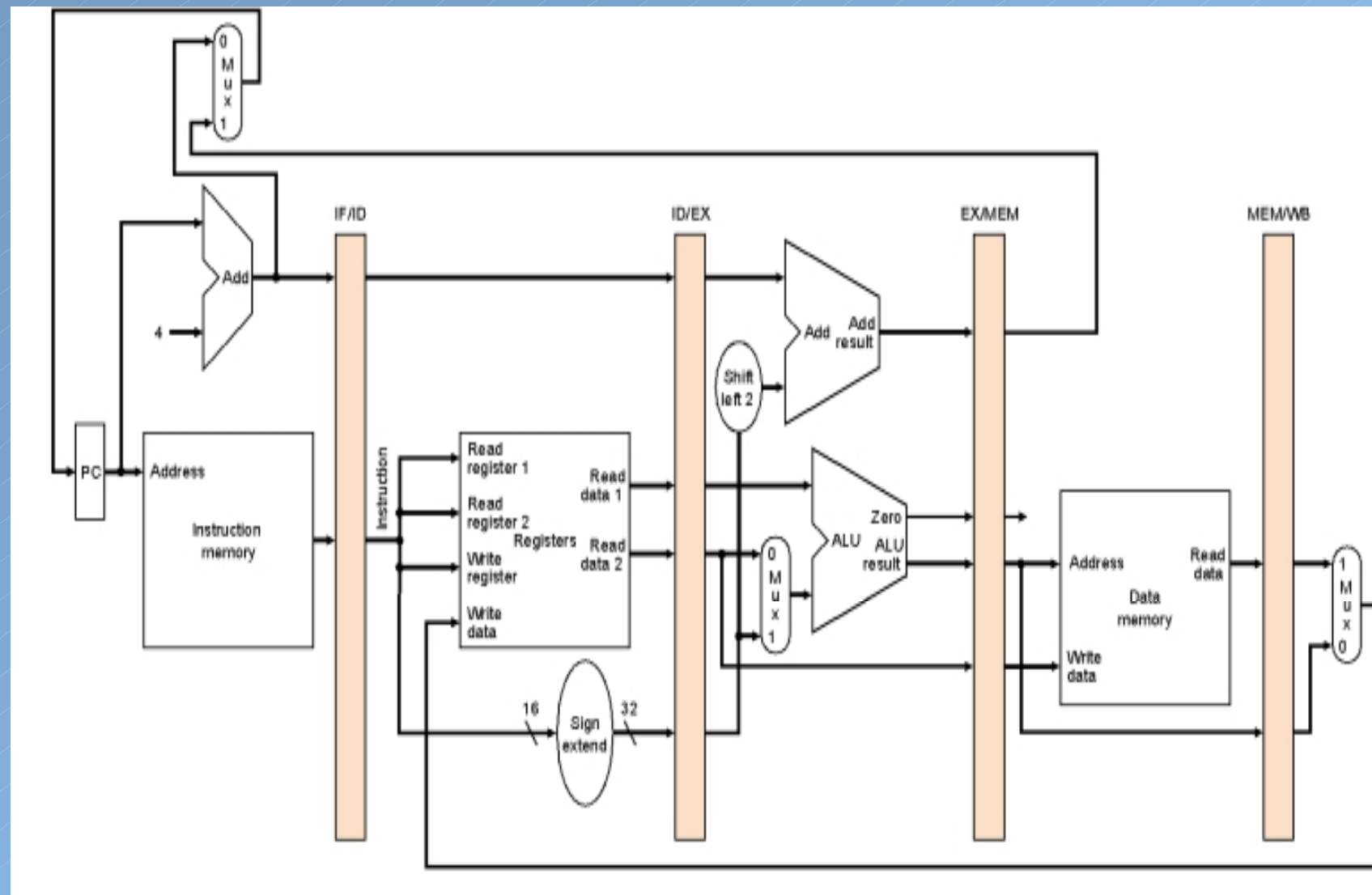


# *Example: IF of $1_w$*

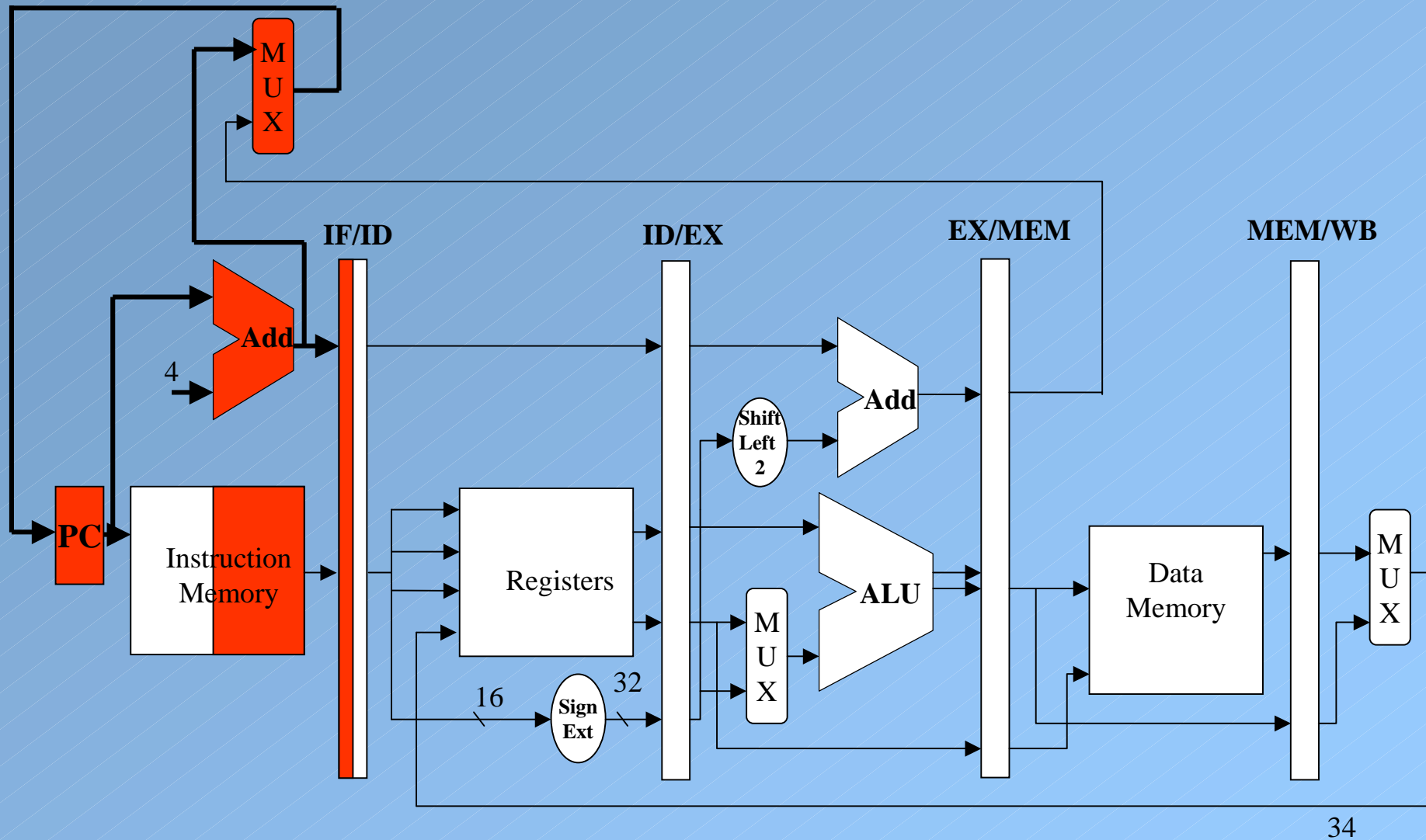


# *Example: ID of 1w*

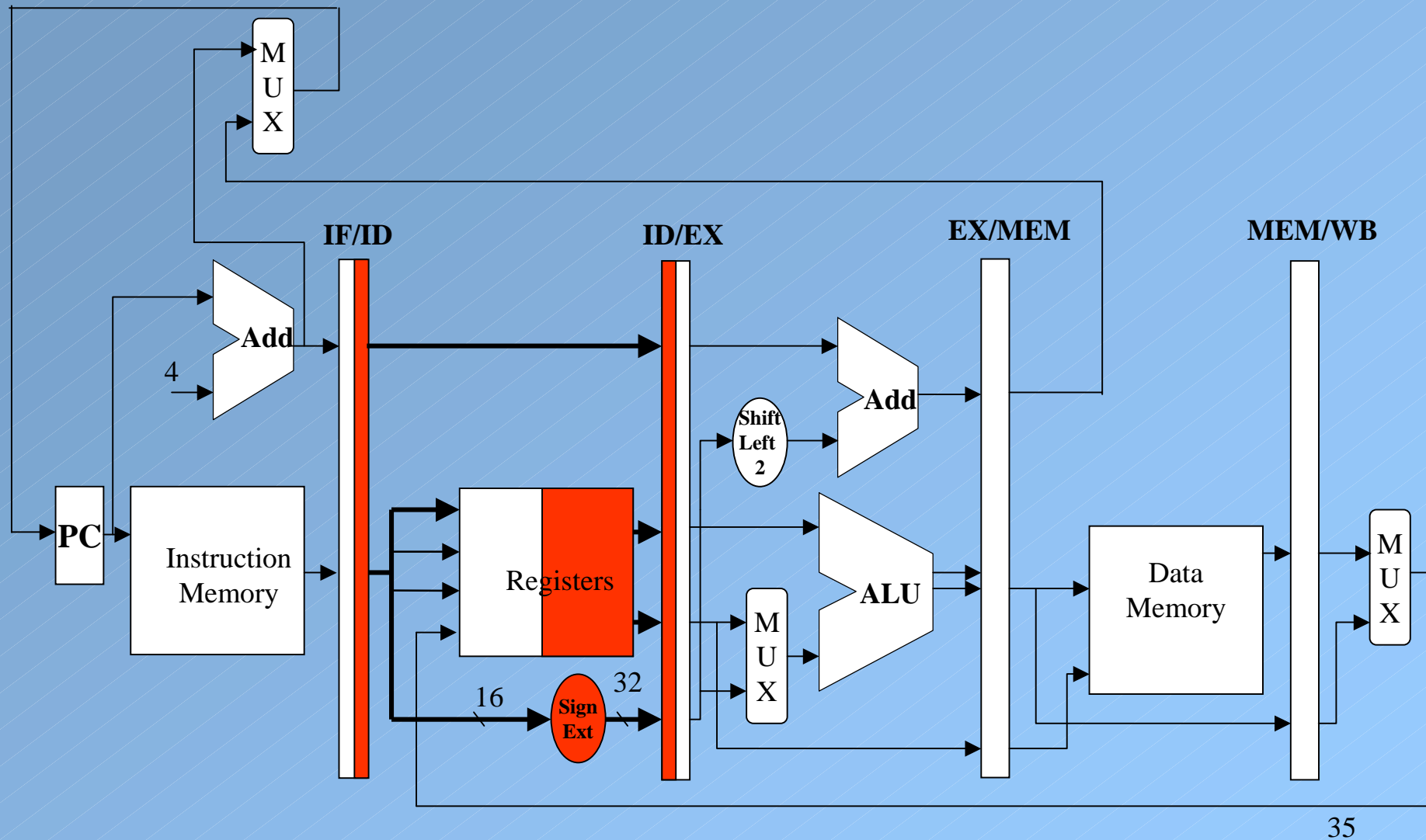


# *Example: EX of $lw$*

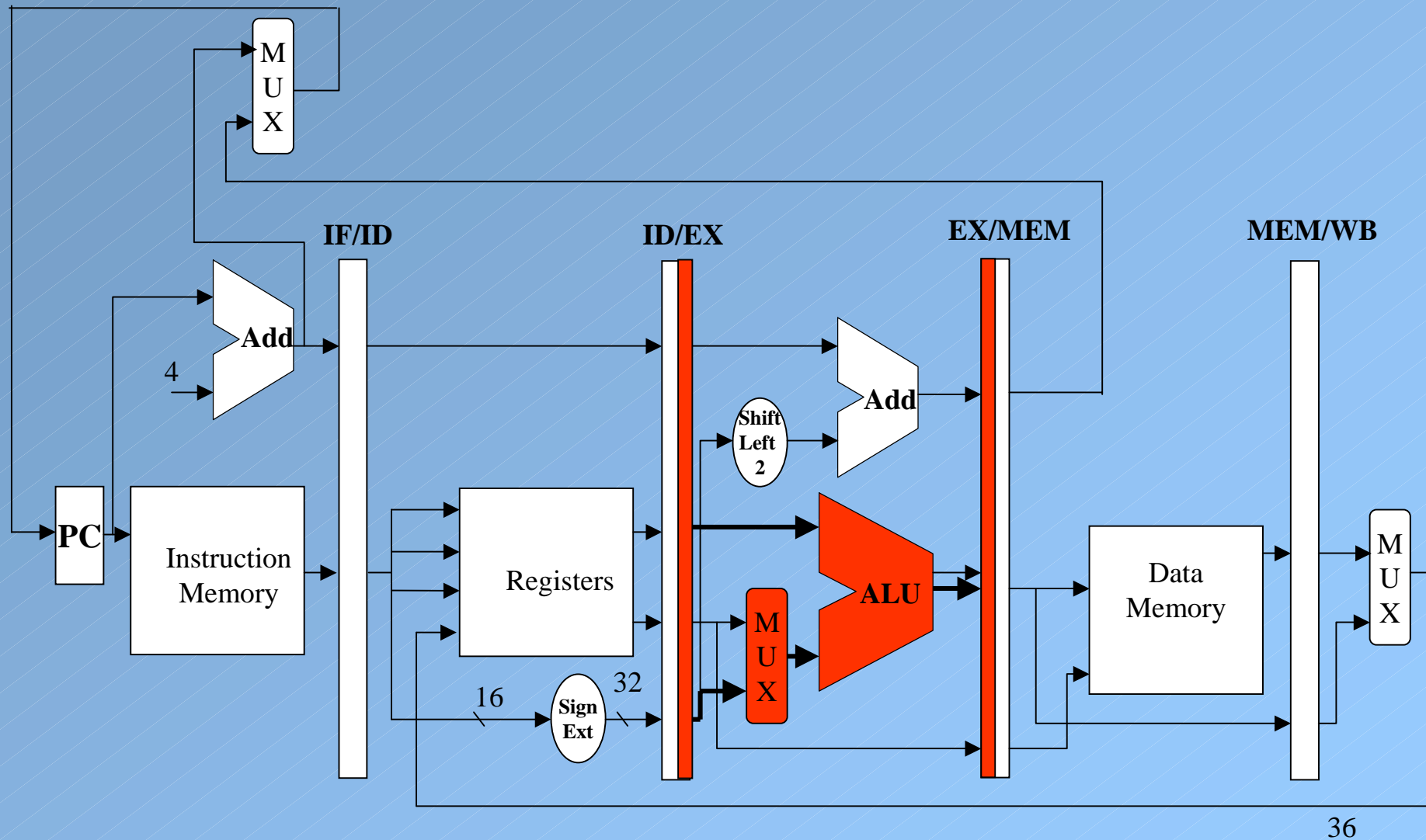


# *Example: MEM of 1w*

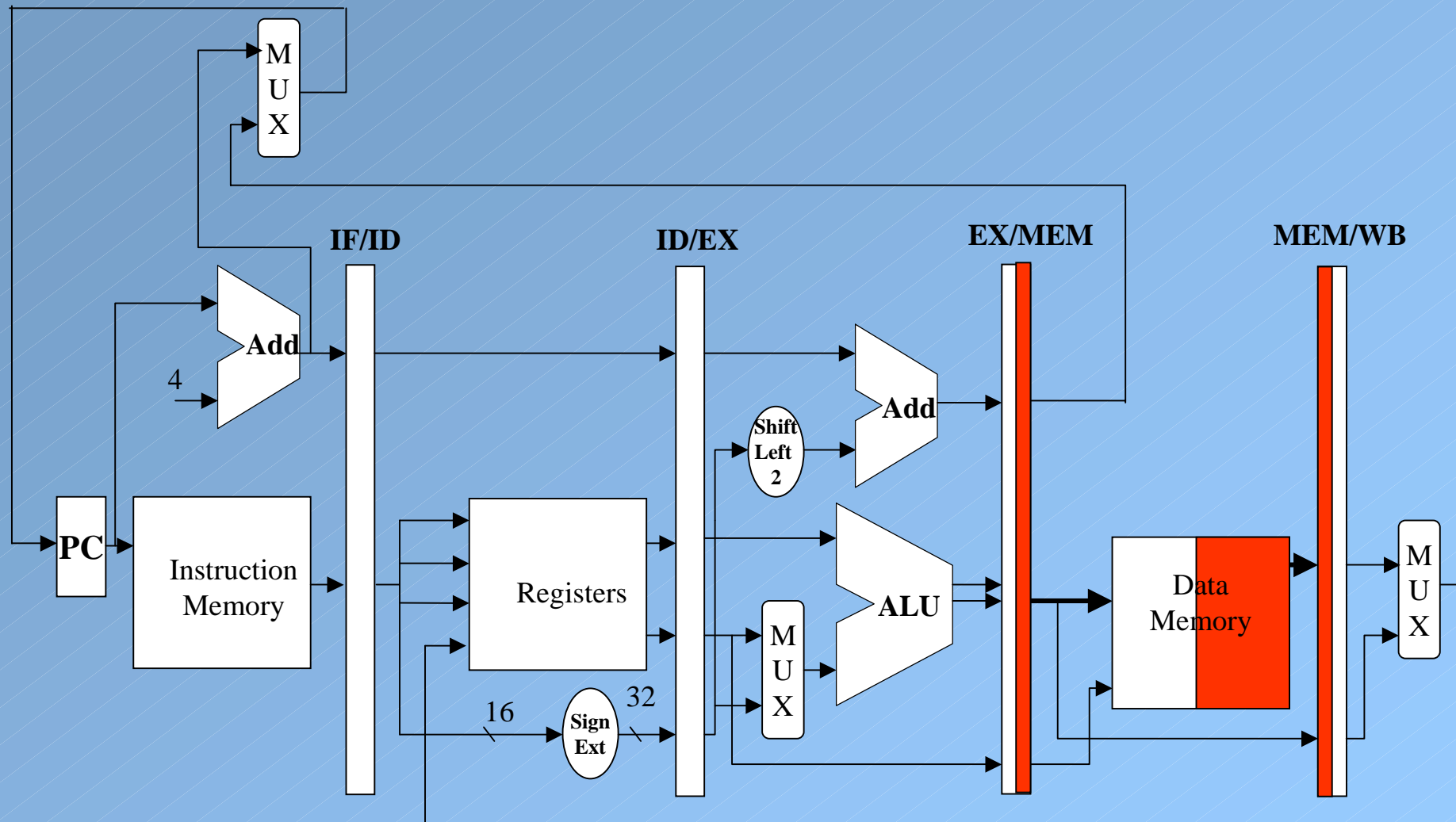


# *Example: WB of $1_w$*

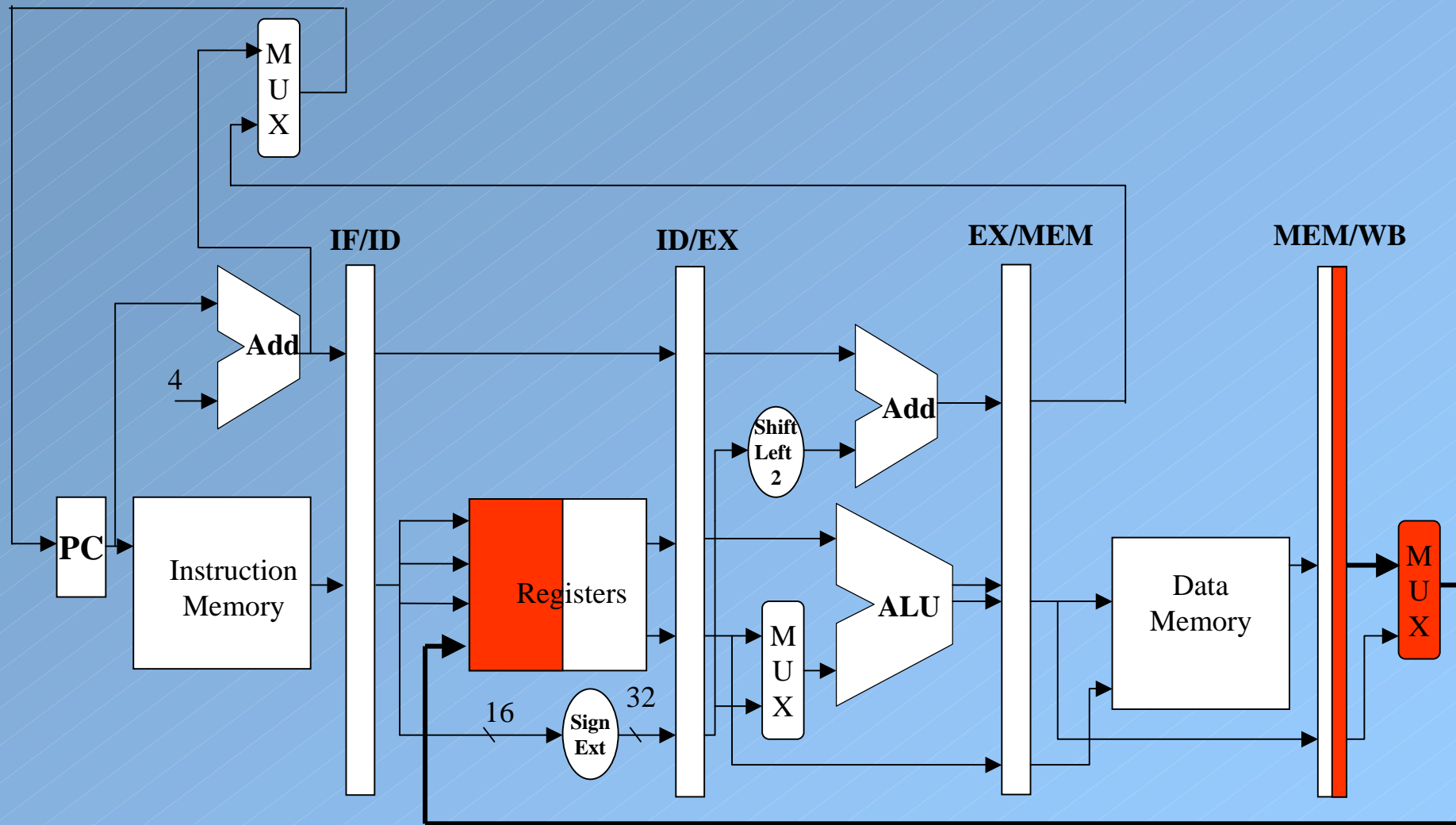

# *Corrected Datapath*

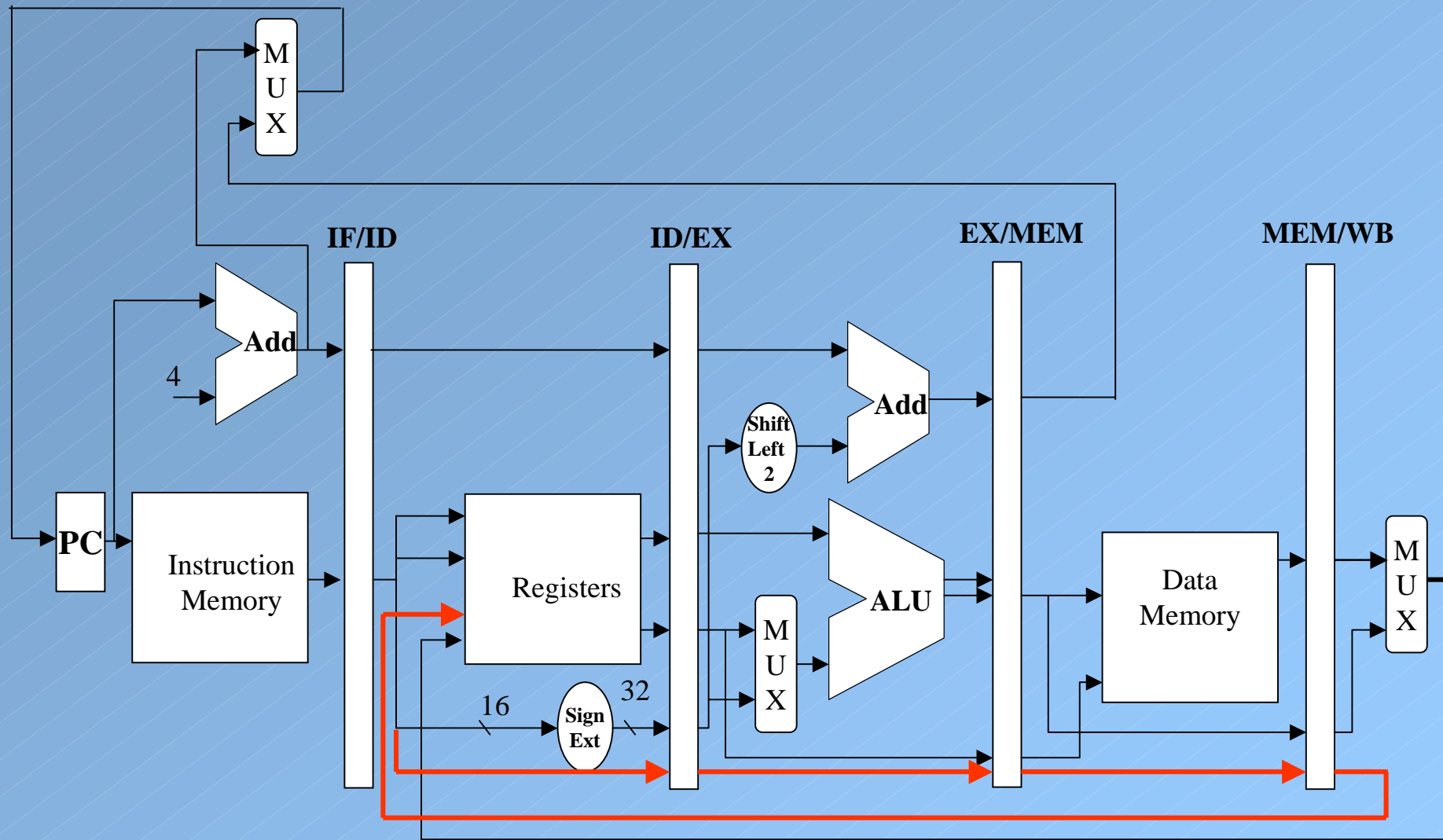


## Example 2: Store word, EX stage

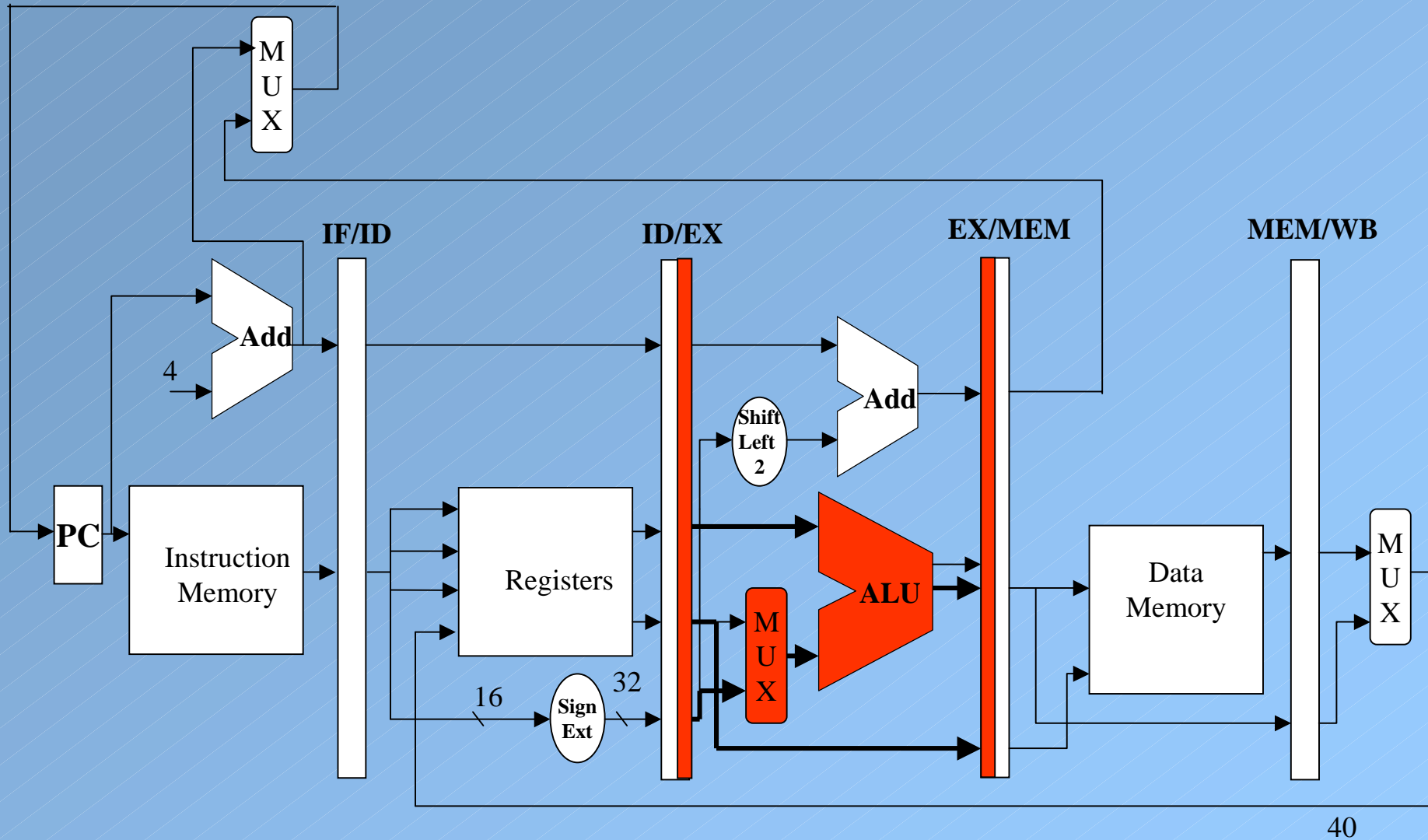




## *Example 2: MEM of sw*

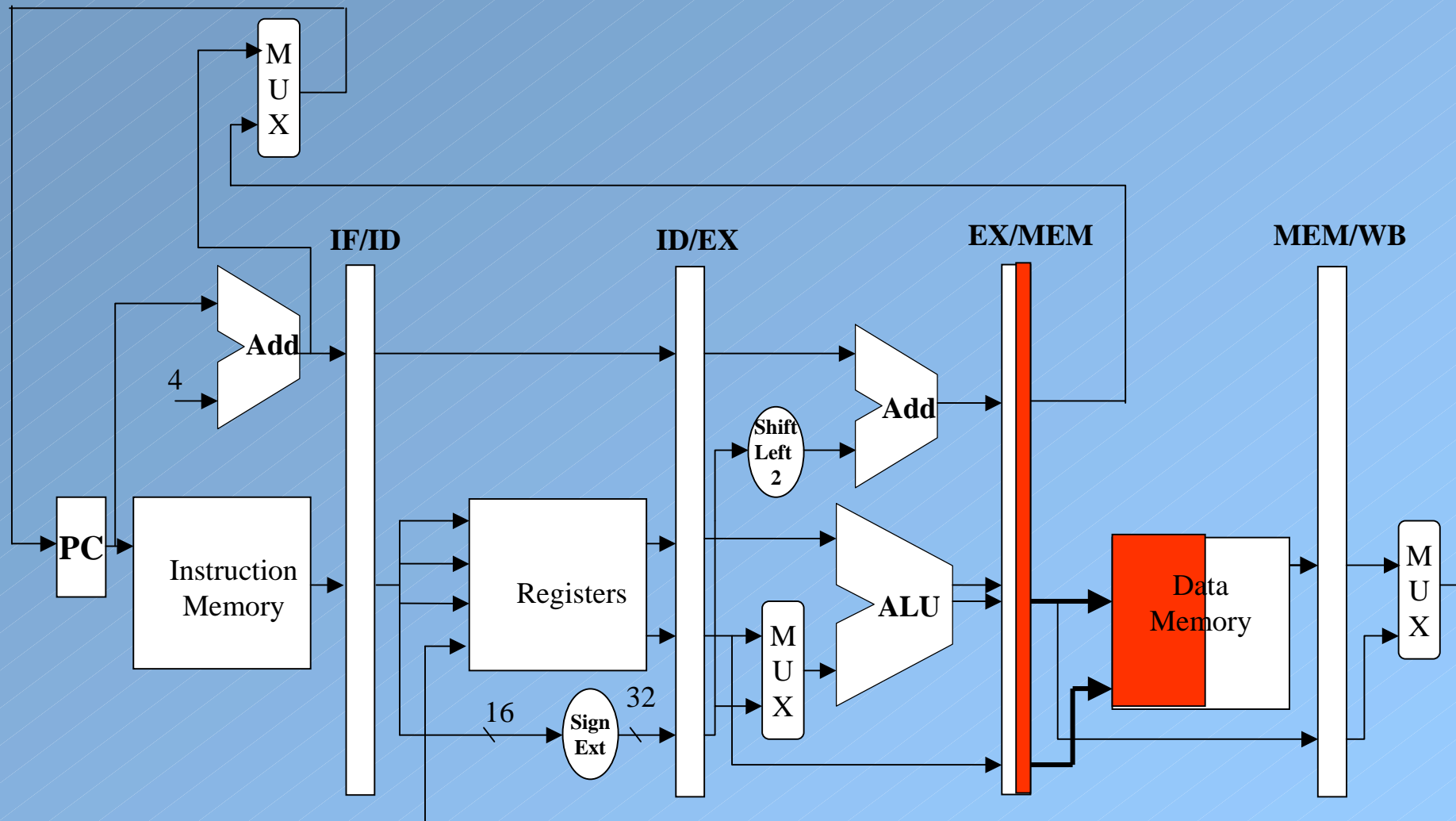

## Example 2: WB of sw


Oops! Nothing happening

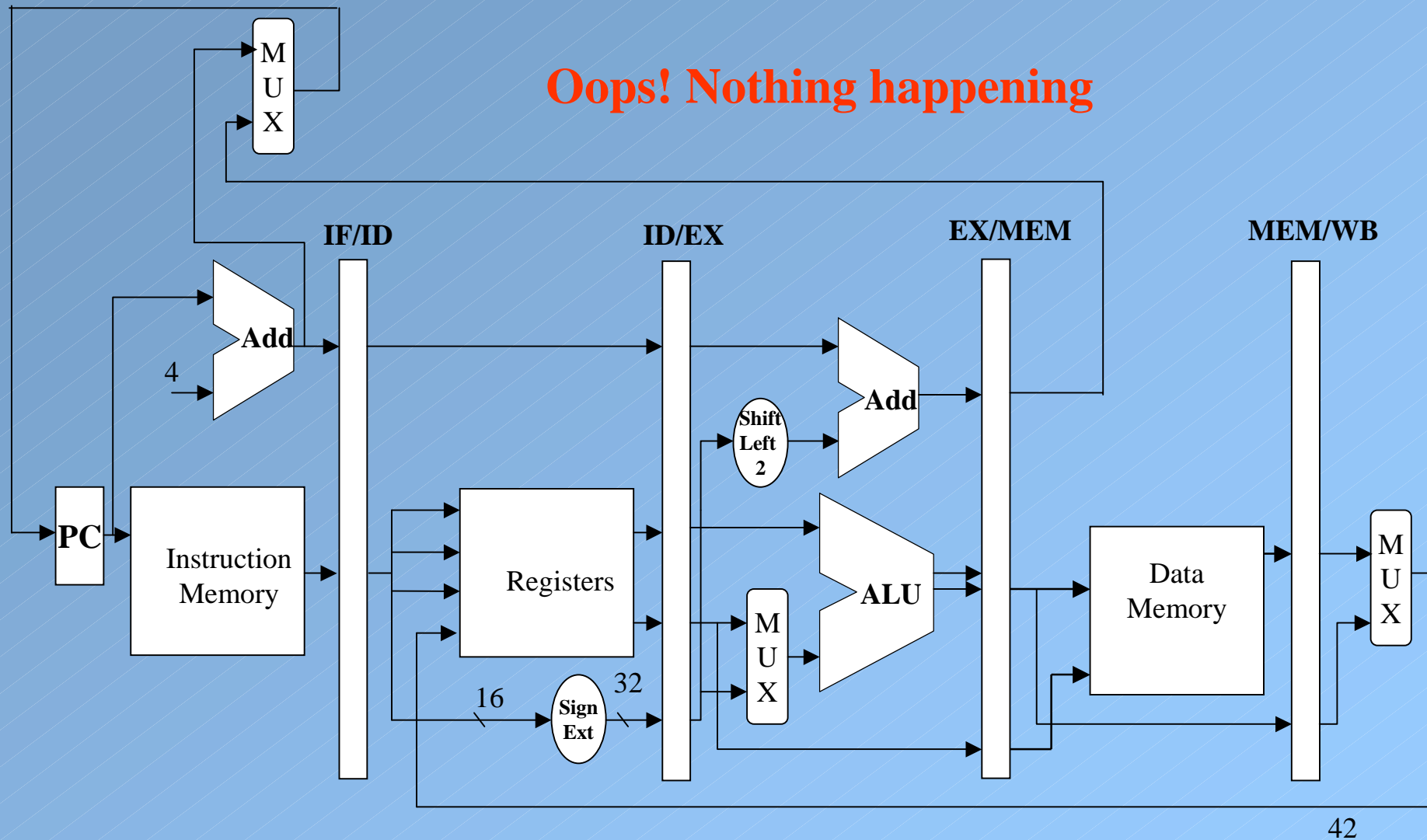

# *Pipelined Control*

- PC is written on each clock cycle (no write signal)
- No write signals for pipeline registers.
- IF stage: no control signal since instruction is read and PC is updated each cycle
- ID stage: No control signals
- EX stage: RegDst, ALUOp, ALUSrc
- MEM stage: branch, MemRead, MemWrite
- WB stage: MementoReg, RegWrite
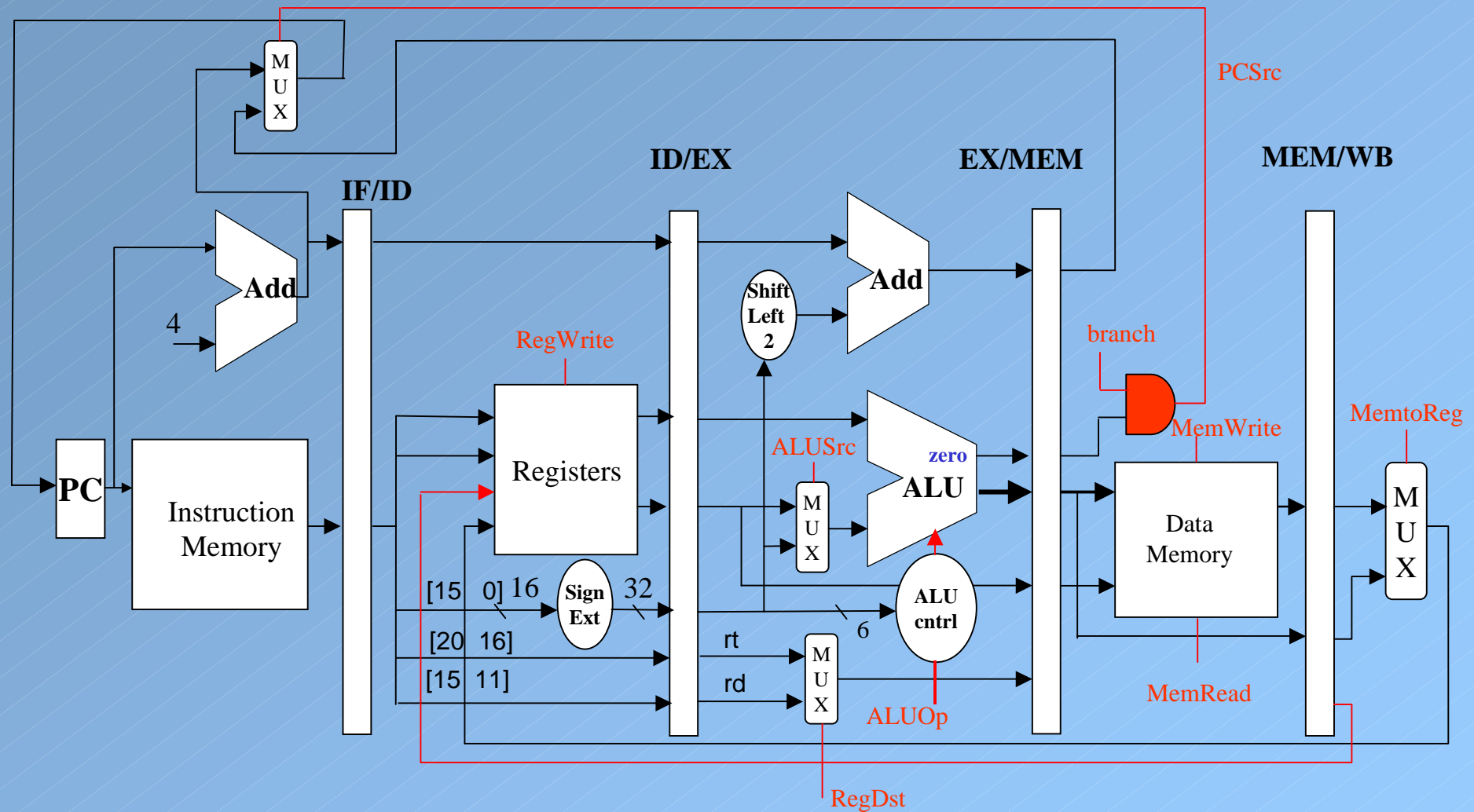
# *Pipelined Datapath with Control Signals*



## Reminder: Seven Control Signals


Signal name	Effect when deasserted	Effect when asserted
RegDst	The destination register number comes from <u>rt</u> .	The destination register number comes from <u>rd</u> .
RegWrite	None	Destination register is written with value on <u>Writedata</u>
ALUSrc	2 <sup>nd</sup> ALU op comes from Read data 1 (i.e. rt)	2 <sup>nd</sup> ALU op is the sign extended, lower 16 bit of the instruction
PCSrc	The PC is replaced by PC + 4	The PC is replaced by the branch target address
MemRead	None	Memory is read
MemWrite	None	Memory is written
MemtoReg	The value to the register <u>Writedata</u> input comes from the ALU.	The value to the register <u>Writedata</u> input comes from the data memory

# *Control Signals for Instructions*


- Nine control signals that start in the EX stage
- Main control unit generates the control signals during the ID stage.

Instruction	EX Stage				MEM Stage			WB Stage	
	RegDest	ALU Op1	ALU Op0	ALU Src	Branch	Mem Read	Mem Write	Reg Write	Memto-Reg
R-format	1	1	0	0	0	0	0	1	0
lw	0	0	0	1	0	1	0	1	1
sw	x	0	0	1	0	0	1	0	x
beq	x	0	1	0	1	0	0	0	x
 
# *Control Lines for the Last Three Stages*


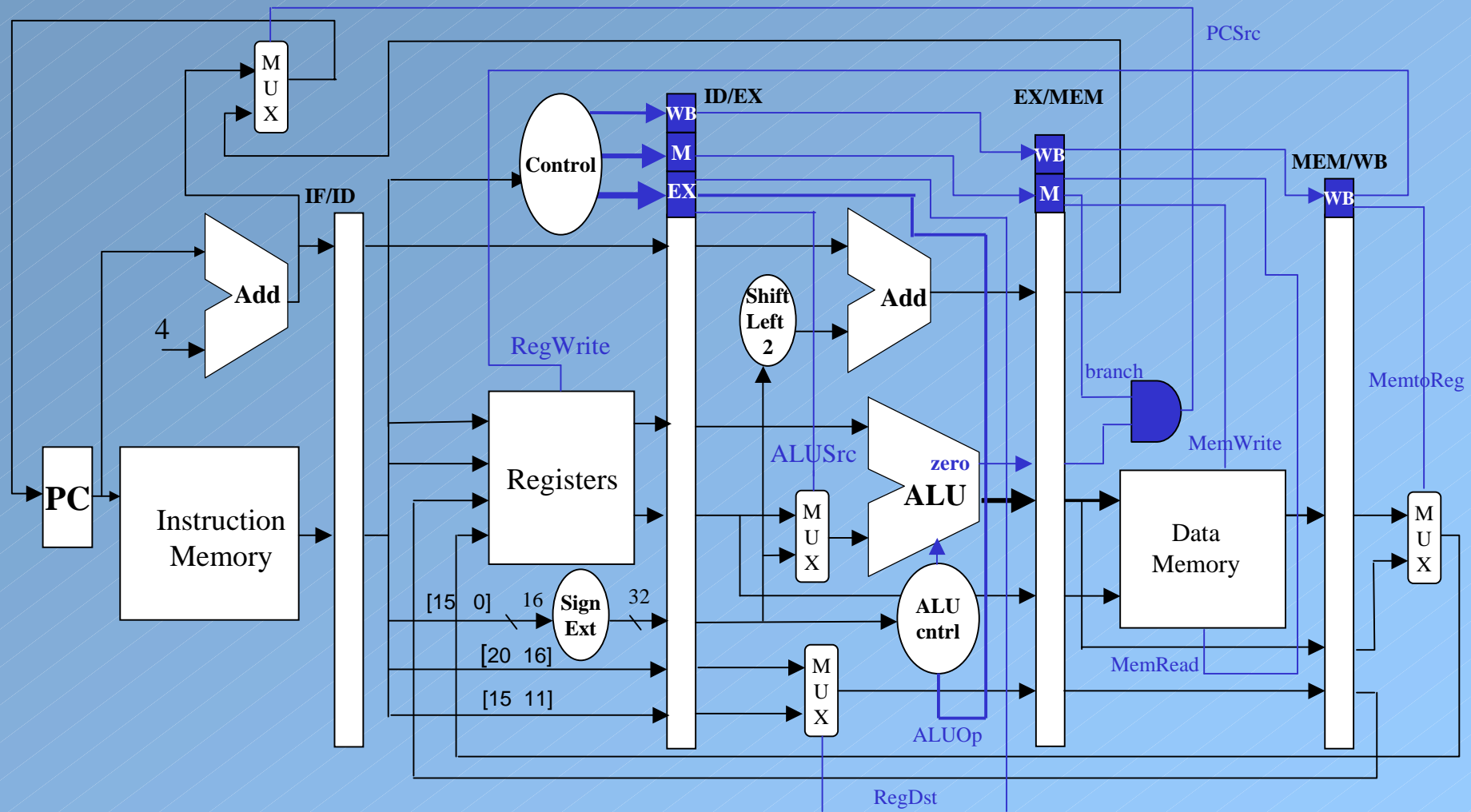
# *Pipelined Datapath with Control Signals*






## Example

- Show these five instructions going through the pipeline:

```
lw      $10,      20($1)
sub      $11,      $2,    $3
and      $12, $4,    $5
or       $13, $6,    $7
add      $14, $8,    $9
```

# Clock 1

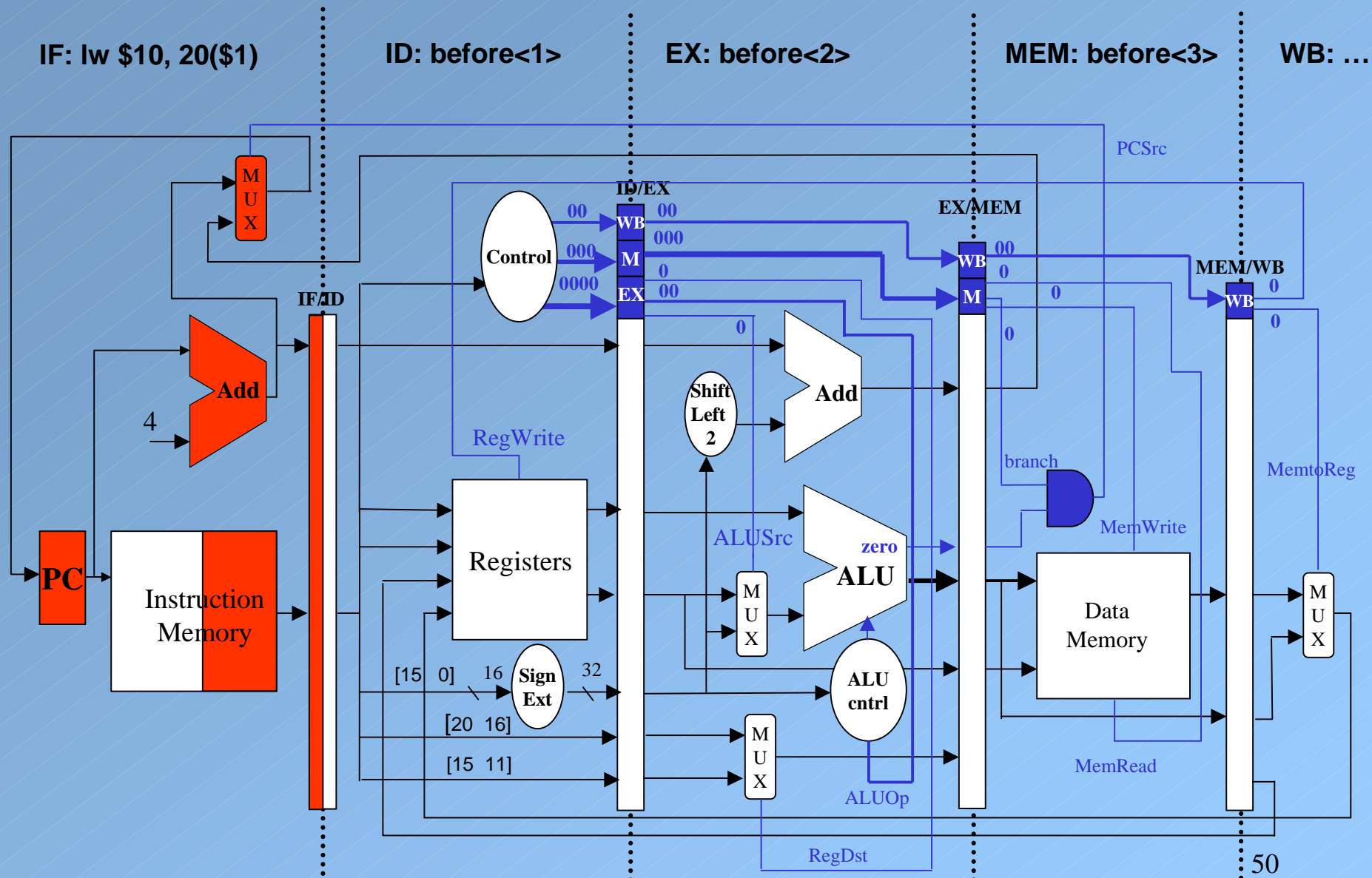

# Clock 2


IF: sub \$11, \$2, \$3

ID: lw \$10, 20(\$1)

EX: before<1>

MEM: before<2>

WB: ...

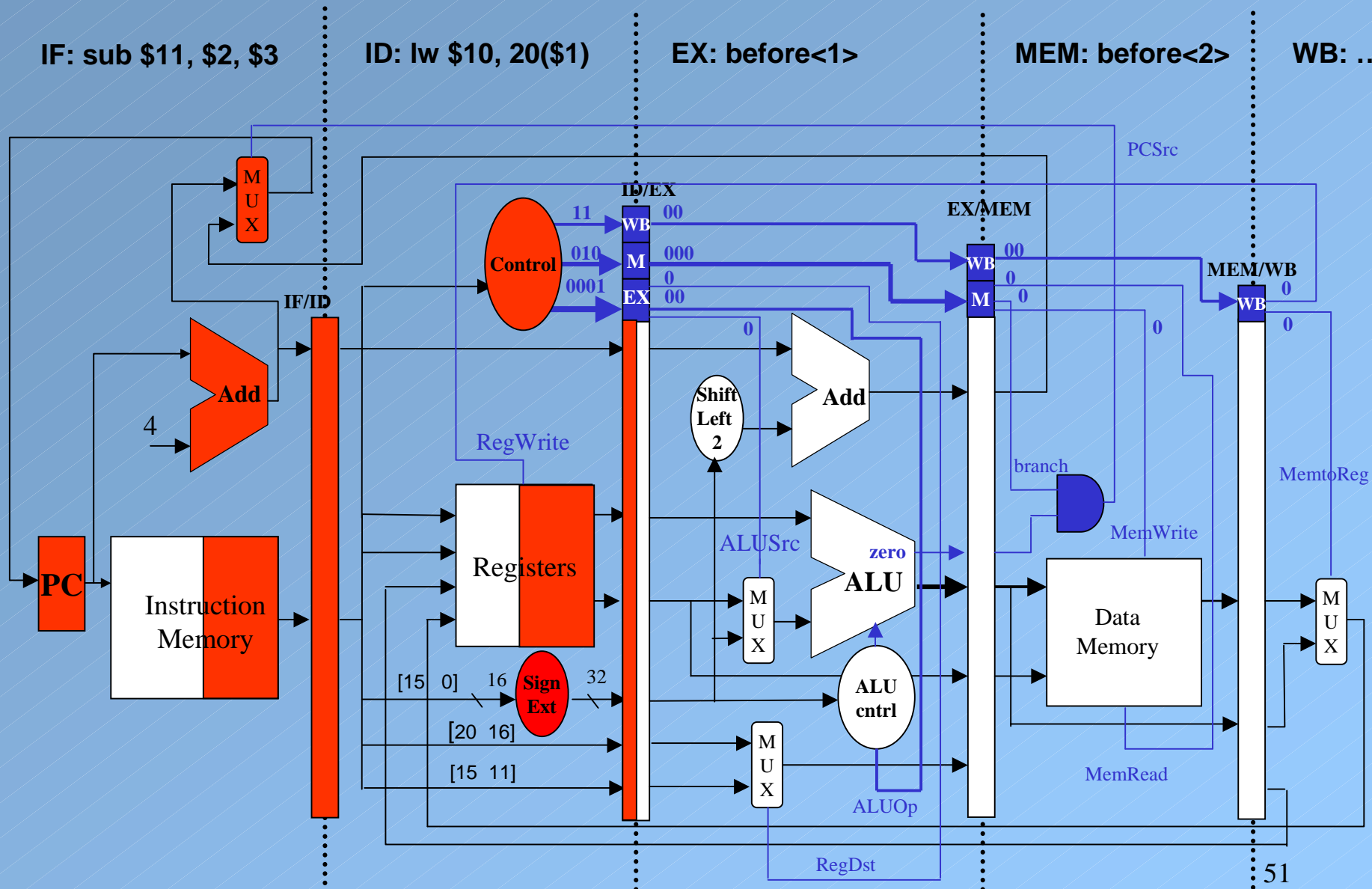

# Clock 3


IF: and \$12, \$4, \$5

ID: sub \$11, \$2, \$3

EX: lw \$10, 20(\$1)

MEM: before<1>

WB: ...

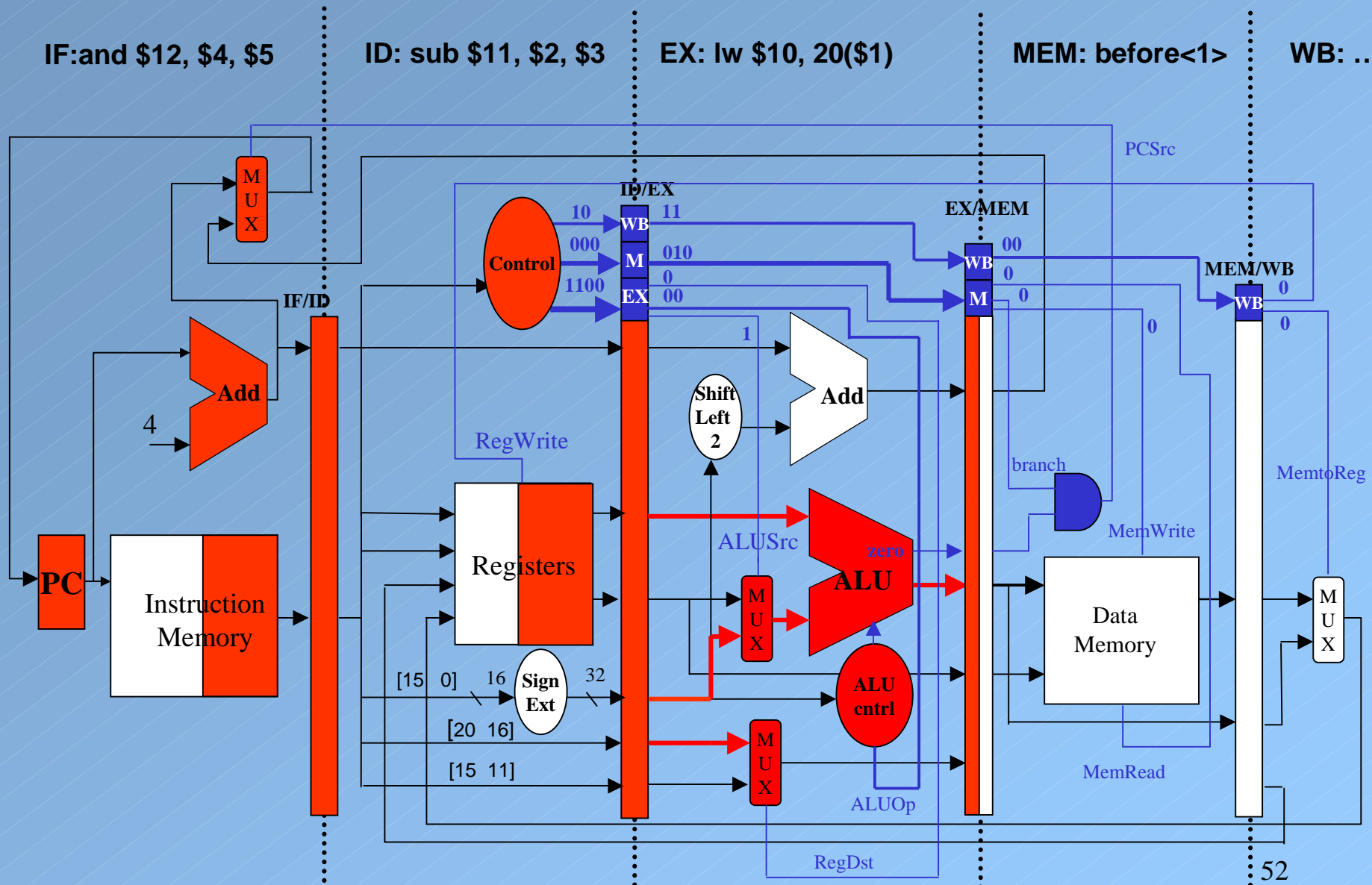

# Clock 4


IF: or \$13, \$6, \$7

ID: and \$12, \$4, \$5


EX: sub \$11, \$2, \$3

MEM: lw \$10, 20(\$1)

WB: ...

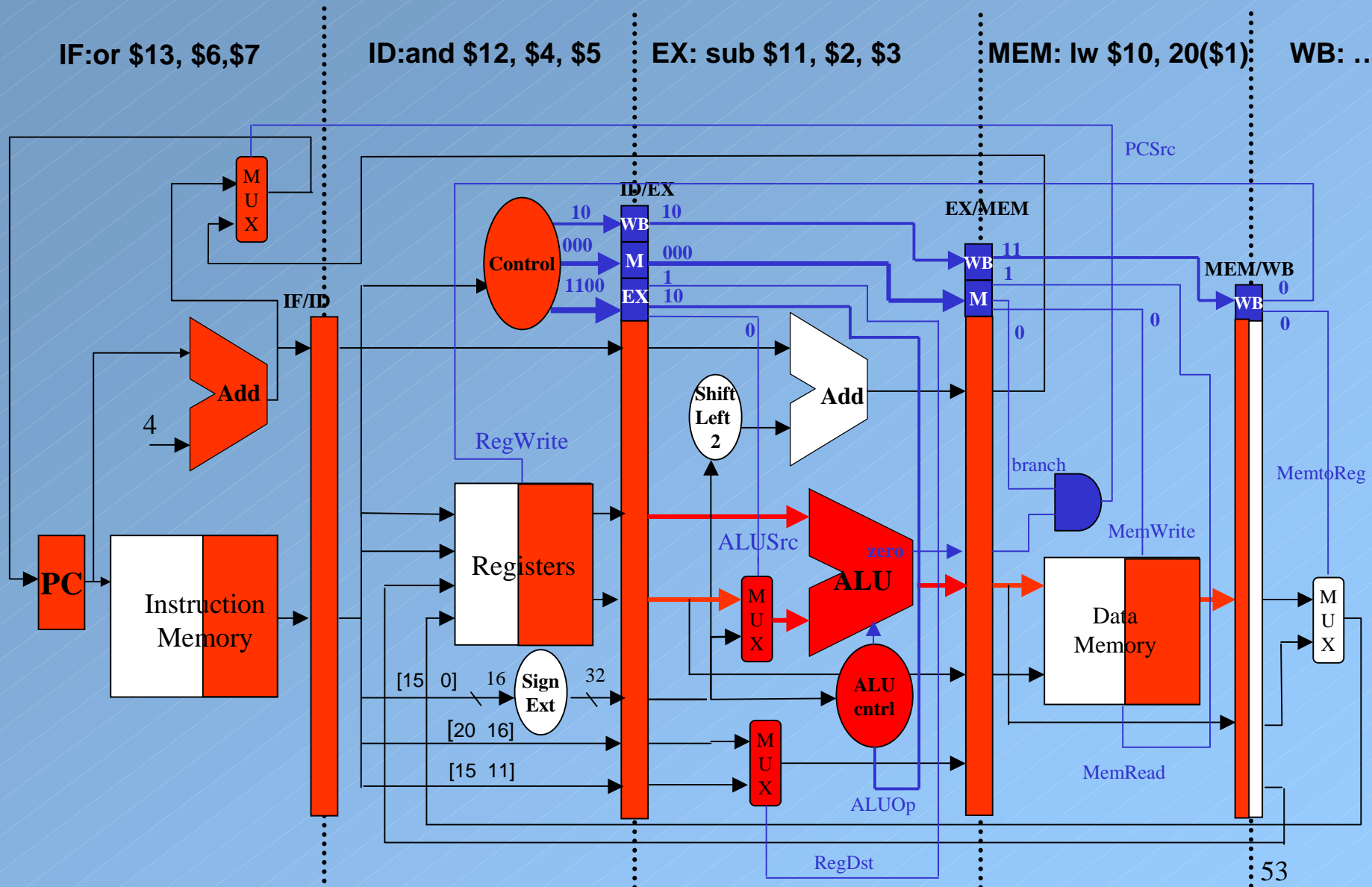

# Clock 5

 


## *Example: Exception in the Pipelined Datapath*

- 0x40      sub    \$11, \$2, \$4  
0x44      and    \$12, \$2, \$5  
0x48      or     \$13, \$2, \$6  
0x4C      add    \$1, \$2, \$1  
0x50      slt    \$15, \$6, \$7  
0x54      lw     \$16, 50(\$7)
- Suppose an overflow exception occurs in the add instruction.
- Exception handling routine  
0x40000040    sw     \$25, 1000(\$0)  
0x40000044    sw     \$26, 1004(\$0)

# Example: clock 6

causing an exception

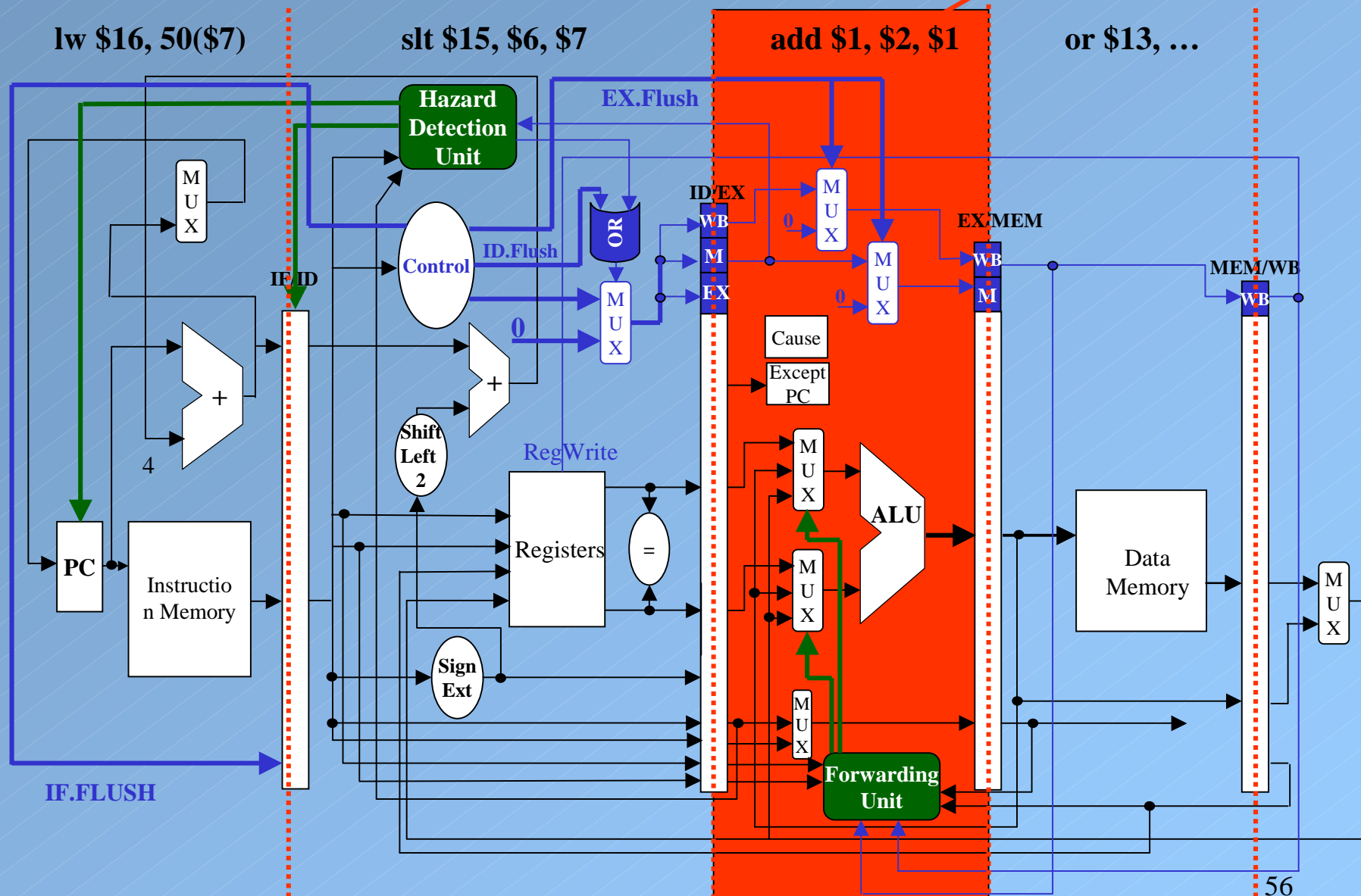



*Example: clock 7*

