

# *VHDL*

## *Modeling Digital Systems*

EL 310  
Erkay Savaş  
Sabancı University

# *Simulation and Synthesis*

- VHDL programs are unlike programs written in Pascal, C, C++.
- VHDL is for describing a digital system for mainly two purposes
  - Simulation
  - Synthesis
- The idea is to come up with a description that behaves like the real system with a desired level of accuracy


# *Describing System*

- A system is an assemblage of objects united by some form of regular interaction or interdependence
  - Could be anything from single chips to large supercomputers
- What aspects of a digital system we want to describe
  - Interface
  - Function: Structural or Behavioral
  - Structural and behavioral descriptions are complementary of each other and are expected to be supported by any HDL.

# *A digital system*


- Consists of
  - Binary signals that may take values of 1 or 0.
  - Components
    - Gates, flip-flops, counters, etc.
    - Transforms input signals to output signals
  - Wires that connect components.

- Half adder

 

a	b	sum	carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


# Events and Propagation Delays

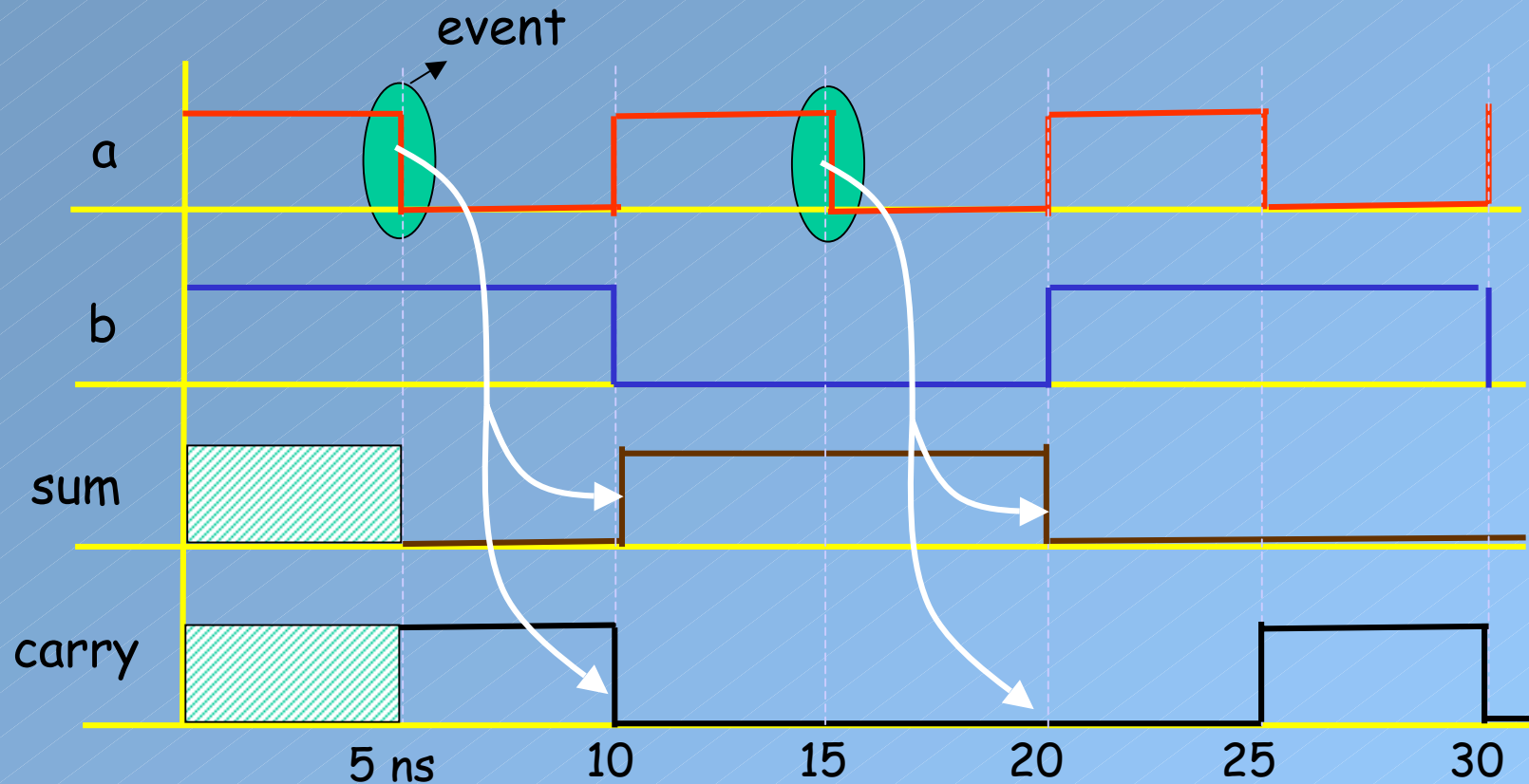

- Event: when a signal changes values (1-to-0, 0-to-1)
- Propagation delay: time elapsed before changes at input will produce a change at output (5 ns for this example)
 
# Concurrency of Operations

- From our previous example
  - When a change occurs at one of the inputs, say a, the two gates concurrently compute the values of output signals, sum and carry.
  - New events occur at these signals → trigger more events




Events on signals lead to computations that may generate events on other signals

# *Full Adder 1*

- Truth table

a	b	c_in	sum	carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


# Full Adder 2

 



 
# Waveforms and Timing

- The sequence of events that occur on a signal produces a waveform on that signal



$S'$	$R'$	clk	D	Q	$Q'$
0	1	X	X	1	0
1	0	X	X	0	1
1	1	R	1	1	0
1	1	R	0	0	1
0	0	X	X	?	?

 


# *Synchronous Circuit*


- Synchronous circuits operate with a periodic signal commonly referred to as clock.
  - clock serves as a common time base
  - The transition in clock (rising or falling) determines when the computation of output events is initiated.
  - The input value on signal is sampled at clock transition,
  - if there is an event on input signal before the clock transition occurs, the output may also change.
  - This change, of course, takes some time (propagation time).
 
# Asynchronous 1

- No global clock
  - Request-acknowledge protocols
  - Or handshaking
  - Need to wait for events on specific signals
  - Example: Asynchronous communication channels




# *Asynchronous 2*

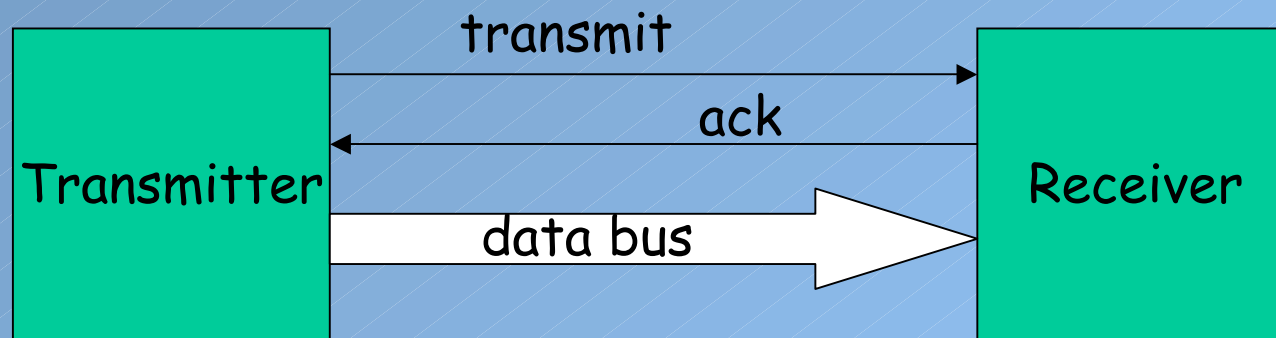

# *Signal Values*

- Binary values
  - 0 or 1  
(driven by a power supply or the output of a gate)
  - Voltage values
  - $[0-0.8] \text{ V} \rightarrow \text{logic 0}$
  - $[2.0 - 3.3] \text{ V} \rightarrow \text{logic 1}$
  - What if a signal is disconnected? (high-impedance)
  - What if a signal is currently driven to both a 0 and a 1 value? (unknown)
  - What if the initial value of a signal is unknown?
  - How about the signal strength.
- Recall that we want to describe a digital system as accurately as possible.

# Signal Values

 

- Question: Why do we want to represent a situation which apparently corresponds to a design error?
  - we may want to observe the effects of a design error.
  - how is it propagated?

# Signal Values: IEEE 1164

Value	Interpretation
U	Uninitialized
X	Forcing Unknown
0	Forcing 0
1	Forcing 1
Z	High impedance
W	Weak unknown
L	Weak 0
H	Weak 1
-	Don't care

- This nine valued system is not a part of VHDL language; but rather a standard definition that vendors are motivated to support for portability.

- Use the package that contains this definition.
- Not all these values are synthesizable.


## Signal Values: IEEE 1164

- IEEE 1164 package defines multivalued logic values
- logic operations for multivalued logic
- and some conversion routines from this logic to other types that are part of language
  - function `TO_BIT(S: STD_ULOGIC, XMAP: BIT := '0')`  
return `BIT`;
  - function `TO_BITVECTOR(S: STD_ULOGIC_VECTOR, XMAP: BIT := '0')`  
return `BIT_VECTOR`;
  - function `TO_STDULOGIC(B: BIT)`  
return `STD_ULOGIC`;


 
# Shared Signals

- Multiple drivers for input and multiple destinations for output signals
  - Bus construction
  - Drivers (transmitters): tri-state buffers can be controlled by a decoder to ensure that only one source is driving the bus at a time
  - There may be multiple receivers listening the bus



# Multiple Drivers

- Wired logic
  - Buses permit one transmitter at a time
  - However, certain forms of switching circuits are designed based on wired logic and permit multiple transmitters.
  - Wires in these circuits produce AND and OR Boolean functions.
  - wired-AND logic: if at least one device driving the signal to a 0, the value of the signal will be 0.
  - HDL must be expressive enough to describe such circuits for accurate simulation.
  - See resolved signals for this.
  - Synthesis compilers produce logic that arbitrates among accesses to shared signals. For example, when only one source is permitted then a decoder must be synthesized to control multiple drivers.

# Overview

- We seek to describe attributes of digital systems common to multiple levels of abstraction
  - Events, propagation delays, concurrency
  - Waveforms and timing (synchronous vs. asynchronous)
  - Shared signals
- Hardware description languages must provide constructs for naturally describing these attributes of a specific design
  - Simulators use such descriptions for mimicking the physical system
  - Synthesis compilers use such descriptions for synthesizing hardware