

Boolean Algebra

Logic and Digital System Design - CS 303

Erkay Savaş

Sabanci University

Boolean Algebra

- Algebra: A deductive mathematical system
 1. set of elements
 2. set of operators
 3. Number of unproved axioms (postulates)
- Set of elements
 - a set with countable number of elements
 - $S = \{a, b, c, d\}$
 - $x \in S$, and $y \notin S$
- Operators
 - binary operators: $x \text{ and } y \in S \rightarrow z \in S$
 - unary operators: $x \in S \rightarrow z \in S$

Axioms of Algebra

1. Closure:

- A set is closed w.r.t. a binary operation $*$
- Example: natural numbers are closed w.r.t. $(+)$

2. Associative law:

- $(x * y) * z = x * (y * z)$ for all $x, y, z \in S$

3. Commutative law:

- $x * y = y * x$ for all $x, y \in S$

4. Identity element:

- S is said to have a identity element e if $\exists e \in S$ such that $e * x = x * e = x$ for any $x \in S$
- Set of integers: $e = 1$ w.r.t. $\times$ and $e = 0$ w.r.t. $+$

Axioms of Algebra (cont.)

5. Inverse

- S having an identity element e w.r.t. $*$ is said to have an inverse for every $x \in S$, whenever there exists an element $y \in S$ such that
$$x * y = e$$
- Example: set of integers

6. Distributive law

- If $*$ and $\bullet$ are two binary operators on S , $*$ is said to be distributed over $\bullet$ whenever
- $$x * (y \bullet z) = (x * y) \bullet (x * z)$$

An Example of Algebraic Structure

- $S = \{0, 1, 2\}$ with $\times$ and $+$ forms an algebraic structure

+	0	1	2
0	0	1	2
1	1	2	0
2	2	0	1

$\times$	0	1	2
0	0	0	0
1	0	1	2
2	0	2	1

- additive identity 0
- multiplicative identity 1
- we have additive and multiplicative inverses
- $\times$ is distributed over $+$ (not vice versa)

Boolean Algebra - 1

- A set of elements B
 - There exist at least two elements $x, y \in B$ s. t. $x \neq y$
- Binary operators: $+$ and $\cdot$
 - closure w.r.t both $+$ and $\cdot$
 - additive identity 0
 - multiplicative identity 1
 - commutative w.r.t. both $+$ and $\cdot$
 - Associative w.r.t. both $+$ and $\cdot$
- Distributive law:
 - $\cdot$ is distributive over $+$
 - $+$ is distributive over $\cdot$
 - We do not have both in ordinary algebra

Boolean Algebra - 2

- Complement
 - For every element $x \in B$, there exist an element $x' \in B$ s. t.
 - a. $x + x' = 1$ and
 - b. $x \cdot x' = 0$.
 - Not available in ordinary algebra
- Differences btw ordinary and Boolean algebra
 - Ordinary algebra with real numbers
 - Boolean algebra with elements of set B
 - Complement
 - Distributive law
 - Do not substitute laws from one to another where they are not applicable

Two-Valued Boolean Algebra - 1

- To define a Boolean algebra
 - The elements of B
 - Rules for two binary operations
 - The elements of B and rules should conform to our axioms
- Two-valued Boolean algebra
 - $B = \{0, 1\}$

x	y	$x \cdot y$
0	0	0
0	1	0
1	0	0
1	1	1

X	y	$x + y$
0	0	0
0	1	1
1	0	1
1	1	1

x	x'
0	1
1	0

Two-Valued Boolean Algebra - 2

- Check the axioms
 - Two distinct elements, $0 \neq 1$
 - Closure, associative, commutative, identity elements
 - Complement
 - $x + x' = 1$ and $x \cdot x' = 0$
 - Distributive law

x	y	z
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

$y \cdot z$	$x + (y \cdot z)$
0	0
0	0
0	0
1	1
0	1
0	1
0	1
1	1

$x + y$	$x + z$	$(x + y) \cdot (x + z)$
0	0	0
0	1	0
1	0	0
1	1	1
1	1	1
1	1	1
1	1	1
1	1	1

Two-Valued Boolean Algebra - 2

- Two-valued Boolean algebra is actually equivalent to the binary logic defined heuristically before
 - Operations:
 - $\cdot \rightarrow$ AND
 - $+$ $\rightarrow$ OR
 - Complement $\rightarrow$ NOT
- Binary logic is application of Boolean algebra to the gate-type circuits
 - Two-valued Boolean algebra is developed in a formal mathematical manner
 - This formalism is necessary to develop theorems and properties of Boolean algebra

Duality Principle

- An important principle
 - every algebraic expression deducible from the axioms of Boolean algebra remains valid if the operators and identity elements are interchanged
- Example:
 - $x + x = x$.
 - $x + x = (x + x) \cdot 1$ (identity element)
 $= (x + x)(x + x')$ (complement)
 $= x + xx'$ (+ over ·)
 $= x$ (complement)
 - duality principle
 $x + x = x \quad \rightarrow \quad x \cdot x = x$

Duality Principle & Theorems

- Theorem a:

- $x + 1 = 1$

- $x + 1 = 1 \cdot (x + 1)$
 $= (x + x')(x + 1)$
 $= x + x' \cdot 1$
 $= x + x'$
 $= 1$

- Theorem b: (using duality)

- $x \cdot 0 = 0$

- Absorption Theorem

- a. $x + xy = x$

- b. $x \cdot (x+y) = x$

Involution & DeMorgan's Theorems

- Involution Theorem:

- $(x')' = x$
- $x + x' = 1$ and $x \cdot x' = 0$
- Complement of x' is $(x')'$
- Complement is unique

- DeMorgan's Theorem:

- $(x + y)' = x' \cdot y'$
- $(x \cdot y)' = x' + y'$

Truth Tables for DeMorgan's Theorem

$$-(x + y)' = x' \cdot y'$$

$$-(x \cdot y)' = x' + y'$$

x	y	x+y	(x+y)'	x · y	(x · y)'
0	0	0	1	0	1
0	1	1	0	0	1
1	0	1	0	0	1
1	1	1	0	1	0



x'	y'	x' · y'	x' + y'
1	1	1	1
1	0	0	1
0	1	0	1
0	0	0	0

Operator Precedence

1. Parentheses
2. NOT
3. AND
4. OR

- Example:

- $(x + y)'$
- $x' \cdot y'$
- $x + x \cdot y'$

Boolean Functions

- Consists of
 - binary variables (normal or complement form)
 - the constants, 0 and 1
 - logic operation symbols, "+" and "."
- Example:
 - $F_1(x, y, z) = x + y' z$
 - $F_2(x, y, z) = x' y' z + x' y z + xy'$

x	y	z	F ₁	F ₂
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	0	1
1	0	0	1	1
1	0	1	1	1
1	1	0	1	0
1	1	1	1	0

Logic Circuit Diagram of F_1

$$F_1(x, y, z) = x + y'z$$


 


Fig. 2-1 Gate implementation of $F_1 = x + y'z$

Logic Circuit Diagram of F_2


$$F_2 = x' y' z + x' y z + x y'$$

 

- Algebraic manipulation
- $F_2 = x' y' z + x' y z + x y'$
 $= x' z (y' + y) + x y'$
 $= x' z + x y'$

Alternative Implementation of F_2

$$F_2 = x' z + x y'$$

 

OTHER LOGIC OPERATORS - 1

- AND, OR, NOT are logic operators
 - defined by Boolean functions
 - three of the 16 possible Boolean functions


x	y	F ₀	F ₁	F ₂	F ₃	F ₄	F ₅	F ₆	F ₇
0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1

x	y	F ₈	F ₉	F ₁₀	F ₁₁	F ₁₂	F ₁₃	F ₁₄	F ₁₅
0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1


OTHER LOGIC OPERATORS - 2

- Some of the Boolean functions with two variables
 - Constant functions: $F_0 = 0$ and $F_{15} = 1$
 - AND function: $F_1 = xy$
 - OR function: $F_7 = x + y$
 - XOR function:
 - $F_6 = x' y + xy' = x \oplus y$ (x or y, but not both)
 - XNOR (Equivalence) function:
 - $F_9 = xy + x' y' = (x \oplus y)'$ (x equals y)
 - NOR function:
 - $F_8 = (x + y)' = (x \downarrow y)$ (Not-OR)
 - NAND function:
 - $F_{14} = (x y)' = (x \uparrow y)$ (Not-AND)


Logic Gate Symbols

 


NOT

 


TRANSFER

 


AND

 


XOR

 


OR

 

XNOR

 

NAND

 




NOR

Universal Gates


- NAND and NOR gates are universal
- We know any Boolean function can be written in terms of three logic operations:
 - AND, OR, NOT
- In return, NAND and NOR gate can implement these three logic gates

x	y	$(xy)'$	x'	y'	$(x' y')'$
0	0	1	1	1	0
0	1	1	1	0	1
1	0	1	0	1	1
1	1	0	0	0	1

NAND Gate

   


NOR Gate

 

 
Example - 1

- Two functions:
 - $F_1 = x' y + x y'$ and $F_2 = x' y' + x y$



Example - 2

$$- F_2 = x' y' + x y'$$

 

Multiple Input Gates

- AND and OR gates:
 - they are both commutative and associative
 - No problem with extending the number of inputs
- NAND and NOR gates
 - they are both commutative but not associative
 - Extending the number of inputs is not obvious
- Example:
 - $(x \uparrow y) \uparrow z \neq x \uparrow (y \uparrow z)$
 - $(x \uparrow y) \uparrow z = [(x y)' z]'$
 $= (x y) + z' = x y + z'$
 - $x \uparrow (y \uparrow z) = [x (y z)']'$
 $= x' + y z$

Nonassociativity of NOR operation


 
 


Fig. 2-6 Demonstrating the nonassociativity of the NOR operator; $(x \downarrow y) \downarrow z \neq x \downarrow (y \downarrow z)$


Multiple Input Universal Gates

- To overcome this difficulty, we define multiple-input NAND and NOR gates in slightly different manner


$$x \uparrow y \uparrow z = (x y z)'$$

 

 
$$x \downarrow y \downarrow z = (x + y + z)'$$




Multiple Input Universal Gates

 

(a) 3-input NOR gate

 

(b) 3-input NAND gate

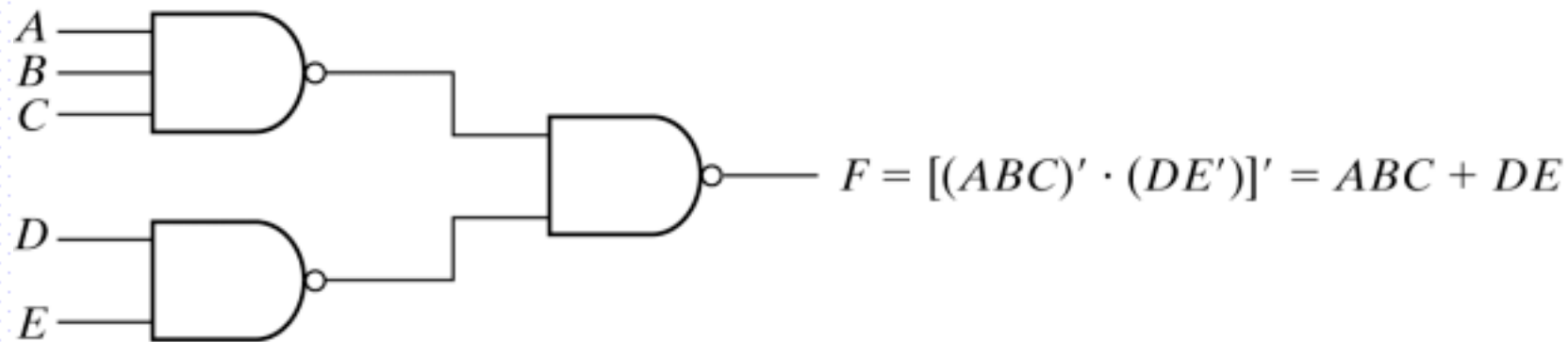


(c) Cascaded NAND gates


Fig. 2-7 Multiple-input and cascaded NOR and NAND gates

XOR and XNOR Gates

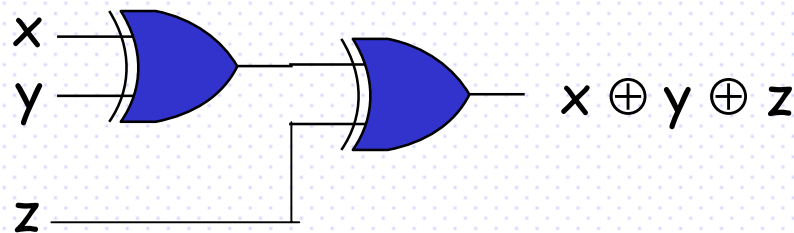
- XOR and XNOR operations are both commutative and associative.
- No problem manufacturing multiple input XOR and XNOR gates
- However, they are more costly from hardware point of view.
- Therefore, we usually have 2 input XOR and XNOR gates



3-input XOR Gates

 

(a) Using 2-input gates

 

(b) 3-input gate

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(c) Truth table

Fig. 2-8 3-input exclusive-OR gate

Algebraic Manipulations

- Previous example:

$$\begin{aligned} - F(x,y,z) &= x' y' z + x y z + x y' \\ &= x' z + x y' \end{aligned}$$

- The goal:

- The reduce the number of terms
- The reduce the number of literals in a term
- to simplify the circuit

- Examples:

$$- x(x'+y) = xy \text{ and } x+x' y = (x+x')(x+y) = x+y$$

$$\begin{aligned} - (x+y)(x+y') &= xx + xy' + xy + yy' \\ &= x + xy' + xy \\ &= x + x(y+y') \\ &= x + x = x \end{aligned}$$

Consensus Theorem

- $xy + x'z + yz$

$$= xy + x'z + yz(x + x')$$

$$= xy + x'z + xyz + x'yz$$

$$= xy(1 + z) + x'z(1 + y)$$

$$= xy + x'z$$

- From duality:

$$(x + y)(x' + z)(y + z) = (x + y)(x' + z)$$

Complement of a Function - 1

- F' is complement of F
 - We can obtain F' , by interchange of 0's and 1's in the truth table
 - We can also utilize DeMorgan's Theorem
 - $(x+y)' = x' y'$
 - $(A+B+C)'$
 - $= (A+x)'$
 - $= A' x'$
 - $= A' (B+C)' = A'B'C'$
- We can generalize DeMorgan's Theorem
 1. $(x_1 + x_2 + \dots + x_N)' = x_1' \cdot x_2' \cdot \dots \cdot x_N'$
 2. $(x_1 \cdot x_2 \cdot \dots \cdot x_N)' = x_1' + x_2' + \dots + x_N'$

Complement of a Function - 2

- Example:

- $F_1 = x'yz' + x'y'z$

- $F_1' = (x'yz' + x'y'z)'$
 $= (x'yz')'(x'y'z)'$
 $= (x + y' + z)(x + y + z')$

- $F_2 = x(y'z' + yz)$

- $F_2' = (x(y'z' + yz))'$
 $= x' + (y'z' + yz)'$
 $= x' + (y'z')'(yz)'$
 $= x' + (y + z)(y' + z')$

- Important: Somewhat easier method is to take the dual of the function and complement each literal

Canonical & Standard Forms

- Minterms
 - A binary variable may appear in its normal (x) and its complement form (x')
 - How many different terms we can get with x and y ?
 - $x'y'$, $x'y$, xy' , and $xy \rightarrow 00, 01, 10, 11$
 - m_0, m_1, m_2, m_3 (AND terms or minterms, standard product)
 - n variables can be combined to form 2^n minterms
- Maxterms (OR Terms, standard sums)
 - $M_0 = x + y$
 - $M_1 = x + y'$
 - $M_2 = x' + y$
 - $M_3 = x' + y'$

Min- & Maxterms with $n = 3$

			Minterms		Maxterms	
x	y	z	term	designation	term	designation
0	0	0	$x'y'z'$	m_0	$x + y + z$	M_0
0	0	1	$x'y'z$	m_1	$x + y + z'$	M_1
0	1	0	$x'yz'$	m_2	$x + y' + z$	M_2
0	1	1	$x'yz$	m_3	$x + y' + z'$	M_3
1	0	0	$xy'z'$	m_4	$x' + y + z$	M_4
1	0	1	$xy'z$	m_5	$x' + y + z'$	M_5
1	1	0	xyz'	m_6	$x' + y' + z$	M_6
1	1	1	xyz	m_7	$x' + y' + z'$	M_7

Boolean Functions in Standard Form

x	y	z	F ₁	F ₂
0	0	0	0	1
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- $F_1(x, y, z) = m_1 + m_4 + m_7 = \Sigma (1, 4, 7)$
- $F_2(x, y, z) = m_0 + m_3 + m_5 + m_6 + m_7 = \Sigma (0, 3, 5, 6, 7)$

Important Properties

- Any Boolean function can be expressed as a sum of minterms
- Example:
 - $F_1' = \Sigma (0, 2, 3, 5, 6)$
 $= x'y'z' + x'yz' + x'yz + xy'z + xyz'$
 - How do we find the complement of F_1' ?
 - $F_1 = (x + y + z)(x + y' + z)(x + y' + z')(x' + y + z')(x' + y' + z)$
 $= M_0 + M_2 + M_3 + M_5 + M_6$
 $= \Pi (0, 2, 3, 5, 6)$
- Any Boolean function can be expressed as a product of maxterms

Canonical Form

- If a Boolean function is expressed as a sum of minterms or product of maxterms the function is said to be in canonical form.
- Example: $F = x + y'z \rightarrow$ canonical form?
 - No
 - But we can put it in canonical form.
 - $F = x + y'z = \Sigma(7, 6, 5, 4, 1)$
- Alternative way:
 - Obtain the truth table first and then the canonical term.

Example: Product of Maxterms

- $F = xy + x'z$
 - Use the distributive law + over ·
 - $F = (xy + x') \cdot (xy + z)$
$$= (x + x') \cdot (y + x') \cdot (x + z) \cdot (y + z)$$
$$= (y + x') \cdot (x + z) \cdot (y + z)$$
$$= (y + x' + zz') \cdot (x + z + yy')$$
$$= (x' + y + z) \cdot (x' + y + z') \cdot (x + y + z) \cdot (x + y' + z)$$
$$\cdot (x + y + z) \cdot (x' + y + z)$$
 - $= \Pi(4, 5, 0, 2)$

Conversion Between Canonical Forms

- Fact:
 - The complement of a function (given in sum of minterms) can be expressed as a sum minterms missing from the original function
- Example:
 - $F(x, y, z) = \Sigma (1, 4, 5, 6, 7)$
 - $F'(x, y, z) = \Sigma (0, 2, 3) = m_0 + m_2 + m_3.$
 - Now take the complement of F' and make use of DeMorgan's theorem
 - $(F')' = (m_0 + m_2 + m_3)' = (m_0' \cdot m_2' \cdot m_3')$
 - $F = M_0 \cdot M_2 \cdot M_3 = \Pi (0, 2, 3)$

General Rule for Conversion


- Important relation:
 - $m_j' = M_j$.
 - $M_j' = m_j$.
- The rule:
 - Interchange symbols Π and Σ , and
 - list those terms missing from the original form
- Example: $F = xy + x'z$
 - derive the truth table
 - Obtain the sum of minterms form
 - $F = \Sigma(1, 3, 6, 7)$
 - $F = \Pi(0, 2, 4, 5)$

Standard Forms


- Fact:
 - Canonical forms are very seldom the ones with the least number of literals
- Alternative representation:
 - Standard form
 - a term may contain any number of literals
 - Two types
 1. the sum of products
 2. the product of sums
 - Examples:
 - $F_1 = y' + xy + x'yz'$
 - $F_2 = x(y' + z)(x' + y + z')$

 Example: Standard Forms

- $F_1 = y' + xy + x'yz'$
- $F_2 = x(y' + z)(x' + y + z')$



(a) Sum of Products

 

(b) Product of Sums


Fig. 2-3 Two-level implementation

Nonstandard Forms

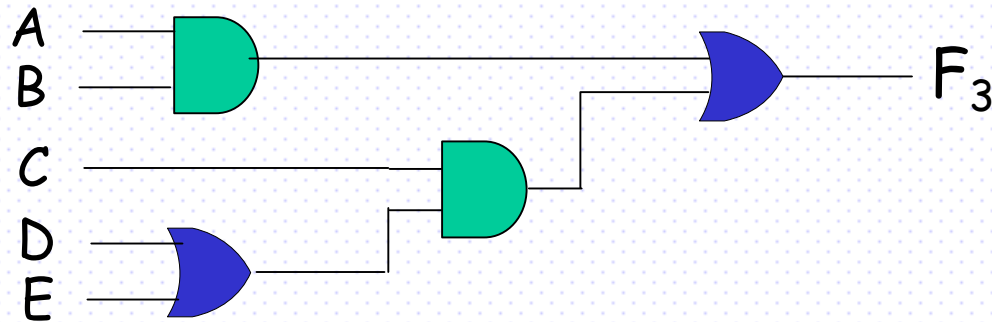- Example:


- $F_3 = AB + C(D + E)$

- This hybrid form yields three-level implementation



- We can always get the standard form

- $F_3 = AB + CD + CE$

 

Positive & Negative Logic

- In digital circuits, we have two digital signal level:
 - H - (higher signal level; e.g. 3 ~ 4 V)
 - L - (lower signal level; e.g. 0 ~ 1 V)
- There is no logic-1 or logic-0 at the circuit level
- We can do any assignment we wish
 - For example:
 - $H \rightarrow \text{logic-1}$
 - $L \rightarrow \text{logic-0}$



(a) Positive logic



(b) Negative logic

Fig. 2-9 signal assignment and logic polarity

Signal Designation - 1




x	y	F
L	L	L
L	H	H
H	L	H
H	H	H

- What kind of logic function does it implement?


Signal Designation - 2

x	y	F
0	0	0
0	1	1
1	0	1
1	1	1

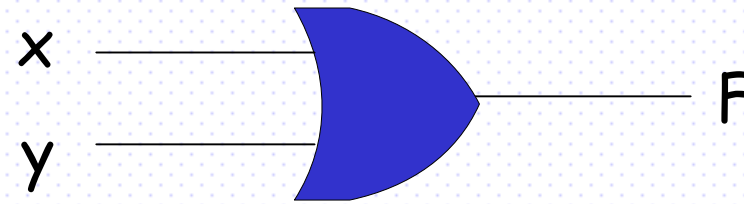

positive logic


x	y	F
1	1	1
1	0	0
0	1	0
0	0	0

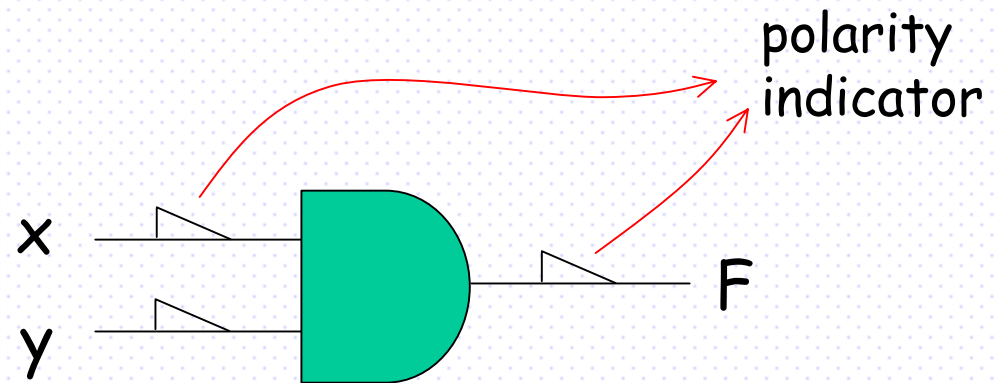

negative logic

Integrated Circuits

 - IC - silicon semiconductor crystal ("chip") that contains gates.
 - gates are interconnected inside to implement a Boolean function
 - Chip is mounted in a ceramic or plastic container
 - Inputs & outputs are connected to the external pins of the IC.
 - Many external pins (14 to several thousands)



Levels of Integration

- SSI (small-scale integration):
 - Up to 100 electronic components per chip
- MSI (medium-scale integration):
 - From 100 to 3,000 electronic components per chip
- LSI (large-scale integration):
 - From 3,000 to 100,000 electronic components per chip
- VLSI (very large-scale integration):
 - From 100,000 to 1,000,000 electronic components per chip
- ULSI (ultra large-scale integration):
 - More than 1 million electronic components per chip

Digital Logic Families

- Circuit Technologies
- TTL → transistor-transistor logic
- ECL → Emitter-coupled logic
 - fast
- MOS → metal-oxide semiconductor
 - high density
- CMOS → Complementary MOS
 - low power

Parameters of Logic Gates - 1


- Fan-out
 - load that the output of a gate drives
 - standard load may be defined as the amount of current needed by the input of a gate of the same family.
 - Maximum fan-out specifies the fan-out that the output can drive without impairing the gate performance
 - Example: the input to an inverter can have load equal to 1.0 standard load.
 - If a, say NAND, gate drives six such inverters, then the fan-out is equal to 6.0 standard loads.
 - The transition time of a gate is affected by the fan-out in CMOS technology
 - Thus, maximum fan-out is the standard load with which the transition time is no greater than the maximum allowable value.

Parameters of Logic Gates - 2

- Fan-in
 - number of inputs that a gate can have in a particular logic family
 - In principle, we can design a CMOS NAND or NOR gate with a very large number of inputs
 - In practice, however, we have some limits
 - 4 for NOR gates
 - 6 for NAND gates
- Power dissipation
 - power consumed by the gate that must be available from the power supply

Parameters of Logic Gates - 3

 - Propagation delay:
 - the time required for a change in value of a signal to propagate from input to output.




Computer-Aided Design - 1

- CAD
 - Design of digital systems with VLSI circuits containing millions of transistors is not easy and cannot be done manually.
- To develop & verify digital systems we need CAD tools
 - software programs that support computer-based representation of digital circuits.
- Design process
 - design entry
 - ...
 - database that contains the photomask used to fabricate the IC

Computer-Aided Design - 2

- Different physical realizations
 - ASIC (application specific integrated circuit)
 - FPGA
 - PLD
- For every piece of device we have an array of software tools to facilitate
 - design,
 - testing,
 - and even programming


Xilinx Foundation

 

Schematic Editor

- Editing programs for creating and modifying schematic diagrams on a computer screen
 - schematic capturing or schematic entry
 - you can drag-and-drop digital components from a list in an internal library (gates, decoders, multiplexers, registers, etc.)
 - You can draw interconnect lines from one component to another

Schematic Editor

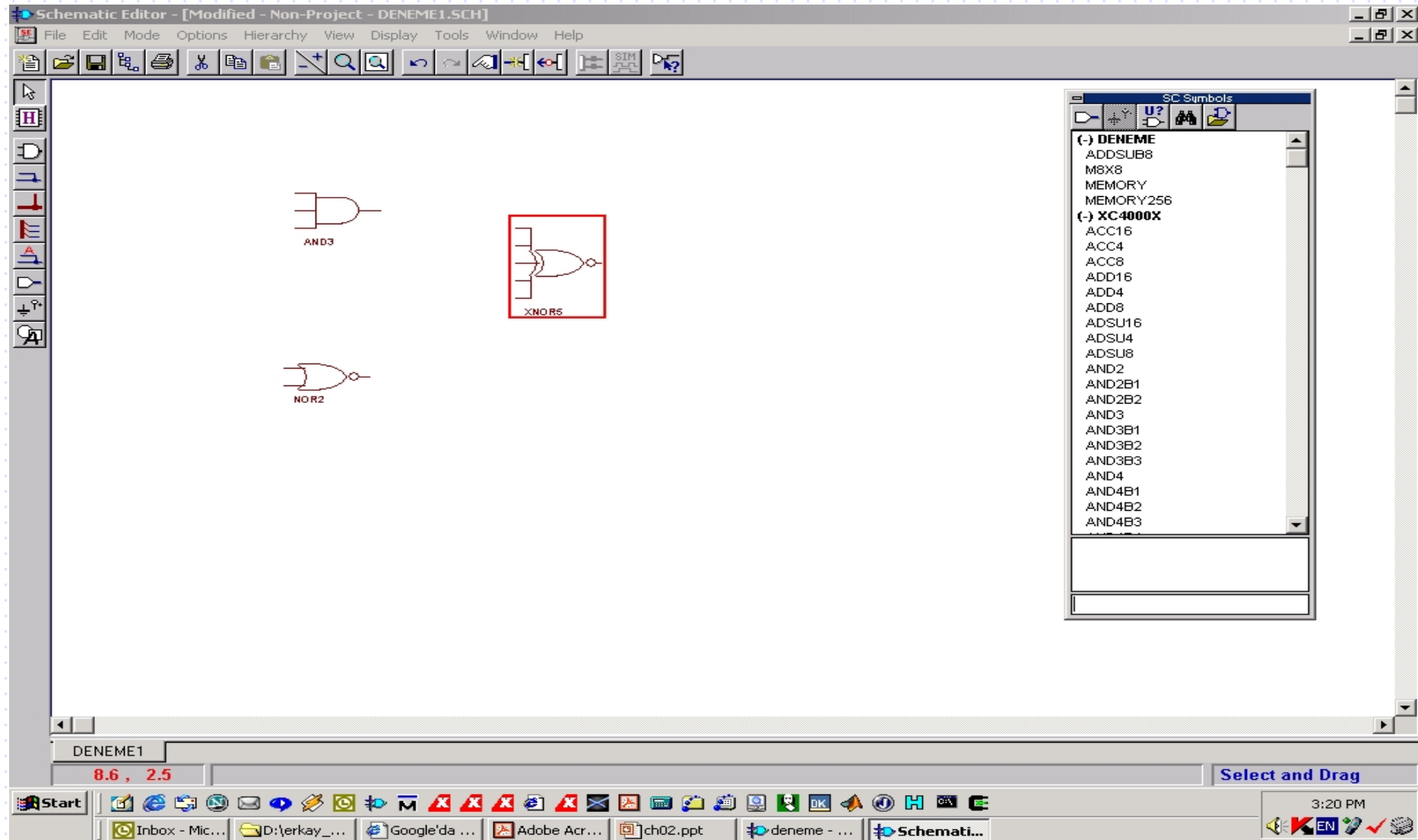

Hardware Description Languages

- HDL
 - Verilog
 - VHDL
 - resembles a programming language
 - designed to describe digital circuits so that we can develop and test digital circuits